

# **Verilog Codes for Basic Digital Components**

W. J. Dally and E. C. Harting, “Digital  
Design, a Systems Approach,” 2012  
Chap. 8: Combinational Building Block

# Outlines

- Combinational Logic
  - multiplexers, de-multiplexers
  - encoder, decoder, priority encoder
  - ripple carry adder
  - saturation adder
  - logical and arithmetic shifter
  - ALU
  - Dot Product
- Sequential Logic
  - latch, asynchronous reset latch
  - flip-flop, asynchronous/synchronous reset flip-flop
  - register file
  - clock gating
  - finite state machine (FSM)
  - shift registers
  - FIR Filter
- Memory
  - ROM, RAM

# Combinational Logic

# multiplexer (1/2)

```
module mux4_1 (  
  output reg out,  
  input i0, i1, i2, i3,  
  s1, s0);
```

```
  always @(*)  
  begin  
    case ({s1, s0})  
      2'd0 : out = i0;  
      2'd1 : out = i1;  
      2'd2 : out = i2;  
      2'd3 : out = i3;  
    end  
  end
```

```
endmodule
```

```
module mux4_1 (  
  output out,  
  input i0, i1, i2, i3, s1, s0);
```

```
  assign out = s1 ? (s0 ? i3 : i2) : (s0 ?  
    i1 : i0);
```

```
endmodule
```

# multiplexer (2/2)

```
// MUX3 with one-hot select
module MUX3_onehot (a2, a1, a0, s,
b);
parameter k = 32;
input [k-1:0] a0, a1, a2;
input [2:0] s; // one-hot select
output [k-1:0] b;
reg [k-1:0] b;

always @ (*) begin
    case (s)
        3'b001: b = a0;
        3'b010: b = a1;
        3'b100: b = a2;
        default: b = {k{1'bx}};
    endcase
end
endmodule
```

```
// MUX3 with binary select
module MUX3_onehot (a2, a1, a0,
s, b);
parameter k = 32;
input [k-1:0] a0, a1, a2;
input [1:0] s; // binary select
output [k-1:0] b;
reg [k-1:0] b;

always @ (*) begin
    case (s)
        0: b = a0;
        1: b = a1;
        2: b = a2;
        default: b = {k{1'bx}};
    endcase
end
endmodule
```

# demultiplexer

```
module demux1_4 (  
  output reg out0, out1, out2, out3;  
  input in,  
  input [1:0] s );  
  
  always @(s, in)  
  case (s)  
    2'b00: begin out0 = in;    out1=1'bz; out2=1'bz; out3=1'bz; end  
    2'b01: begin out0 = 1'bz; out1=in;    out2=1'bz; out3=1'bz; end  
    2'b10: begin out0 = 1'bz; out1=1'bz; out2=in;    out3=1'bz; end  
    2'd11: begin out0 = 1'bz; out1=1'bz; out2=1'bz; out3=in;    end  
    default: $display ("Invalid control signals");  
  endcase
```

# encoder

```
module encoder (  
  input i3, i2, i1, i0,  
  output reg [1:0] out);  
  
  always @(i3, i2, i1, i0)  
    valid = 1;  
    case ({i3, i2, i1, i0})  
      4'b1000: out = 2'b11;  
      4'b0100: out = 2'b10;  
      4'b0010: out = 2'b01;  
      4'b0001: out = 2'b00;  
    endcase  
  
endmodule
```

# priority encoder

```
module priority_enc42  
(input i3, i2, i1, i0,  
  output reg [1:0] out;)
```

```
  always @(i3, i2, i1, i0)  
  casex ({i3, i2, i1, i0})  
    4'b1xxx: out = 2'b11;  
    4'b01xx: out = 2'b10;  
    4'b001x: out = 2'b01;  
    default : out = 2'b00;  
  endcase
```

```
// 8:3 priority encoder  
module priority_enc83 (r, b);  
  input [7:0] r;  
  output [2:0] b;  
  reg [2:0] g;
```

```
  assign b = g;  
  always @ (*) begin  
    casex®  
      8'bxxxxxxx1: g = 0;  
      8'bxxxxxxx10: g = 1;  
      8'bxxxxxx100: g = 2;  
      8'bxxxxx1000: g = 3;  
      8'bxxx10000: g = 4;  
      8'bxx100000: g = 5;  
      8'bx1000000: g = 6;  
      8'b10000000: g = 7;  
      default: g = x;  
    endcase  
  end  
endmodule
```



# decoder (1/3)

```
module decoder (  
input [1:0] in;  
output reg out0, out1, out2, out3) ;  
  
always @(in)  
case (in)  
    2'b00: begin out0=1; out1=0; out2=0; out3=0; end  
    2'b01: begin out0=0; out1=1; out2=0; out3=0; end  
    2'b10: begin out0=0; out1=0; out2=1; out3=0; end  
    2'd11: begin out0=0; out1=0; out2=0; out3=1; end  
endcase  
  
endmodule
```

# decoder (2/3)

```
module decoder_index  
(in1, out1);  
parameter N=8;  
parameter log2N = 3;  
input [log2N-1: 0] in1;  
output reg [N-1:0] out1;
```

```
  
always @ (in1) begin  
    out1 = 0;  
    out1[in1] = 1'b1;  
end  
  
endmodule
```

```
module decoder_loop (in1, out1);  
parameter N=8;  
parameter log2N = 3;  
input [log2N-1: 0] in1;  
output reg [N-1:0] out1;  
  
integer i;  
  
always @ (in1)  
    for (i=0; i<N; i=i+1)  
        out1[i] = (in1 == i);  
  
endmodule
```

# decoder (3/3)

```
// n-to-m decoder  
module Dec (a, b);  
  parameter n=3;  
  parameter m=8;  
  input [n-1: 0] a;  
  output [m-1:0] b;  
  
  assign b = 1 << a;  
  
endmodule
```

# Ripple Carry Adder (RCA) using always

```
always @ (*) begin
```

```
    c[0] = cin;
```

```
    for (i=0; i<=31; i++)
```

```
        {c[i+1], s[i]} = a[i] + b[i] + c[i];
```

```
    cout = c[32];
```

```
end
```

```
// the for loop will be unrolled as follows
```

```
// {c[1],s[0]}=a[0]+b[0]+c[0];
```

```
// {c[2],s[1]}=a[1]+b[1]+c[1];
```

```
...
```

```
// {c[32],s[31]}=a[31]+b[31]+c[31];
```

# RCA (gate primitive vs. logical operator)

```
module ripple_adder(co, sum, a0, a1, ci);
parameter N=4;
output [N-1:0] sum;
output co;
input [N-1:0] a0, a1;
input ci;
wire [N-1:0] carry;
```

```
assign carry[0]=ci;
```

```
genvar i;
```

```
generate
```

```
    for (i=0; i<N; i=i+1)
```

```
    begin: r_loop
```

```
        wire t1, t2, t3;
```

```
        xor g1(t1, a0[i], a1[i]);
```

```
        xor g2(sum[i], t1, carry[i]);
```

```
        and g3(t2, a0[i], a1[i]);
```

```
        and g4(t3, t1, carry[i]);
```

```
        or g5(carry[i+1], t2, t3);
```

```
    end
```

```
endgenerate
```

```
assign co = carry[N]
```

```
endmodule
```

```
module ripple_adder(co, sum, a0, a1, ci);
parameter N=4;
output [N-1:0] sum;
output co;
input [N-1:0] a0, a1;
input ci;
```

```
wire [N-1:0] p = a0 ^ a1;
```

```
wire [N-1:0] g = a0 & a1;
```

```
wire [N:0] carry = {g | ( p & carry[N-1:0] ), ci};
```

```
// carry[0] = ci;
```

```
// carry[1] = g[0] | ( p[0] & carry[0] );
```

```
// carry[2] = g[1] | ( p[1] & carry[1] );
```

```
// carry[3] = g[2] | ( p[2] & carry[2] );
```

```
// carry[4] = g[3] | ( p[3] & carry[3] );
```

```
assign sum = p ^ carry[N-1:0];
```

```
assign co = carry [N];
```

```
endmodule+
```

# RCA (always vs. logic perators)

```
module ripple_adder(co, sum, a0, a1, ci);
parameter N=4;
output [N-1:0] sum;
output co;
input [N-1:0] a0, a1;
input ci;
wire [N:0] carry;

assign carry[0]=ci;

always @ (a0 or a1)
begin
for (i=0; i<N; i=i+1)
    {carry[i+1], sum[i]} = a0[i] + a1[i] +
    carry[i] ;
end

assign co = carry[N]

endmodule
```

```
module ripple_adder(co, sum, a0, a1, ci);
parameter N=4;
output [N-1:0] sum;
output co;
input [N-1:0] a0, a1;
input ci;
wire [N:0] carry;

assign carry[0]=ci;

always @ (a0 or a1)
begin
for (i=0; i<N; i=i+1)
    begin
        carry[i+1] = a0[i]&a1[i] | a0[i]&carry[i] |
        a1[i]&carry[i];
        sum[i] = a0[i]^a1[i]^carry[i];
    end
end

assign co = carry[N]

endmodule
```

# RCA with **generate** loop

- use **generate** loop to duplicate module instances
  - e.g. in FA-cascaded RCA
- or simple
  - **array of instances**

```
// structural level modeling
module RCA (sum, c_out, a, b, c_in);

    output [3:0] sum;
    output c_out;
    input [3:0] a, b;
    input c_in;

    wire c1, c2, c3;

    // construct 4-bit adder fulladd4 from
    // previously defined module fulladd

    fulladd fa0 (sum[0], c1, a[0], b[0], c_in);
    fulladd fa1 (sum[1], c2, a[1], b[1], c1);
    fulladd fa2 (sum[2], c3, a[2], b[2], c2);
    fulladd fa3 (sum[3], c_out, a[3], b[3], c3);

endmodule
```

```
module RCA_generate (sum, c_out, a, b, c_in);
    parameter N=4;
    output [N-1:0] sum;
    output c_out;
    input [N-1:0] a, b;
    input c_in;
    wire [N:0] c;

    assign c[0]=c_in;

    genvar i;
    generate
        for (i=0; i<=N-1; i=i+1)
            begin: FA_loop // block named "FA_loop"
                fulladd fa (sum[i], c[i+1], a[i], b[i], c[i]);
                // fulladd FA_loop[0].fa ( sum[0], c[1], a[0], b[0], c[0] );
                // fulladd FA_loop[1].fa ( sum[1], c[2], a[1], b[1], c[1] );
                // fulladd FA_loop[2].fa ( sum[2], c[3], a[2], b[2], c[2] );
                // fulladd FA_loop[3].fa ( sum[3], c[4], a[3], b[3], c[3] );
            end
    endgenerate

    // fulladd FA_loop[0:3] (sum[0:3], c[1:4], a[0:3], b[0:3], c[0:3]);

    assign c_out = c[N];

endmodule
```

# Verilog code for Saturation Adder

- clip the computation results to a fixed range

```
wire signed [7:0] a, b, tmp, max, min;
reg signed [7:0] sum;

assign max = 8'd127; // max = 0111_1111
assign min = 8'd-128; // min = 1000_0000
assign tmp = a + b;
always @ (*) begin
    if ( a[7] == b[7] && tmp[7] != a[7] ) // carry[ [8] != carry]7]
        sum = a[7] ? min : max; // sum = { a[7], 7{~a[7]} };
    else
        sum = tmp;
end
```



# left/right shifter

```
module shifter (  
    input left,  
    input [2:0] shift_amt,  
    input [7:0] data_in,  
    output [7:0] shifted_data);  
  
    assign shifted_data = (left) ? data_in << shift_amt : data_in >>  
        shift_amt;  
  
endmodule
```

# wrap-around barrel shifter

```
module barrel_shift (n, a, b);

parameter k=8;
parameter lk=3;
input [lk-1:0] n;  // how much to shift
input [k-1:0] a;  // number to shift
output [k-1:0] b; // the output

wire [2*k-2:0] x = a << n; // output before wrapping

assign b = x[k-1 : 0] | {1'b0, x[2k-2 : k] };

endmodule
```

# arithmetic shift (<<<, >>>) in Verilog-2001

```
// Verilog-2001


integer data_value,
        data_value_1995,
        data_value_2001;

...
data_value = -9;                // stored as 1111_..._1111_0111
...
data_value_1995 = data_value >> 3; // stored as 0001_..._1111_1110
...
data_value_2001 = data_value >>> 3; // stored as 1111_..._1111_1110
                                   // repeat sign bit during arithmetic right shift
...
data_value_1995 = data_value << 3; // stored as 1111_..._1011_1000
...
data_value_2001 = data_value <<< 3; // stored as 1111_..._1011_1000
                                   // repeat sign bit during arithmetic left shift
// give an example where the logical left shift << 3 is different from arithmetic shift
// e.g., data_value2 = 32'b 1110_xxx ....
```

# ALU

```
module MIPSALU (  
  input [31:0] a, b;  
  input [3:0] ALU_ctl;  
  output reg [31:0] ALU_out;  
  output Zero );  
  
  assign Zero = (ALU_out == 0);  
  
  always @ (ALU_ctl, a, b)  
    case (ALU_ctl)  
      4'd0 : ALU_out = a & b;  
      4'd1 : ALU_out = a | b;  
      4'd 2 : ALU_out = a + b;  
      4'd6 : ALU_out = a - b;  
      4'd 7: ALU_out = (a < b) ? 1 : 0;  
      4'd12: ALU_out = ~(a | b);  
      default: ALU_out = 32'b0;  
    endcase  
  
endmodule
```

ALU control lines	Function
0000	AND
0001	OR
0010	add
0110	subtract
0111	set on less than
1100	NOR

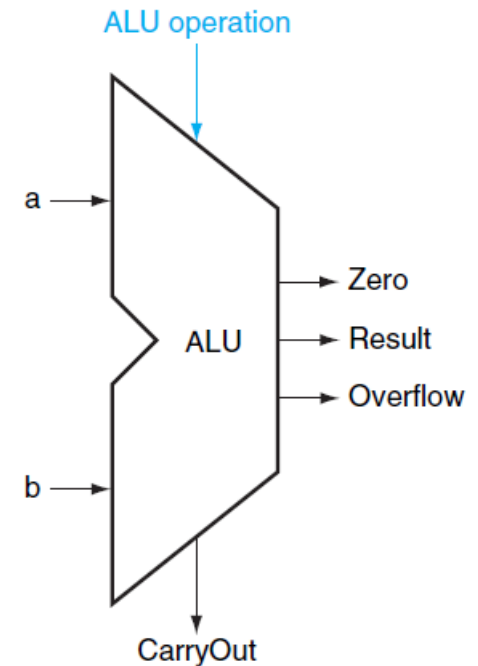

# Dot Product 4 (DP4)

- 4-D dot-product:  $a[0]*b[0] + a[1]*b[1] + a[2]*b[2] + a[3]*b[3]$

```
module DP4 (input[16*4-1:0]in_a, in_b, output [31:0]out);  
  wire [15:0] a[3:0], b[3:0];
```

```
  // convert two long bit-vectors in_a, in_b into two arrays a, b  
  assign {a[3],a[2],a[1],a[0]}=in_a;  
  assign {b[3],b[2],b[1],b[0]}=in_b;
```

```
  integer i;  
  reg [31:0] tmp[0:3];  
  always @ (*) begin  
    tmp[0] = a[0]*b[0];  
    for (i=1; i<=3; i=i+1) tmp[i] = a[i]*b[i] + tmp[i-1];  
  end
```

```
  assign out = tmp[3];
```

```
endmodule
```

# DPn

- n-D dot-product

```
module #parameter n=4 DPn (input[16*n-1:0]in_a, in_b, output [31:0]out);
reg [15:0] a[n-1:0];
reg [15:0] b[n-1:0];
integer i;
always@ (*) begin // convert two long bit-vectors into two arrays
    for (i=0; i<n; i=i+1) begin
        a[i]= in_a[16*i +:16];
        b[i]= in_b[16*i +:16];
    end
end

reg [31:0] tmp[0:n];
always @ (*) begin
    tmp[0] = 0;
    for (i=0; i<=n-1; i=i+1) tmp[i+1] = a[i]*b[i] + tmp[i];
end
assign out = tmp[n];
endmodule
```

# Pipelined DP4

- see previous lectures for pure CL DP4
  - first convert I/O ports into arrays; then pipeline it

```
module DP4 (input clk, input[16*4-1:0]in_a, in_b, output reg [31:0]out);
wire [15:0] a[3:0];
wire [15:0] b[3:0];
assign {a[3],a[2],a[1],a[0]}=in_a;
assign {b[3],b[2],b[1],b[0]}=in_b;
integer i;
reg [31:0] pipe1_tmp[0:3], pipe2_tmp[1:4];
always @(posedge clk) begin
    for (i=0; i<=3; i=i+1) pipe1_tmp[i] <= a[i]*b[i];
end
always @ (posedge clk) begin
    pipe2_tmp[1] = pipe1_tmp[0];
    for (i=1; i<=3; i=i+1) pipe2_tmp[i+1] <= pipe2_tmp[i] + pipe1_tmp[i];
    out<= pipe2_tmp[4];
end
endmodule
```

# Pipelined DPn

- parametrized long bit-vectors as I/O ports

```
module #parameter n=4 DPn (input clk, input[16*n-1:0]in_a, in_b, output reg [31:0]out);
reg [15:0] a[n-1:0];
reg [15:0] b[n-1:0];
integer i;
always@ (*) begin
    for (i=0; i<n; i=i+1) begin
        a[i]= in_a[16*i+:16];
        b[i]= in_b[16*i+:16];
    end
end
reg [31:0] pipe1_tmp[0:n-1], pipe2_tmp[1:n];
always @(posedge clk) begin
    for (i=0; i<=n-1; i=i+1) pipe1_tmp[i] <= a[i]*b[i];
end
always @ (*) begin
    pipe2_tmp[1] = pipe1_tmp[0];
    for (i=1; i<=n-1; i=i+1) pipe2_tmp[i+1] = pipe2_tmp[i] + pipe1_tmp[i];
end
always @ (posedge clk) begin
    out <= pipe2_tmp[n];
end
endmodule
```



# Sequential Logic

# **Latches and Flip-Flops**


# Sequencing Elements (Latch and Flip-Flop)


 
## Latch: *Level sensitive*

- pass input to output at **time interval** when level of control is logic 1
- a.k.a. transparent latch

```
// Verilog code for latch
always @ (CLK or D)
  if (CLK) Q <= D;
```






## Flip-Flop: *edge triggered*

- pass input to output at the **moment** of clock rising or falling edge
- a.k.a. opaque edge-triggered flip-flop

```
// Verilog code for DFF
always @ (posedge CLK)
  Q <= D;
```

# latch vs. FF

   


# register inference



- D latch
  - with asynchronous set
  - with asynchronous reset
  - with asynchronous set/reset
- D flip flop
  - with asynchronous set
  - with asynchronous reset
  - with asynchronous set/reset
  - with synchronous set
  - with synchronous reset
  - with synchronous and asynchronous load

# D Latches in TSMC 0.18um Cell Library


**TLAT**  
active-high

 



G	D	Q[n+1]	QN[n+1]
1	0	0	1
1	1	1	0
0	x	Q[n]	QN[n]

  


**TLATN**  
active-low

 



GN	D	Q[n+1]	QN[n+1]
0	0	0	1
0	1	1	0
1	x	Q[n]	QN[n]

  

 
**TLATNR**  
asynchronous  
active-low  
reset





RN	GN	D	Q[n+1]	QN[n+1]
1	0	0	0	1
1	0	1	1	0
1	1	x	Q[n]	QN[n]
0	x	x	0	1

 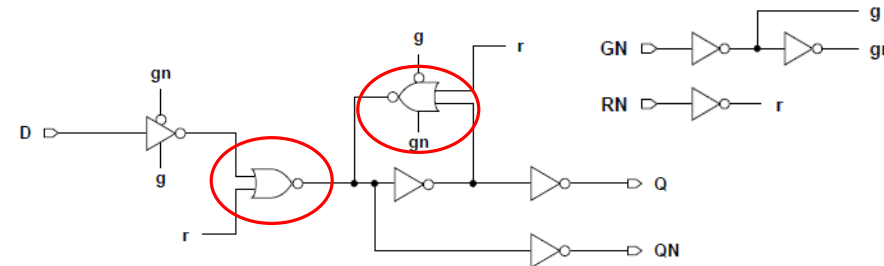

 **TLATNSR**  
asynchronous  
active-low  
set/reset




RN	SN	GN	D	Q[n+1]	QN[n+1]
1	1	0	0	0	1
1	1	0	1	1	0
1	1	1	x	Q[n]	QN[n]
0	1	x	x	0	1
1	0	x	x	1	0
0	0	x	x	1	0

  


# DFFs in TSMC 0.18um Cell Library


## DFF

 


D	CK	Q[n+1]	QN[n+1]
0		0	1
1		1	0
x		Q[n]	QN[n]

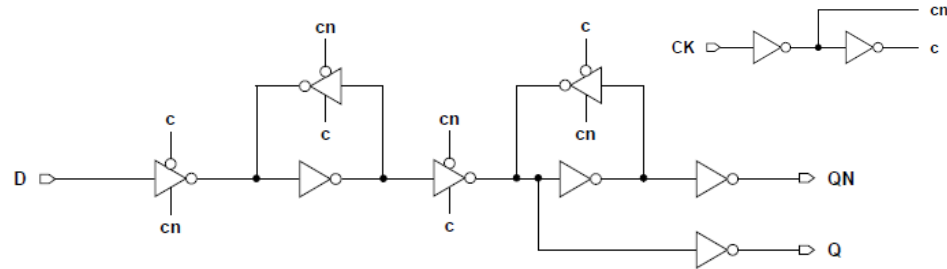


## DFFR asynchronous active-low

 


RN	D	CK	Q[n+1]	QN[n+1]
0	x	x	0	1
1	0		0	1
1	1		1	0
1	x		Q[n]	QN[n]

 


## DFFTR synchronous active-low

 


RN	D	CK	Q[n+1]	QN[n+1]
0	x		0	1
x	x		Q[n]	QN[n]
1	0		0	1
1	1		1	0

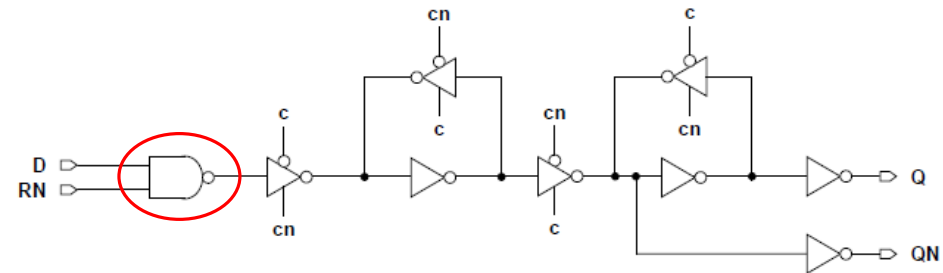
 
## DFFSR asynchronous active-low set/reset




RN	SN	D	CK	Q[n+1]	QN[n+1]
0	1	x	x	0	1
1	0	x	x	1	0
0	0	x	x	1	0
1	1	0		0	1
1	1	1		1	0
1	1	x		Q[n]	QN[n]

 
 
# inferring simple D-latch

- always @ (clk or d) ...
  - lclk evel-sensitive

```
module d_latch (GATE, DATA, Q);  
  input GATE, DATA;  
  output Q;  
  reg Q;  
  
  always @(GATE or DATA)  
    if (GATE)  
      Q = DATA;  
  
endmodule
```





```
module d_CL (  
  input gate, data,  
  output reg q );  
  
  // infer a combinational logic,  
  // not a latch  
  always @ (gate or data)  
    if (gate)  
      q <= data;  
    else  
      q <= 'b0;  
  
endmodule
```



  
# D Latch Circuit using CMOS

- constructed from back-to-back inverters


 
# D-latch with asynchronous set (active-low)


```
module d_latch_async_set (GATE, DATA, SET, Q);  
    input GATE, DATA, SET;  
    output Q;  
    reg Q;  
  
    //synopsys async_set_reset "SET"  
    always @(GATE or DATA or SET)  
        if (~SET)  
            Q = 1'b1;  
        else if (GATE)  
            Q = DATA;  
endmodule
```


 
# D-latch with **asynchronous reset (active-low)**

- sensitive list includes control signals and input data signals

```
module d_latch_async_reset (RESET, GATE, DATA, Q);  
    input RESET, GATE, DATA;  
    output Q;  
    reg Q;  
  
    //synopsys async_set_reset "RESET"  
    always @ (RESET or GATE or DATA)  
        if (~RESET)  
            Q = 1'b0;  
        else if (GATE)  
            Q = DATA;  
    endmodule
```




# D-latch with asynchronous set and reset (active-low)

```
module d_latch_async (GATE, DATA, RESET, SET, Q);
    input GATE, DATA, RESET, SET;
    output Q;
    reg Q;


    // synopsys async_set_reset_local infer "RESET, SET"
    // synopsys one_cold "RESET, SET"
    always @ (GATE or DATA or RESET or SET)
    begin : infer
        if (!SET)
            Q = 1'b1;
        else if (!RESET)
            Q = 1'b0;
        else if (GATE)
            Q = DATA;
    end

     // synopsys translate_off
    always @ (RESET or SET)
        if (RESET == 1'b0 & SET == 1'b0)
            $write ("ONE-COLD violation for RESET and SET.");
    // synopsys translate_on
endmodule
```


 
# latch with **asynchronous set and reset**


```
module d_latch_async (  
  input gate, data, reset_n, set_n;  
  output reg q;  
  
  always @ (gate, data, reset_n, set_n)  
    if (!set_n) q <= 1'b1;  
    else if (!reset_n) q <= 1'b0;  
    else if (gate) q <= data;  
  
endmodule
```



 
# inferring D-flipflop

- always @ (posedge clk) ...
  - clk edge-triggered

```
module dff_pos (DATA, CLK, Q);  
  input DATA, CLK;  
  output Q;  
  reg Q;  
  
  always @(posedge CLK)  
    Q <= DATA;  
endmodule
```




 
```
module dff_neg (DATA, CLK, Q);  
  input DATA, CLK;  
  output Q;  
  reg Q;  
  
  always @(negedge CLK)  
    Q <= DATA;  
endmodule
```


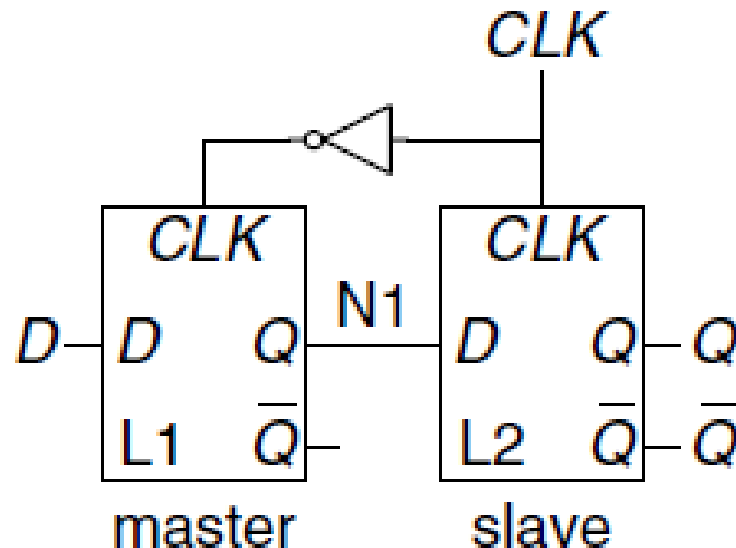 
# Logic of D Flip-Flop


- composed of master and slave D-latches
- triggered at the time instance of clock edge
  - unlike latch which is active (transparent) when clock is at logic level of high




# D Flip-Flop using CMOS

- constructed from two D latches (either dynamic or static)
  - cell library usually adopts static design

Dynamic  
DFF

 

Static  
DFF

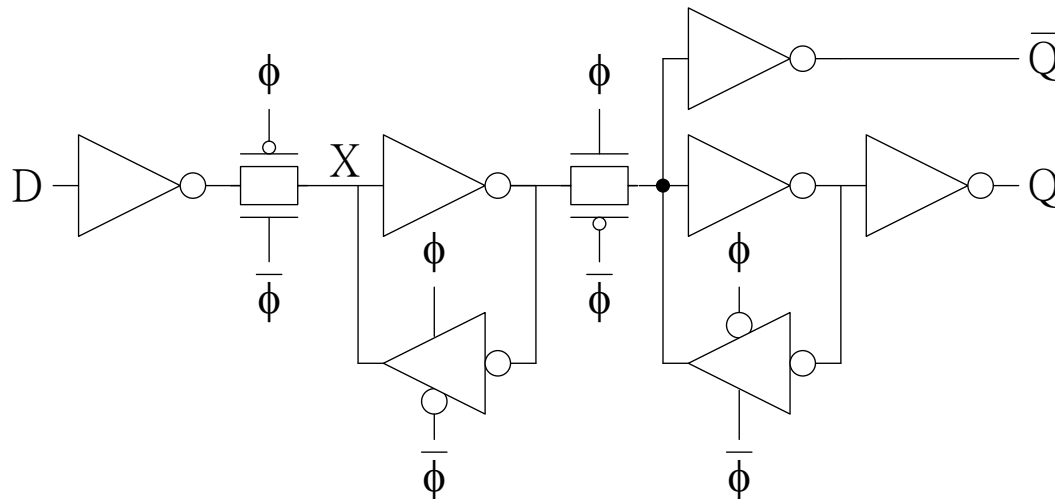



 
# DFF with **asynchronous set (active-low)**


- sensitive list includes edges of both clock and control signals
  - synthesized into hardware different from normal DFF

```
module dff_async_set (DATA, CLK, SET, Q);  
  input DATA, CLK, SET;  
  output Q;  
  reg Q;  
  
  always @(posedge CLK or negedge SET)  
    if (~SET)  
      Q <= 1'b1;  
    else  
      Q <= DATA;  
endmodule
```



 
# DFF with asynchronous reset (active-high)

```
module dff_async_reset (DATA, CLK, RESET, Q);  
  input DATA, CLK, RESET;  
  output Q;  
  reg Q;  
  
  always @(posedge CLK or posedge RESET)  
    if (RESET)  
      Q <= 1'b0;  
    else  
      Q <= DATA;  
endmodule
```


 
# DFF with asynchronous set and reset (active-high)

```
module dff_async (RESET, SET, DATA, Q, CLK);  
    input CLK;  
    input RESET, SET, DATA;  
    output Q;  
    reg Q;  
  
    // synopsys one_hot "RESET, SET"  
    always @(posedge CLK or posedge RESET or  
            posedge SET)  
        if (RESET)  
            Q <= 1'b0;  
        else if (SET)  
            Q <= 1'b1;  
        else Q <= DATA;  
  
    // synopsys translate_off  
    always @ (RESET or SET)  
        if (RESET + SET > 1)  
            $write ("ONE-HOT violation for RESET and SET.");  
    // synopsys translate_on  
endmodule
```



# DFF with asynchronous set and reset

```
module dff_async (  
  input clk, reset, set, data,  
  output reg q);
```


```
  always @ (posedge clk or posedge reset or posedge set)
```

```
    if (reset) q <= 1'b0;
```

```
    else if (set) q <= 1'b1;
```

```
    else q <= data;
```


```
endmodule
```

 
 
# DFF with **synchronous set (active-high)**


- sensitive list includes only clock signal
  - synthesized into normal DFF with extra combinational logic for the input data

```
module dff_sync_set (DATA, CLK, SET, Q);  
  input DATA, CLK, SET;  
  output Q;  
  reg Q;  
  
  //synopsys sync_set_reset "SET"  
  always @(posedge CLK)  
    if (SET)  
      Q <= 1'b1;  
    else  
      Q <= DATA;  
endmodule
```



 
# DFF with **synchronous reset (active-low)**

```
module dff_sync_reset (DATA, CLK, RESET, Q);  
  input DATA, CLK, RESET;  
  output Q;  
  reg Q;  
  
  //synopsys sync_set_reset "RESET"  
  always @(posedge CLK)  
    if (~RESET)  
      Q <= 1'b0;  
    else  
      Q <= DATA;  
endmodule
```




 
# DFF with **synchronous and asynchronous load**

```
module dff_a_s_load (ALOAD, SLOAD, ADATA, SDATA, CLK, Q);  
  input ALOAD, ADATA, SLOAD, SDATA, CLK;  
  output Q;  
  reg Q;  
  
  always @ (posedge CLK or posedge ALOAD)  
    if (ALOAD)  
      Q <= ADATA;  
    else if (SLOAD)  
      Q <= SDATA;  
endmodule
```





# Resettable DFF Circuits using CMOS



Symbol

  

Synchronous Reset

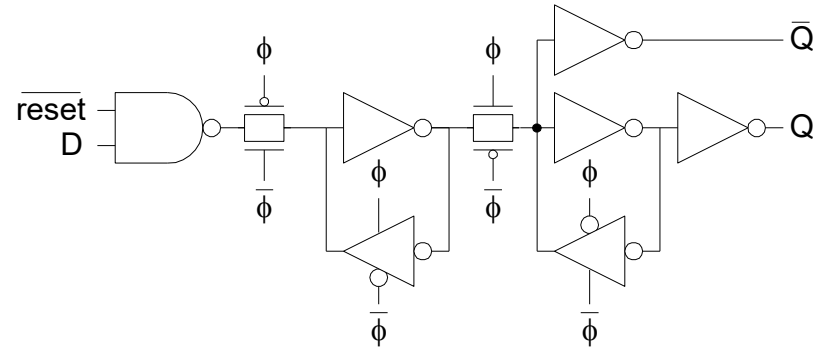 

Asynchronous Reset

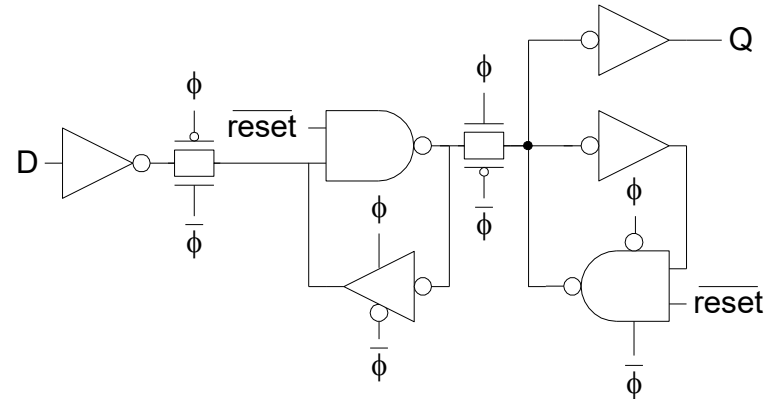 



# register file

- register file is composed of registers
  - can access many registers at the same time
    - cp. single-port RAM which can access only one data

```
module RegisterFile (r_adr1, r_adr2, data1, data2, w_adr, w_data, w_cntl, clk)
input [5:0] r_adr1, r_adr2, w_adr;
input [31:0] w_data;
input w_cntl, clk;
output [31:0] data1, data2;
reg [31:0] RF [0:31];

// read from register file
assign data1 = RF[r_adr1];
assign data2 = RF[r_adr2];

// write to register file
always @ (posedge)
    if (w_cntl) RF[w_adr] = w_data;


endmodule
```

# Clock gating methods

- Method 1 (unsafe gclk with possible glitches)


```
assign gclk = clk && enable ;

 always@(posedge gclk or negedge nrst)
begin
    if(!nrst)
        Q <= 8'd0;
    else
        Q <= D ;
end
```



- Method2 (high switching activity of clk )
 
```
always@(posedge clk or negedge nrst)
begin
    if(!nrst)
        Q <= 8'd0;
    else if(enable)
        Q <= D ;
end
```



# **Finite State Machine (FSM)**

# Two types of Sequential Logic


- Pipeline
  - break long datapath into several stages, each realized in one clock cycle
  - use pipelined registers to cut the combinational logic into several stages
  - better pipelining with balanced delay for each pipeline stage
- Finite State Machine (FSM)
  - generate control signals for datapath components
  - use registers to store the states
  - output depends on either the current states, and/or the current inputs

# Pipeline


```
module pipelined (  
  input [31:0] A, B, C;  
  input clk;  
  output [63:0] out);  
  
  reg [63:0] C_pipe1;  
  reg [63:0] out_pipe1, out_pipe2;  
  
  always @ (posedge clk) begin  
    out_pipe1 <= A*B;  
    C_pipe1 <= C;  
  end  
  
  always @(posedge clk)  
    out_pipe2 <= out_pipe1 + C_pipe1;  
  
  assign out = out_pipe2;  
  
endmodule
```
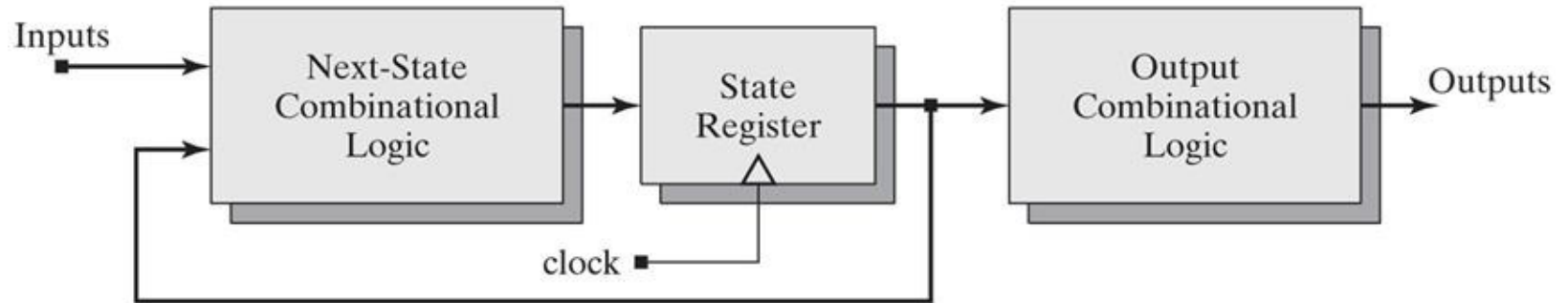
# Moore vs. Mealy FSM

- Moore FSM
  - output is a function of only present state



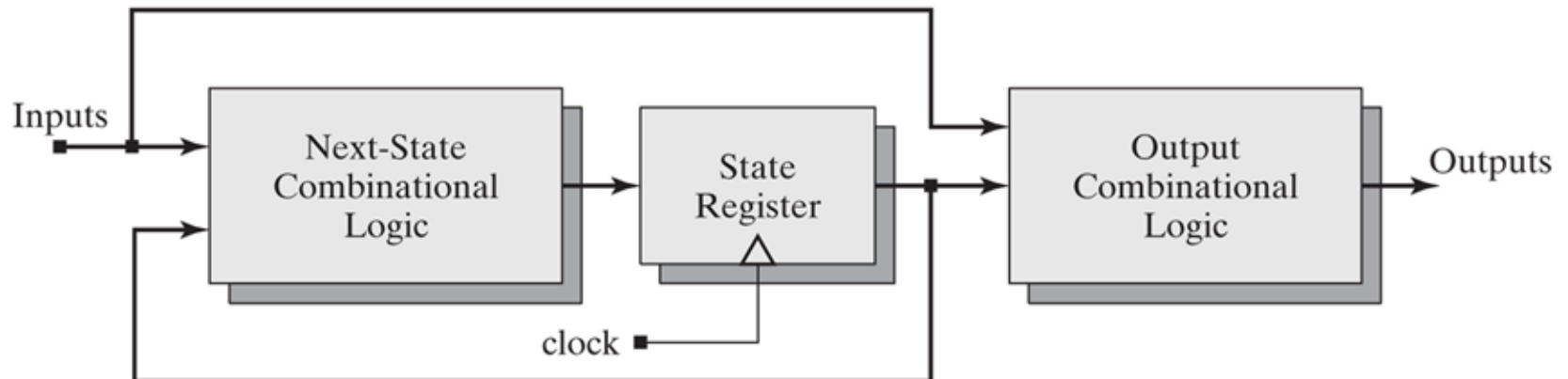- Mealy FSM
  - output is a function both present state and input




# FSM (Finite State Machine)

```
// lower section of FSM
always @ (posedge clk, posedge rst) begin
    if (rst == 1) pr_state <= ... ;
    else          pr_state <= nx_state;
    // out <= temp_out;    // for stored output
end

// upper section of FSM
always @ (pr_state, input) begin
case pr_state
    state1: begin
        tmp_out = ...; // Moore machine
        if ( input == ...) nx_state = ...;
        else nx_state = ...;
    end
    state2: ...
    ...
endcase
end

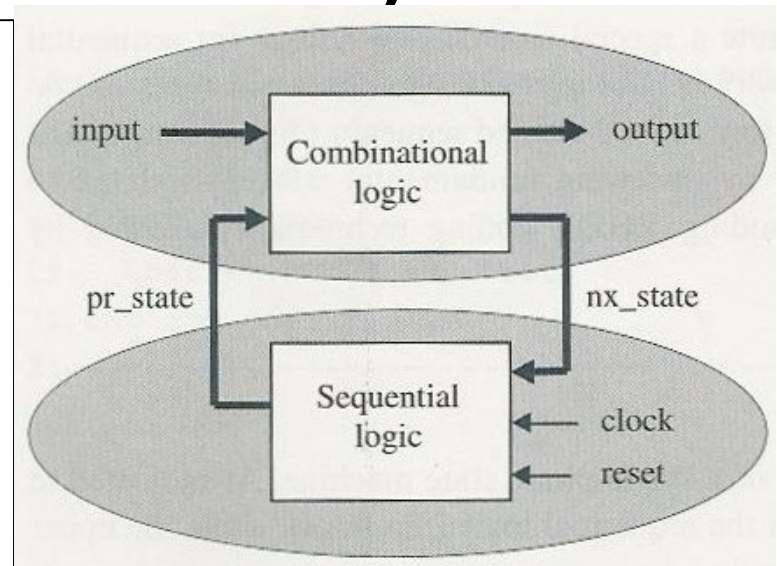// output section for not non-stored output
assign out = tmp_out;
```



Mealy FSM:  
 $output = f(input, pr\_state)$   
 $nx\_state = g(input, pr\_state)$


# Example: Newspaper Vendor Machine

- . newspaper costs 15 cents
- . accept coins of nickels (5 cents) and dimes (10 cents) only
- . do not return extra money

State	Money
S0	0 cents
S5	5 cents
S10	10 cents
S15	15 cents

Input	coin[1:0]
x0	2'b00
x5	2'b01
x10	2'b10
-	don't care



 

# FSM Example: Vendor Machine (1/7)

## binary encoding of states


```
module vend(coin, clock, reset, newspaper);  
input [1:0] coin;  
input clock;  
input reset;  
output newspaper;  
wire newspaper;  
wire [1:0] NEXT_STATE;  
reg [1:0] PRES_STSTE;
```

```
// state encodings (binary)  
// cp. one-hot encoding  
parameter s0 = 2'b00;  
parameter s5 = 2'b01;  
parameter s10 = 2'b10;  
parameter s15 = 2'b11;
```

State	Money
S0	0 cents
S5	5 cents
S10	10 cents
S15	15 cents


  

Input	coin[1:0]
x0	2'b00
x5	2'b01
x10	2'b10
-	don't care

 

# FSM Example: Vendor Machine (2/7)
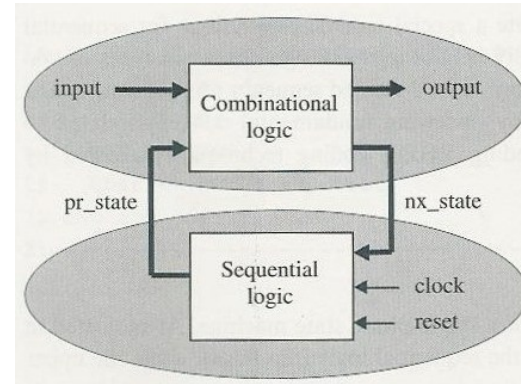
## generate output/next states (combinational logic in upper FSM)



// combinational logic


```
function [2:0] fsm;
input [1:0] fsm_coin;
input [1:0] fsm_PRESTATE;
reg fsm_newspaper;
reg [1:0] fsm_NEXT_STATE;
begin
```

```
case (fsm_PRESTATE)
```

State	Money
S0	0 cents
S5	5 cents
S10	10 cents
S15	15 cents

Input	coin[1:0]
x0	2'b00
x5	2'b01
x10	2'b10
-	don't care

 

# FSM Example: Vendor Machine (3/7)


## generate output and next state for each present state

```

s0: // state = s0
begin

if (fsm_coin == 2'b10) begin
    fsm_newspaper = 1'b0;
    fsm_NEXT_STATE = s10; end
else if (fsm_coin == 2'b01) begin
    fsm_newspaper = 1'b0;
    fsm_NEXT_STATE = s5; end
else begin
    fsm_newspaper = 1'b0;
    fsm_NEXT_STATE = s0; end


end
    
```

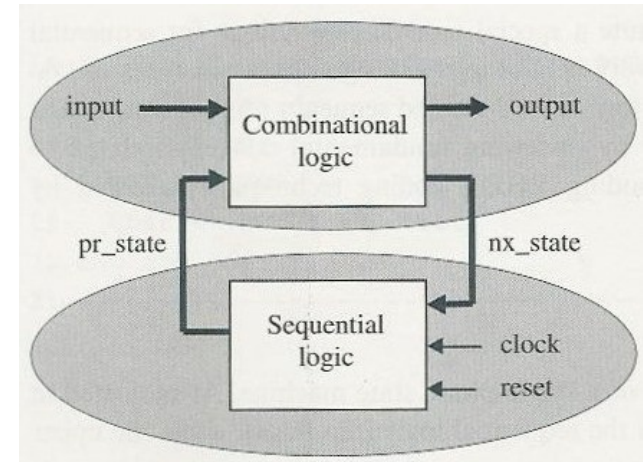

State	Money
S0	0 cents
S5	5 cents
S10	10 cents
S15	15 cents

Input	coin[1:0]
x0	2'b00
x5	2'b01
x10	2'b10
-	don't care

 


# FSM Example: Vendor Machine (4/7)

## generate output and next state for each present state

```

s5: // state = s5
begin
  if (fsm_coin == 2'b10) begin
    fsm_newspaper = 1'b0;
    fsm_NEXT_STATE = s15; end
  else if (fsm_coind == 2'b01) begin
    fsm_newspaper = 1'b0;
    fsm_NEXT_STATE = s10; end
  else begin
    fsm_newspaper = 1'b0;
    fsm_NEXT_STATE = s5; end
end


```

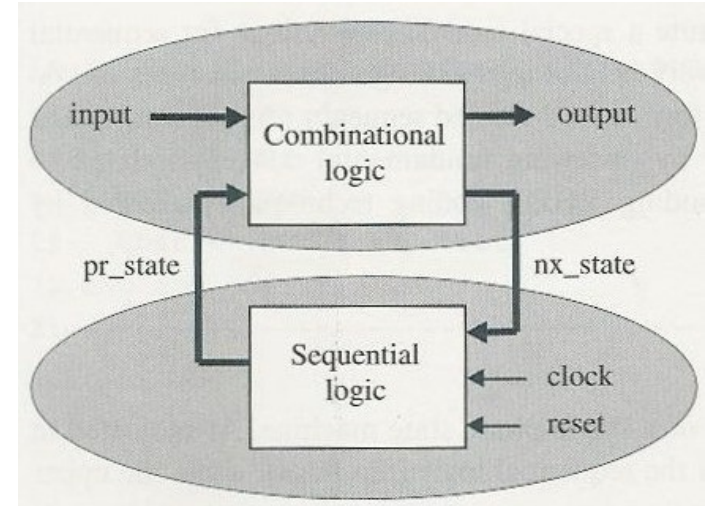

State	Money
S0	0 cents
S5	5 cents
S10	10 cents
S15	15 cents

Input	coin[1:0]
x0	2'b00
x5	2'b01
x10	2'b10
-	don't care



 



# FSM Example: Vendor Machine (5/7)

## generate output and next state for each present state

```
s10: // state = s10
begin
```

```
if (fsm_coin == 2'b10) begin
    fsm_newspaper = 1'b0;
    fsm_NEXT_STATE = s15; end
else if (fsm_coind == 2'b01) begin
    fsm_newspaper = 1'b0;
    fsm_NEXT_STATE = s15; end
else begin
    fsm_newspaper = 1'b0;
    fsm_NEXT_STATE = s10; end
```

```
end
```

 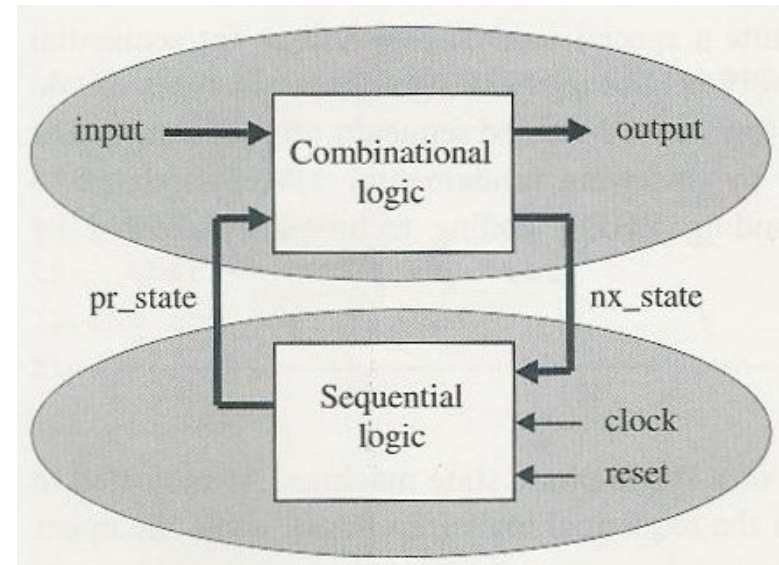

# FSM Example: Vendor Machine (6/7)

## generate output and next state for each present state

```

s15: // state = s15
begin
    fsm_newspaper = 1'b1;
    fsm_NEXT_STATE = s0;
end


endcase

```

State	Money
S0	0 cents
S5	5 cents
S10	10 cents
S15	15 cents

Input	coin[1:0]
x0	2'b00
x5	2'b01
x10	2'b10
-	don't care

 

```

fsm = {fsm_newspaper, fsm_NEXT_STATE};

```

```


end

```

```

endfunction

```

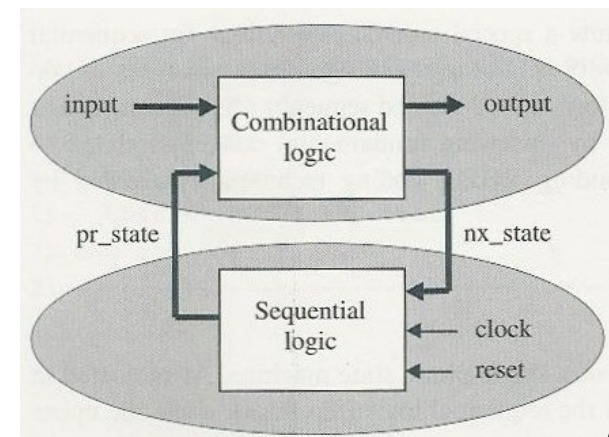

# FSM Example: Vendor Machine (7/7)

store next state

(sequential logic in lower FSM)

```
// reevaluate combinational logic each time a coin is put or  
// the present state changes  
assign {newspaper, NEXT_STATE} = fsm(coin, PRES_STATE);
```

```
// clock the state FFs using synchronous reset
```

```
always @(posedge clock)
```

```
begin
```

```
    if (reset == 1'b)
```


```
        PRES_STATE <= s0;
```

```
    else
```

```
        PRES_STATE <= NEXT_STATE;
```

```
end
```

```
endmodule
```

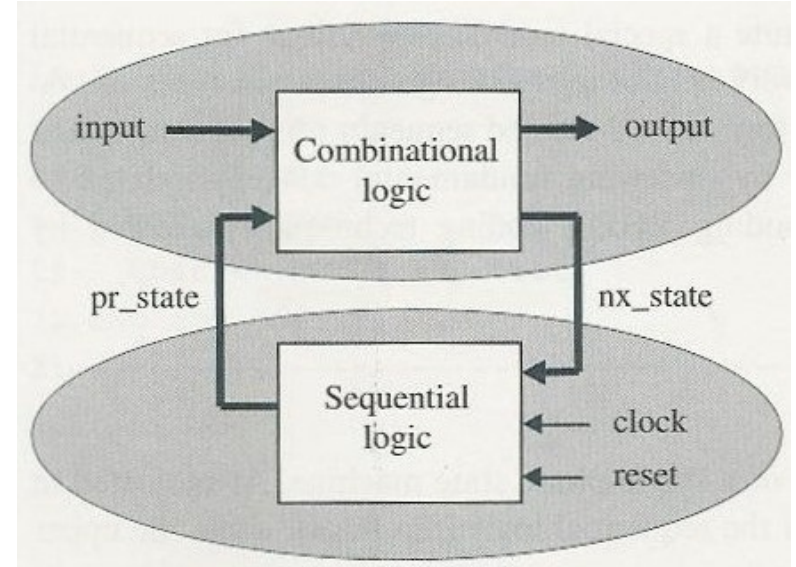

# Stimulus for the FSM Vendor Machine

```
module stimulus;  
reg clock, reset  
reg [1:0] coin;  
wire newspaper;  
vend vendY(coin, clkok, reset,  
    newspaper);  
always  
#20 clkok = ~clock;  
  
initial  
begin  
clock = 0;  
coin = 0;  
reset = 1;  
#50 reset = 0;  
@(negedge clock);
```

```
// put 3 nickles  
#80 coin=1; #40 coin=0;  
#80 coin=1; #40 coin=0;  
#80 coin=1; #40 coin=0;  
// put 1 nickle and 1 dime  
#180 coin=1; #40 coin=0;  
#80 coint=2; #40 coin=0;  
// put 2 dimes  
#180 coin=2; #40 coin=0;  
#80 coint=2; #40 coin=0;  
// put 1 dime and 1 nickle  
#180 coin=2; #40 coin=0;  
#80 coint=1; #40 coint=0;  
  
#80 $finish;  
end  
endmodule
```



# Divide-by-3 counter using FSM


```
module divideby3FSM (input clk, input reset, output y);  
  reg [1:0] state, nextstate;  
  parameter S0 = 2'b00; //binary encoding  
  parameter S1 = 2'b01;  
  parameter S2 = 2'b10;
```

```
  // state register  
  always @(posedge clk, posedge reset)  
    if (reset) state <= S0;  
    else      state <= nextstate;
```

```
  // next state logic  
  always @ (*)  
    case (state)  
      S0:  nextstate = S1;  
      S1:  nextstate = S2;  
      S2:  nextstate = S0;  
      default: nextstate = S0;  
    endcase
```

```
  // output logic  
  assign y = (state == S0); // duty cycle = 1/3 = 33%)
```

```
endmodule
```

 

# divide-by-5 clock with ~1/2 duty cycle

- count the accumulated number of clk edges
  - $\text{clk\_ou}=1$  if  $\text{count} = 5/2 = 2$ ,
  - reset count and  $\text{clk\_out}$  if  $\text{count} = M = 5$
- wo methods

```
// M=5
reg clk_out;
reg [3:0] counter;
always @ (posedge clk) begin
    counter <= counter+1;
    if (counter == M/2)
        clk_out <= 1;
    else if (counter == M) begin
        clk_out <= 0;
        counter <= 0; end
end
end
```

```
always @ (posedge clk)
    state <= next+state;

always @ (*) begin
    case state
    s0: begin next_state = s1; clk_out =0; end
    s1: begin next_state = s2; clk_out =0; end
    s2: begin next_state = s3; clk_out =1; end
    s3: begin next_state = s4; clk_out =1; end
    s4: begin next_state = s0; clk_out =1; end
    endcase
end
```

# Shift Registers

```
x[0] <= d
x[1] <= x[0]
x[2] <= x[1]
...
x[N-2] <= x[N-3]
out <= x[N-2]
```

```
// a total of N shift registers, each bw bits
reg [bw-1:0] x[0:N-2];
reg [bw-1:0] d, out;
always @ (posedge clk) begin
    x[0] <= d;
    for (i=1; i<=N-2; i=i+1)
        x[i] <= x[i-1];
    out <= x[N-2];
end
```

```
// a total of N shift registers
reg [bw-1:0] x[0:N-2];
reg [bw-1:0] d, out;
always @ (posedge clk) begin
    {x[0:N-2], out} <= {d, x[0:N-2]};
end
```

# shift register with parallel load

```
module shiftreg #(parameter N=32)
(input clk, reset, load, si,
input [0:N-1] d,
output [0:N-1] q,
output so);

always @(posedge clk)

if (reset) q <= 0;
else if (load) q <= d;
else {q, so} <= {si, q};

endmodule
```

# left/right/load shift register

```

module LRL_Shift_Register(clk, rst, left,
right, load, sin, in, out) ;
  parameter n = 4 ;
  input clk, rst, left, right, load, sin ;
  input [n-1:0] in ;
  output [n-1:0] out ;
  reg [n-1:0] next ;

```

```


  DFF #(n) cnt(clk, next, out) ;
  // always @ (posedge clk) out <= next;

```

```


  always @(*) begin
    casex({rst,left,right,load})
      4'b1xxx: next = 0 ;           // reset
      4'b01xx: next = {out[n-2:0],sin} ; // left
      4'b001x: next = {sin,out[n-1:1]} ; // right
      4'b0001: next = in ;         // load
      default: next = out ;        // hold
    endcase
  end
endmodule

```

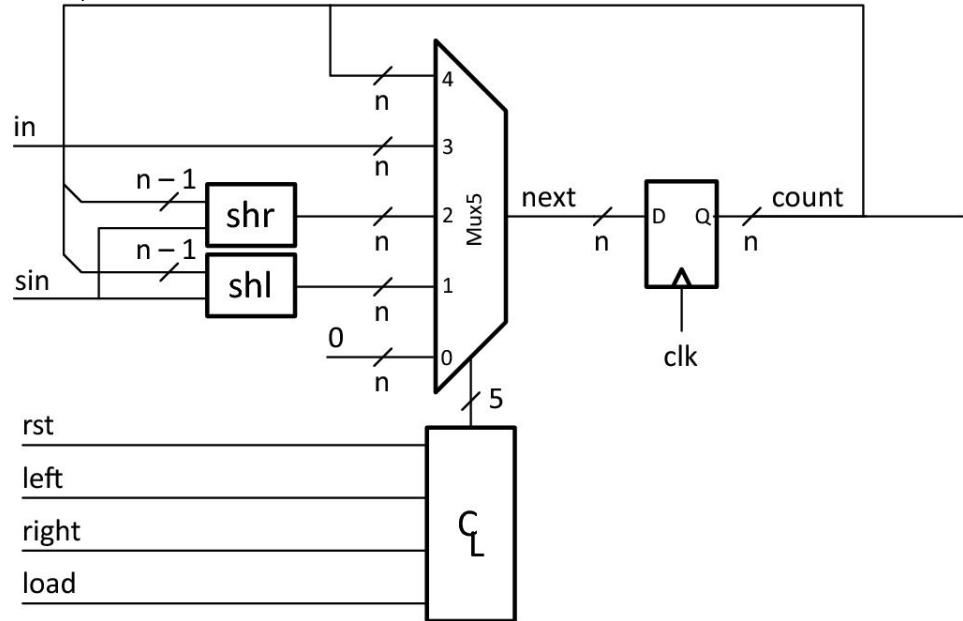
 
# FIR (Finite Impulse Response) Filter

- combinational logic of  $y=y+1$  has the path from output to input, creating a feedback loop !



**// wrong codes,  
// Why?**

```
...
reg [word_size_in-1:0] x[0:M];
reg [word_size_out-1:0] y;
```

```
y=0;
always @(x)
  for (i=0; i<=M-1; i++)
    y = y + x[i]*b[i];
```

...

...

```
parameter bw=8, bw_out=16;
reg [bw-1:0] x[0:M-1]. b[0:M-1];
reg [bw_out-1:0] temp[0:M];
reg [bw_out-1:0] y;
```

```
always @(posedge clk)
  x [0:M-1] <= {in, x[0:M-2]};
```

```
temp[0]=0;
always @(x)
  for (i=0; i<=M-1; i++)
    temp[i+1] = temp[i] + x[i]*b[i];
  assign y = temp[M];
```

...

# Quiz

- how about one-hot state encoding?
  - parameter  $S0 = 3'b001$
  - parameter  $S1 = 3'b010$
  - parameter  $S2 = 3'b100$
  - cp. binary state encoding
- how to design divide-by-5 counter with duty cycle=  $1/5=20\%$  ?
- how to design divide-by-5 counter with duty cycle  $\sim 50\%$  (e.g.  $3/5$ ) ?

# **Memory (ROM, RAM)**




# RAM vs. Registers

- Registers

- use array to model registers
- e.g., reg [31:0] R [0:15];
  - ✓ register file with 16 registers, each with 32 bits
  - ✓ realized using 16\*32 FFs
- many register locations can be accessed simultaneously
  - ✓ e.g.,  $R[3] = R[0] + R[1] + R[2]$ ;
- much more area than RAM


- RAM

 - need memory compiler tool to generate RAM
- only the specified address can be accessed at a time
- much smaller area than registers




24 transistors in a flip-flop

## 6 transistors in a sram cell

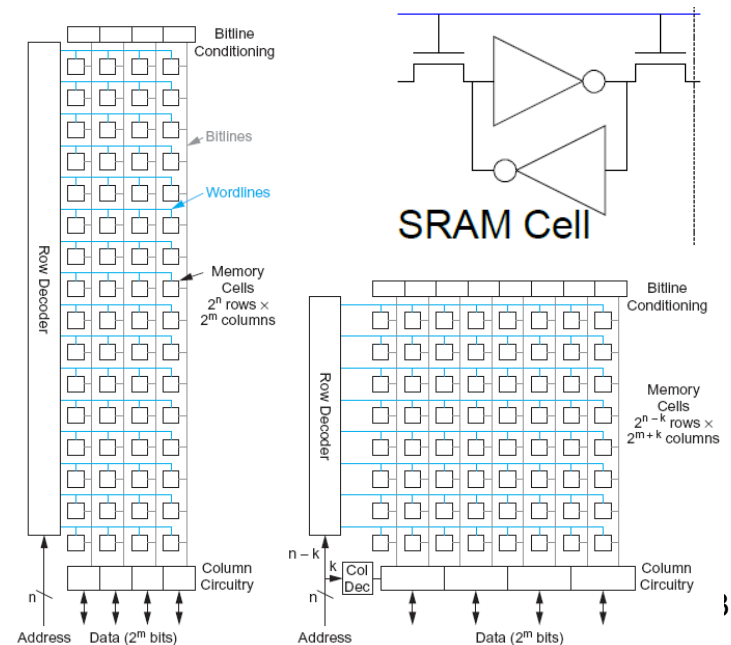


# ROM vs. Random Logic

- Use **case** LookUp Table \*LUT) to specify ROM
  - synthesized with random logic (such as Sum-of-Product Boolean equations)
- Use ROM compiler tool to implement ROM

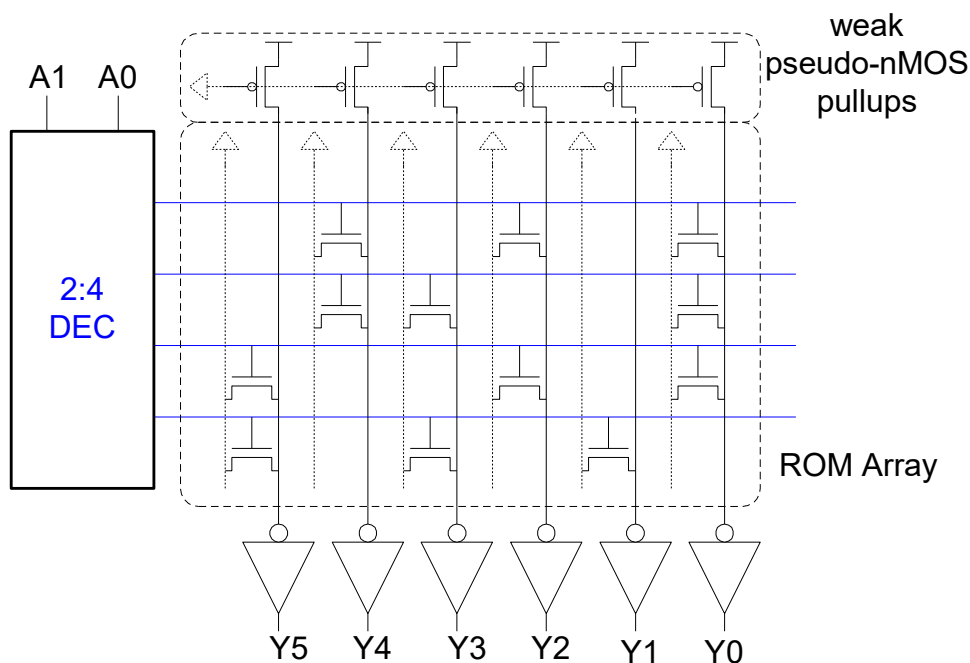

Word 0:	010101
Word 1:	011001
Word 2:	100101
Word 3:	101010

 

# Synthesis of ROM, RAM

- use synthesis pragma and attribute
  - (\* synthesis, rom\_block = "ROMCELLXYZ01" \*)
  - (\* synthesis, ram\_block \*)
  - without synthesis attributes, ROM is usually synthesized into combinational random logic, and synchronous RAM is usually synthesized into flip-flops
    - ✓ much larger area
- declare as 1-D array (e.g., bit-vector) for address and for memory cell
  - specify s ROM contents using case ... endcase
- declare as 2-D array
  - specify ROM content using either of the following two ways
    - ✓ initial begin .... end
    - ✓ read from inputfiles

# Synthesis of ROM/RAM

- If synthesis tool supports *pragmas* to control the structure of the synthesized netlist or to give direction to the synthesis tool, ***synthesis attributes*** shall be used
  - The first attribute within the attribute instance shall be *synthesis* followed by a comma separated list of synthesis-related attributes.

```
(* synthesis, <attribute=value_or_optional_value>
    { , <attribute=value_or_optional_value> } *)

(* synthesis, async_set_reset ["signal_name1, signal_name2, ..."] *)
(* synthesis, black_box      [ =<optional_value> ] *)
(* synthesis, combinational  [ =<optional_value> ] *)
(* synthesis, fsm_state      [ =<encoding_scheme> ] *)
(* synthesis, full_case      [ = <optional_value> ] *)
(* synthesis, implementation = "<value>" *)
(* synthesis, keep           [ =<optional_value> ] *)
(* synthesis, label          = "name" *)
(* synthesis, logic_block    [ = <optional_value> ] *)
(* synthesis, op_sharing     [ = <optional_value> ] *)
(* synthesis, parallel_case  [ = <optional_value> ] *)
(* synthesis, ram_block      [ = <optional_value> ] *)
(* synthesis, rom_block      [ = <optional_value> ] *)
(* synthesis, sync_set_reset ["signal_name1, signal_name2, ..."] *)
(* synthesis, probe_port     [ = <optional_value> ] *)
```

```

module rom_case (a, d) ;
  input [3:0] a;
  output [7:0] d;
  reg [7:0] d;
  always@(*)
  begin
    case(a)
      4'h0: d=8'h00;
      4'h1: d=8'h11;
      4'h2: d=8'h22;
      4'h3: d=8'h33;
      4'h4: d=8'h44;
      4'h5: d=8'h12;
      4'h6: d=8'h34;
      4'h7: d=8'h56;
      4'h8: d=8'h78;
      4'h9: d=8'h9a;
      4'ha: d=8'hbc;
      4'hb: d=8'hde;
      4'hc: d=8'hf0;
      4'hd: d=8'h12;
      4'he: d=8'h34;
      4'hf: d=8'h56;
      default: d=8'h0;
    endcase
  end
endmodule

```

# Two Implementations of ROM

## (using case, or using input text file)

```

module rom_reg (a, d) ;
  parameter b = 8;
  parameter w = 4;
  parameter fileName = "datafile";
  input [w-1:0] a;
  output [b-1:0] d;
  reg [b-1:0] memory [2**w-1:0] ;
  initial
  begin
    $readmemb (fileName, memory);
  end
  assign d = memory[a];
endmodule

```

```

// content of file "datafile"
// address in hexadecimal
@002
11111111 01010101
00000000 10101010
@006
1111zzzz 00001111
...

```

```

memory[0]=xxxxxxx
memory[1]=xxxxxxx
memory[2]=11111111
memory[3]=01010101
memory[4]=00000000
memory[5]=10101010
memory[6]=1111zzzz
memory[7]=00001111
...

```

# ROM

- Three types of ROM models
  - one-dimensional array with data in case statement
  - two-dimensional array with data in initial statement
  - two-dimensional array with data in text file

# ROM: 1D array using **case**

- Synthesis attribute **rom\_block** model ROM
- Attribute **logic\_block** implies combinational logic

```
module rom_case(  
    (* synthesis, rom_block = "ROM_CELLXYZ01" *)  
    output reg [3:0] z,  
    input wire [2:0] a); // Address - 8 deep memory.  
  
    always @*          // @(a)  
        case (a)  
            3'b000: z = 4'b1011;  
            3'b001: z = 4'b0001;  
            3'b100: z = 4'b0011;  
            3'b110: z = 4'b0010;  
            3'b111: z = 4'b1110;  
            default: z = 4'b0000;  
        endcase  
endmodule // rom_case  
// z is the ROM, and its address size is determined by a.
```

# ROM: 2D array using **initial**


- initial statement shall be supported when synthesis attributes **logic\_block** or **rom\_block** is used
- without specifying attributes, a synthesis tool may opt to implement either as random combintional logic or as a ROM

```
module rom_2dimarray_initial (  
    output wire [3:0] z,  
    input wire [2:0] a); // address- 8 deep memory  
// Declare a memory rom of 8 4-bit registers. The indices are 0 to 7:  
(* synthesis, rom_block = "ROM_CELL XYZ01" *) reg [3:0] rom[0:7];  
// (* synthesis, logic_block *) reg [3:0] rom [0:7];
```

```
initial begin  
    rom[0] = 4'b1011;  
    rom[1] = 4'b0001;  
    rom[2] = 4'b0011;  
    rom[3] = 4'b0010;  
    rom[4] = 4'b1110;  
    rom[5] = 4'b0111;  
    rom[6] = 4'b0101;  
    rom[7] = 4'b0100;
```

```
end
```
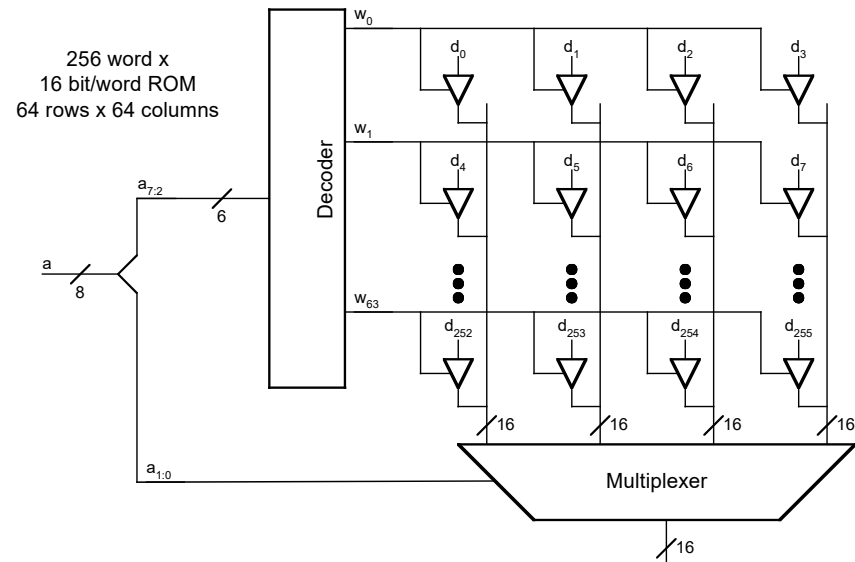
```
    assign Z = rom[a];  
endmodule
```





# ROM: 2D array with data in text file

- use **\$readmemb** to read ROM data from a text file

```
module rom_2dimarray_initial_readmem (  
    output wire [3:0] z,  
    input wire [2:0] a);  
    // Declare a memory rom of 8 4-bit registers.  
    // The indices are 0 to 7:  
    (* synthesis, rom_block = "ROM_CELL XYZ01" *) reg [3:0] rom[0:7];  
  
    initial $readmemb("rom.data", rom);  
  
    assign z = rom[a];  
endmodule
```

```
// Example of content "rom.data" file:  
// file: /user/name/project/design/rom/rom.data  
// date : Jan 08, 02  
1011      // addr=0  
1000      // addr=1  
0000      // addr=2  
1000      // addr=3  
0010      // addr=4  
0101      // addr=5  
1111      // addr=6  
1001      // addr=7
```

**RAM**

# Edge-sensitive RAM

- RAM shall be modeled with synthesis attribute ***ram\_block***
- If latch or register logic is desired instead of a RAM, use the attribute ***logic\_block*** instead of ***ram\_block***
- RAM could be ***edge-*** or ***level-***sensitive
- e.g. *we* (write-enable) control signal is synchronized with clock signal

```
// A RAM element is an edge-sensitive storage element:
module ram_test(
    output wire [7:0] q,
    input wire [7:0] d,
    input wire [6:0] a,
    input wire clk, we);
    (* synthesis, ram_block *) reg [7:0] mem [127:0];

    always @(posedge clk) if (we) mem[a] <= d;

    assign q = mem[a];
endmodule
```

# level-sensitive RAM

- we (write-enable) is the level-sensitive control signal
  - no clock signal is used

```
// A RAM element is a level-sensitive storage element:
module ramlatch (
    output wire [7:0] q, // output
    input  wire [7:0] d, // data input
    input  wire [6:0] a, // address
    input  wire      we); // clock and write enable
// Memory 128 deep, 8 wide:
(* synthesis, ram_block *) reg [7:0] mem [127:0];

always @* if (we) mem[a] <= d;

    assign q = mem[a];
endmodule
```

# dual-port (one-read, one-write) RAM

- check definitions of two-port or dual-port in document
  - 1R/1W, 2R, or 2W, or
  - 1R/1W only

```
module RAM(ra, wa, write, din, dout) ;  
    parameter b = 32;  
    parameter w = 4;  
  
    input [w-1:0] ra, wa;  
    input        write;  
    input [b-1:0] din;  
    output [b-1:0] dout;  
  
    reg [b-1:0]    ram [2**w-1:0];  
  
    assign dout = ram[ra]; // one read port  
  
    always@(*) begin  
        if(write == 1)  
            ram[wa] = din; // one write port  
    end  
endmodule
```

# RAM with bidirectional data bus

```
module ram #(parameter N=6, M=32)
(input clk, we,
input [N-1:0] adr,
inout [M-1:0] data);

reg [M-1:0] mem [2**N-1:0];

always @ (posedge clk)
    if (we) mem[adr] <= data;

assign data = we ? 'z : mem[adr];

endmodule
```

# RAM: 2D array using **always**

- in general, standard cell library vendors or FPGA synthesis tools usually provide automatic generator (compiler) of memory, such as RAM, ROM, register file which are usually custom designs

```
// A RAM element is an edge-sensitive storage element:
module ram_test(
    output wire [7:0] q,
    input wire [7:0] d,
    input wire [6:0] a,
    input wire clk, we);
    (* synthesis, ram_block *) reg [7:0] mem [127:0];

    always @(posedge clk) if (we) mem[a] <= d;

    assign q = mem[a];
endmodule
```

# **ARM TSMC Memory Compiler**




# TSMC 90nm Memory Compiler


- 90nm

TSMC_90nm	Register file	SRAM
Single-port	RF_SP_ADV	SRAM_SP_ADV
Two-port	RF_2P_ADV	-
Dual-port	--	SRAM_DP_ADV


single-port,

 

two-port ,

 


dual-port

 

TSMC_40nm	Register file	SRAM
Single-port	RF_SP_HDE (rvt_hvt_rvt) RF_SP_HSD (rvt_rvt_hvt)	SRAM_SP_HDE (rvt_hvt_rvt) SRAM_SP_HSC (rvt_hvt_rvt)
Two-port	RF_2P_HSE (rvt_hvt_rvt)	-
Dual-port	--	SRAM_DP_HDE (rvt_hvt_rvt)

# TSMC 90nm Single-Port Pins

 

Pin	Description
A[9:0]	Addresses (A[0] = LSB)
D[31:0]	Data Inputs (D[0] = LSB)
CLK	Clock
CEN	Chip Enable (active low)
WEN	Write Enable (active low)
Q[31:0]	Data Outputs (Q[0] = LSB)
EMA[2:0]	Extra Margin Adjustment (EMA[0] = LSB)

# TSMC 40nm Single-Port Pins

- more complicate pins

Pin	Description
<b>CEN</b>	Chipe Enable (active low)
<b>WEN</b>	Write Enable (active low)
<b>A</b>	Addresses(A[0]=LSB)
<b>D</b>	Data Inputs (D[0]=LSB)
<b>Q</b>	Data Outputs (Q[0]=LSB)
<b>CLK</b>	Clock
WENY	Multiplexor out (WEN CEN A D)
CENY	
AY DY	

Pin	Description
EMA	Extra Margin Adjustment
EMAW	
EMAS	
BEN	Bypass mode,active low
TEN (enable)	TEST MODE,active low (CEN WEN A D Q 同前面意思)
TCEN	
TWEN	
TA TD TQ	
RET1N	Retention mode, acitve low
STOV	Synchronous clock enable, acitve low

# TSMC 90nm Memory: Register-File

- register-file-based memory
  - single-port

two-port

**Single-Port 90nm Register File**  
rf\_sp\_adv

Parameter	Ranges	
Numbers of words	Mux=1	8 to 128
	Mux=2	16 to 256
	Mux=4	32 to 512
Numbers of bits	Mux=1	8 to 128
	Mux=2	4 to 128
	Mux=4	2 to 64
Total memory bits	Mux=1	64 to 16,384 bits
	Mux=2, 4	64 to 32,768 bits

**Two-Port 90nm Register File**  
rf\_2p\_adv

Parameter	Ranges	
Numbers of words	Mux=1	8 to 128
	Mux=2	16 to 256
	Mux=4	32 to 512
Numbers of bits	Mux=1	2 to 128
	Mux=2	2 to 64
	Mux=4	2 to 32
Total memory bits	16 to 16,384 bits	

# TSMC 90nm Memory: SRAM

- sram-based memory  
single-port

Single-Port 90nm SRAM sram_sp_adv		
Parameter	Ranges	
Numbers of words	Mux=8	256 to 4096
	Mux=16	512 to 8192
	Mux=32	1024 to 16384
Numbers of bits	Mux=8	2 to 128
	Mux=16	2 to 64
	Mux=32	2 to 32
Total memory bits	512 to 524,288 bits	

dual-port

Dual-Port 90nm SRAM sram_dp_adv		
Parameter	Ranges	
Numbers of words	Mux=4	128 to 2048
	Mux=8	256 to 4096
	Mux=16	512 to 8192
Numbers of bits	Mux=4	2 to 128
	Mux=8	2 to 64
	Mux=16	2 to 32
Total memory bits	256 to 262,144 bits	

# Memory Synthesis

- use memory compiler to generate .lib and .v files
  - select register-file or sram
  - select single-port, two-port, or dual-port
  - specify # of words, # of bits, mux\_width
  - give module name (e.g., sram\_sp\_1024x32)
- add the memory modules into your design
  - first convert .lib into .db file for Synopsys DC synthesis
  - use module instantiation to add memory modules
  - combine with your other RTL codes, e.g., in top.v
- use Synopsys DC to synthesize the entire ckt.
  - synthesized ckt., e.g., in top\_gate.v
- simulate with all .v files