

**Verilog:
overview
structural modeling,
dataflow modeling**


Outlines

- Overview
- Testbench
- System Task, Compiler Directives
- Verilog Operators, Data Types
- Structural-level Modeling
- Modules and Ports
- Dataflow Modeling

Overview

Components of a Verilog Module

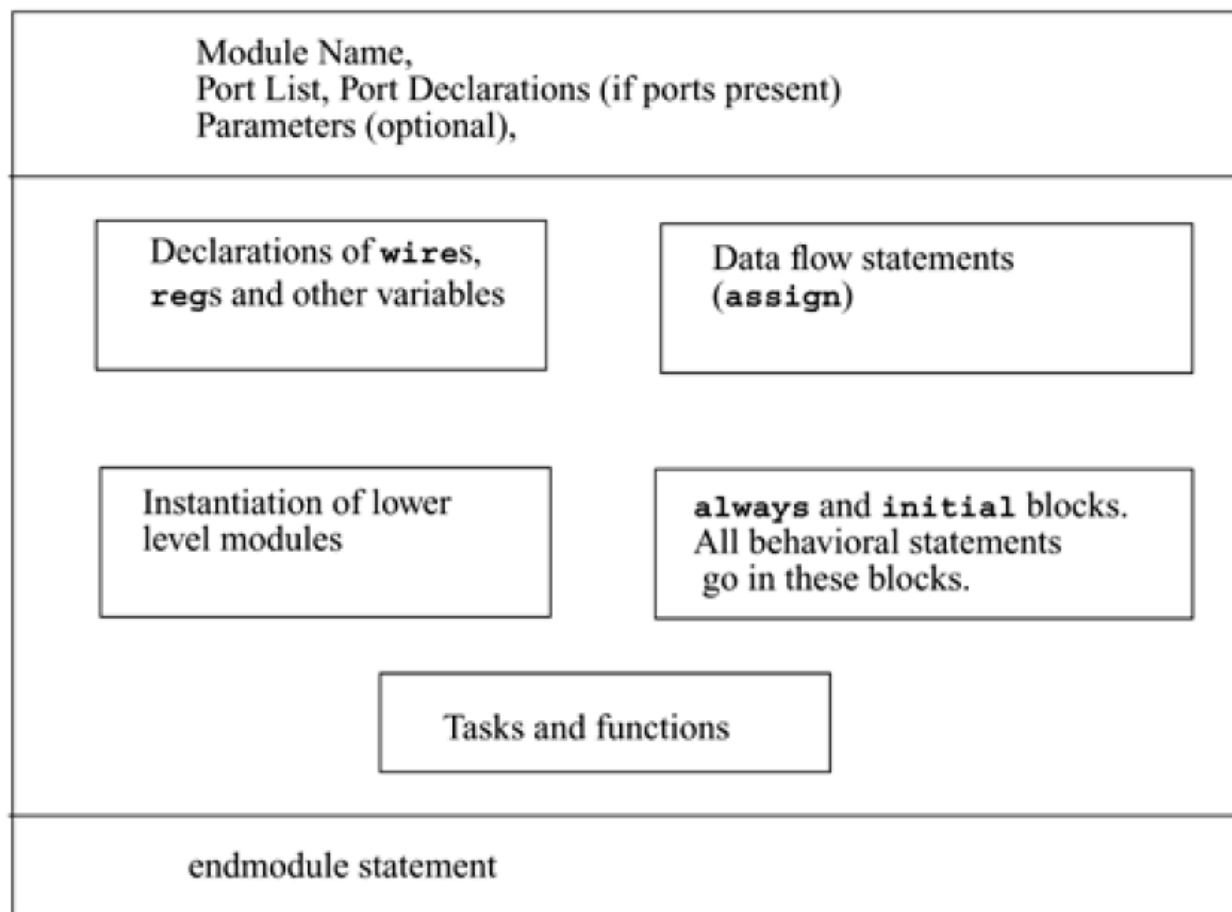- declaration
 - inputs, outputs
 - parameters
 - data types
- **structure** model
- module *instantiation*
- **dataflow** model
 - *continuous assignment*
- **behavior** model
 - *procedural assignment*



```
module M (P1, P2, P3, P4);
input P1, P2;
output [7:0] P3;
inout P4;
```

```
reg [7:0] R1, M1[0:1023];
wire W1, W2, W3, W4;
wire [3:0] W5;
parameter C1=const;
```

```
// non-synthesizable coding
// used in testbench
```

```
initial
begin : blockname
    // statements
end
```

```
// behavioral modeling
always
begin
    // statements
end
```


```
// dataflow: continuous assignment
assign W1 = expr ; // use operators
```

```
// module instances: structural
modeling
```

```
COMP U1 (.PP2(W2), .PP1(W1);
COMP U2 (W3, W4);
```

```
task T1;
input A1, A2;
output A3, A4;
begin
    // statements
end
endtask
```
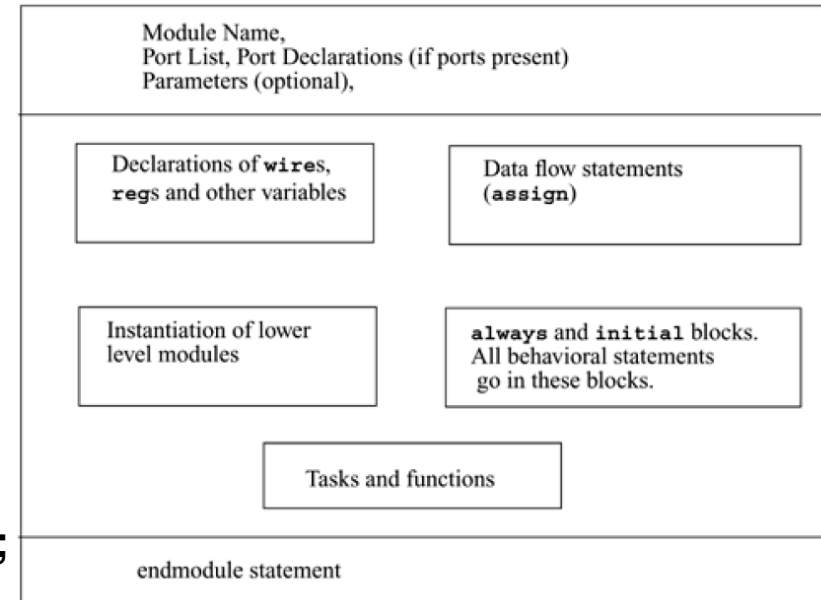
```
function [7:0] F1;
input A1;
begin
    // statements
end
endfunction
```



Parallel Coding in Hardware

- hardware programming is basically parallel coding
 - order of codes does NOT matter
 - e.g., describe two hardware units: adder and multiplier

```
...  
assign c=a+b; // describe adder first  
assign out=c*d; // then describe multiplier  
...
```

```
...  
assign out=c*d; // describe multiplier  
assign c=a+b; // then describe adder  
...
```

- software programming is usually sequential
 - order of codes matters

```
...  
c=a+b;  
out=c*d; // out = (a+b) *d  
...
```

```
...  
out=c*d; // out = old_c *d  
c=a+b; // new_c = a+b  
...
```

Combinational VS. Sequential Logic

- Combinational Logic

- Logic circuits with pure *feed-forward* datapath
- No flip flops or latches
- e.g.

```
module adder (input wire [7:0], a, b, output wire [7:0] c);  
  assign c = a + b; // dataflow modeling  
endmodule
```

- Sequential Logic

- Logic circuits with latches or flip-flop storage elements
- e.g.

```
module lateched (input [7:0], a, b, input clk, output reg [7:0] c);  
  always @ (poedge clk) // behavioral modeling  
    c = a + b; // result c stored in a positive-edge-riggered register  
endmodule
```

module definition

- declaration of I/O port and datatype could be merged with module declaration in the first line, e.g.,

```
module myCPU (
    input Reset, Clock,
    input [31:0] Address,
    inout [31:0] Data,
    output R_Wb );

    .
    .
    .
    .
    .
    .
endmodule
```

`module MyCPU(R_Wb, Data, Address, Clock, Reset);`
`input Reset, Clock;`
`input [31:0] Address;`
`inout [31:0] Data;`
`output R_Wb;`

} I/O port declarations

.
.
.

} Resource / variable declarations

.
.
.

} Structural / behavioral modeling


`endmodule`

module


- define a hardware component and its input/output ports

```
module sillyfunction(input a, b, c,  
                    output y);  
  
    assign y = ~a & ~b & ~c |  
              a & ~b & ~c |  
              a & ~b & c;  
  
endmodule
```

- simulation

 

- synthesis results

 


32-bit adder

- dataflow modeling (**assign** ...)
 - real adder hardware circuit implementation depends on synthesis constraints (delay, area, power)
 - ripple carry adder (slow but smaller), or
 - carry lookahead adder (fast but larger)

SystemVerilog

```
module adder(input  logic [31:0] a,  
             input  logic [31:0] b,  
             output logic [31:0] y);  
  
    assign y = a + b;  
endmodule
```

 logic in SystemVerilog corresponds to **wire** (default) , **reg** in Verilog




4:1 multiplexer

- *structure* of hardware is described
- Construct lower layer components (mux2) into higher ones (mux4)

```
module mux4 (input  [3:0] d0, d1, d2, d3,
              input  [1:0] s,
              output [3:0] y);

  wire [3:0] low, high;

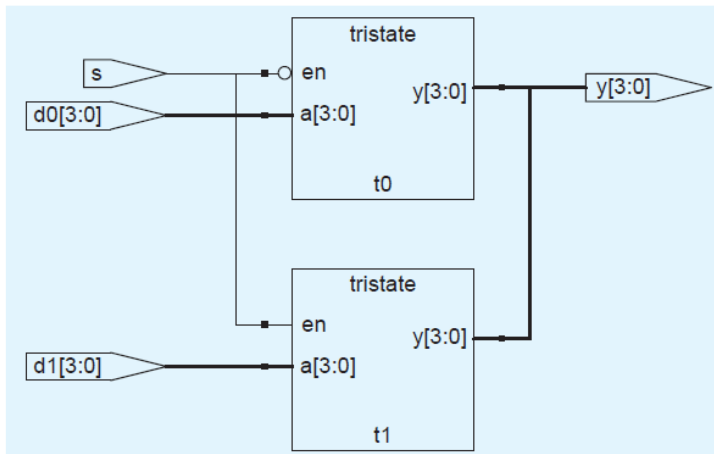  mux2 lowmux (d0, d1, s[0], low);
  mux2 highmux (d2, d3, s[0], high);
  mux2 finalmux (low, high, s[1], y);
endmodule
```




mux2 is composed of two tri-state buffers

// built-in tri-state inverters or buffers
notif1, notif0, bufif1, bufif0

```
module mux2 (input  [3:0] d0, d1,
              input      s,
              output [3:0] y);

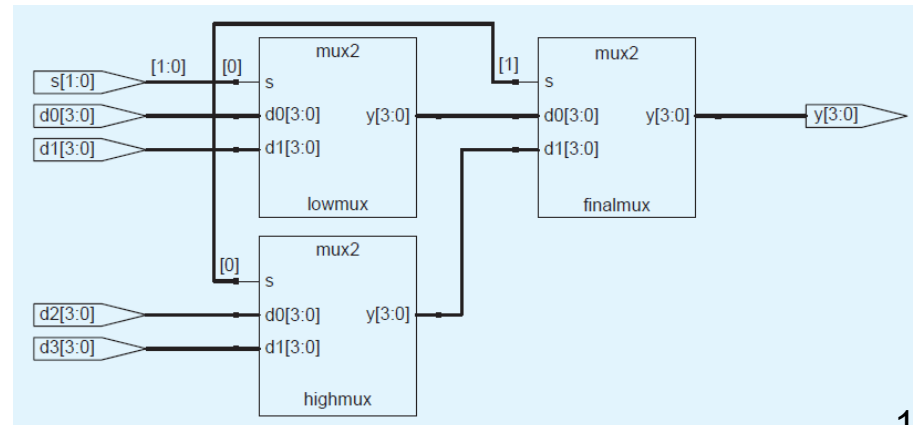  tristate t0 (d0, ~s, y);
  tristate t1 (d1, s, y);
endmodule
```



other modeling methods for mux4

```
// dataflow using
// nested
// conditional
// operator
...
assign y = s[1] ?
(s[0] ? d3 : d2) :
(s[0] ? d1 : d0);
...
```

```
// behavior using case
...
always @ (d0, d1, d2, d3, s)
begin
case (s[1], s[0])
    2'b00: y=d0;
    2'b01: y=d1;
    2'b10: y=d2;
    2'b11: y=d3;
endcase
end
...
```

```
// behavior using if else
...
always @ (*)
begin
if (s=2'b00) y=d0;
    else if (s=2'b01) y=d1;
    else if (s=2'b10) y=d2;
    else y=d3);
...
```

half adder (HA)

a	b	sum	cout
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$sum = a \oplus b$$

$$cout = ab$$

// structural description

module HA (a, b, sum, cout);

input a, b;

output sum, cout;

// use built-in gates

xor X1(sum, a, b);

and a1(cout, a, b);

endmodule

// dataflow

module halfadder (a,b,sum,cout);

input a, b;

output sum; cout;

assign s = a ^ b ; // ^ is XOR operator

assign c = a & b; // & is AND operator

// **assign** {c, s} = a + b;

endmodule

// behavior

module halfadder (a,b,sum,cout);

input a, b;

output reg sum; cout;

always @ (a, b)

{cout, sum} = a + b;

endmodule

8-b Adder

- declare signal as bit-vector
 - e.g., **wire** [7:0] s; // 8-bit signal s
 - most significant bit (MSB) is s[7]
 - least significant bit (LSB) is s[0]

```
module add8 (A, B, S, Co);  
input [7:0] A; // declare a signal as a multi-bit vector  
input [7:0] B;  
output [7:0] S;  
output Co;  
  
assign {Co, S} = A + B;  
  
endmodule
```

Latch



- Use “**always**” block to describe latch
 - pass input to output when control signal is active
 - keep the previous output value when control signal is in-active

```

module latch (D, G, Q, QN);
  input wire D, G;
  output reg Q, QN;

  always @ ( D or G )
  begin
    if (G)
      begin
        Q <= D;
        QN <= ~D;
      end
    end
  endmodule
    
```

G	D	Q[n+1]	QN[n+1]
1	0	0	1
1	1	1	0
0	x	Q[n]	QN[n]

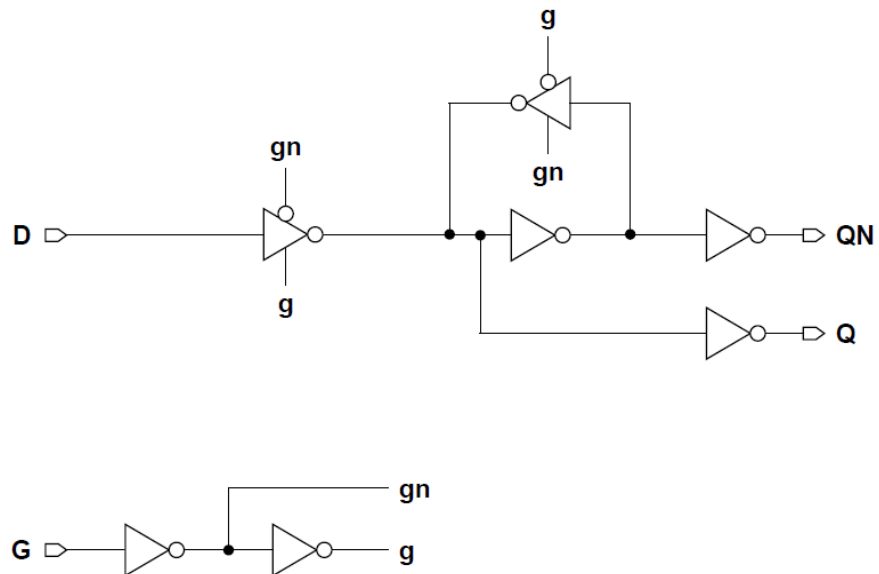 




Flip-Flop (FF)



- Use “always” block to describe flip-flop (FF)
 - pass the input to output at the time instance of clock edge
 - keep the previous output values at other time
 - usually consists of two back-to-back latches

```

module flip_flop (D, CK, Q,QN);
  input wire D, CK;
  output reg Q, QN;


  always @ ( posedge CK )
  begin
    Q <= D;
    QN <= ~D;
  end
endmodule
    
```

 D	CK	Q[n+1]	QN[n+1]
0		0	1
1		1	0
x		Q[n]	QN[n]

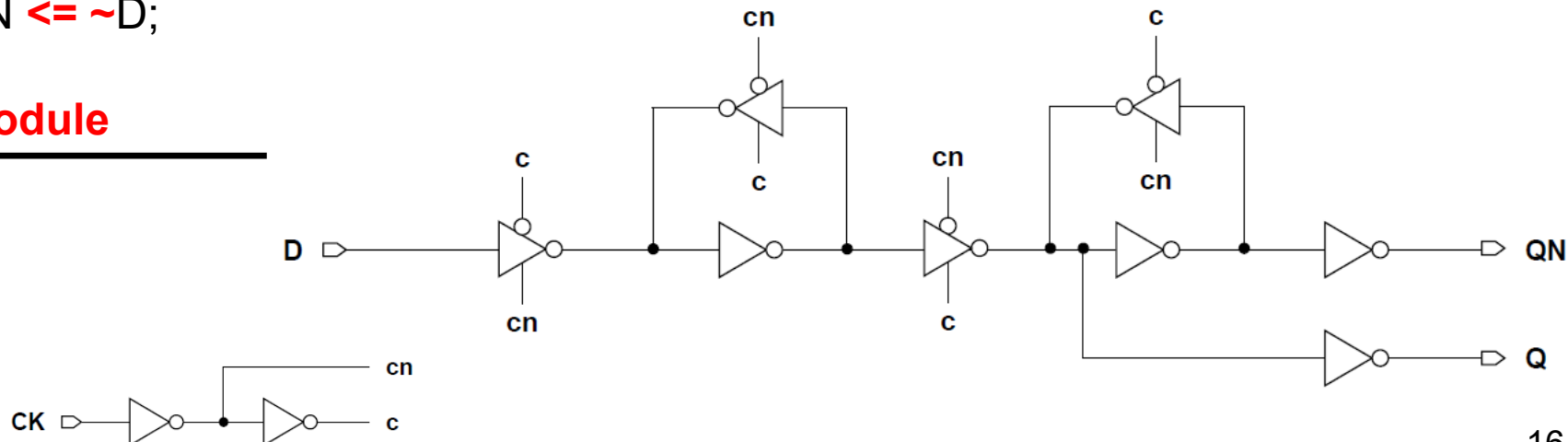 

register (multiple-bit flip-flops)
 
```
module flop (input          clk,  
             input    [3:0] d,  
             output reg [3:0] q);  
  
    always @ (posedge clk)  
        q <= d;  
endmodule
```



resettable register

```
module flopr (input          clk,
              input          reset,
              input  [3:0] d,
              output reg [3:0] q);

// asynchronous reset
always @ (posedge clk, posedge reset)
    if (reset) q <= 4'b0;
    else      q <= d;
endmodule
```

```
module flopr (input          clk,
              input          reset,
              input  [3:0] d,
              output reg [3:0] q);
```

```
// synchronous reset
always @ (posedge clk)
    if (reset) q <= 4'b0;
    else      q <= d;
endmodule
```

// asynchronous reset FF


...

always @ (posedge clk
or positive reset)

if (reset) q <= 4'd0;

else q <= d;

...

 

Finite State Machine (FSM):

divide-by-3 counter

(3 times period, or 1/3 frequency)

SystemVerilog

```
module divideby3FSM(input  logic clk,  
                   input  logic reset,  
                   output logic y);
```

```
    logic [1:0] state, nextstate;
```

```
    // State Register
```

```
    always_ff @(posedge clk)
```

```
        if (reset) state <= 2'b00;
```

```
        else      state <= nextstate;
```

```
    // Next State Logic
```

```
    always_comb
```

```
        case (state)
```


```
            2'b00: nextstate = 2'b01;
```

```
            2'b01: nextstate = 2'b10;
```

```
            2'b10: nextstate = 2'b00;
```

```
            default: nextstate = 2'b00;
```

```
        endcase
```

 

```
    // Output Logic
```


```
        assign y = (state == 2'b00);
```

```
endmodule
```

Testbench

simulation and testbench

- verify the hardware design
- simulation block (also called **testbench**, or **test fixture**)
 - instantiates design block, i.e., the hardware under test
 - apply stimulus (test patterns or test vectors)
 - observe/compare the output with expected results
- design block must be in **synthesizable** HDL codes
- simulation block could be in **non-synthesizable** HDL codes
- testbench consists 4 parts
 - instantiate hardware design
 - prepare inputs and expected outputs
 - ✓ inside testbench, or read files from outside
 - assign inputs to the hardware
 - compare outputs with expected
 - ✓ inside testbench, or write files to outside

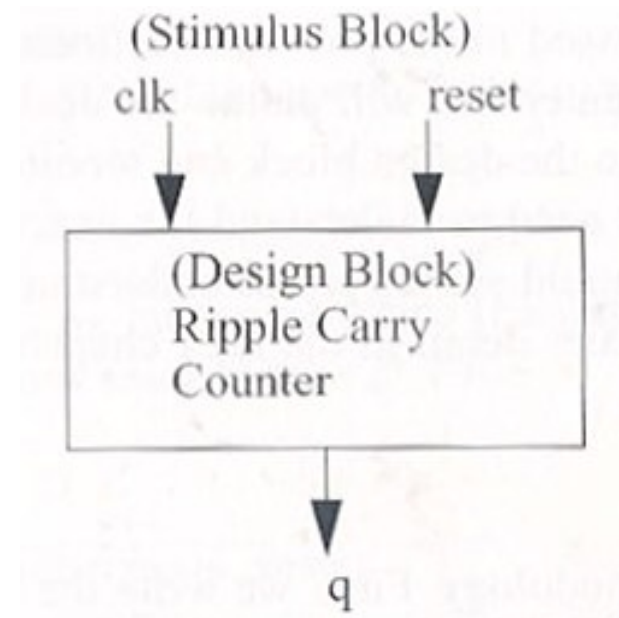

Testbench example (manually specified inputs)

- Not synthesizable statements are OK

```
module testbench1();  
  reg a, b, c;  
  wire y;  
  // instantiate device under test  
  sillyfunction dut (a, b, c, y);  
  // apply inputs one at a time  
  initial begin  
    a = 0; b = 0; c = 0; #10;  
    c = 1; #10;  
    b = 1; c = 0; #10;  
    c = 1; #10;  
    a = 1; b = 0; c = 0; #10;  
    c = 1; #10;  
    b = 1; c = 0; #10;  
    c = 1; #10;  
  end  
endmodule
```


```
module sillyfunction(input a, b, c,  
                    output y);  
  
  assign y = ~a & ~b & ~c |  
             a & ~b & ~c |  
             a & ~b & c;  
  
endmodule
```

Testbench examples

Verilog

```
module sillyfunction(input a, b, c,
                    output y);

    assign y = ~a & ~b & ~c |
               a & ~b & ~c |
               a & ~b & c;
```

 

Verilog

```
module testbench2();
    reg a, b, c;
    wire y;

    // instantiate device under test
    sillyfunction dut(a, b, c, y);

    // apply inputs one at a time
    // checking results
    initial begin
        a = 0; b = 0; c = 0; #10;
        if (y != 1) $display("000 failed.");
        c = 1; #10;
        if (y != 0) $display("001 failed.");
        b = 1; c = 0; #10;
        if (y != 0) $display("010 failed.");
        c = 1; #10;
        if (y != 0) $display("011 failed.");
        a = 1; b = 0; c = 0; #10;
        if (y != 1) $display("100 failed.");
        c = 1; #10;
        if (y != 1) $display("101 failed.");
        b = 1; c = 0; #10;
        if (y != 0) $display("110 failed.");
        c = 1; #10;
        if (y != 0) $display("111 failed.");
    end
endmodule
```

Verilog

```
module testbench3();
    reg      clk, reset;
    reg      a, b, c, yexpected;
    wire      y;
    reg [31:0] vectornum, errors;
    reg [3:0] testvectors [10000:0];

    // instantiate device under test
    sillyfunction dut(a, b, c, y);

    // generate clock
    always
    begin
        clk = 1; #5; clk = 0; #5;
    end

    // at start of test, load vectors
    // and pulse reset
    initial
    begin
        $readmemb("example.tv", testvectors);
        vectornum = 0; errors = 0;
        reset = 1; #27; reset = 0;
    end

    // apply test vectors on rising edge of clk
    always @ (posedge clk)
    begin
        #1; {a, b, c, yexpected} =
            testvectors[vectornum];
    end

    // check results on falling edge of clk
    always @ (negedge clk)
    if (~reset) begin // skip during reset
        if (y != yexpected) begin

            $display ("Error: inputs = %b", {a, b, c});
            $display (" outputs = %b (%b expected)",
                y, yexpected);
            errors = errors + 1;
        end
        vectornum = vectornum + 1;
        if (testvectors[vectornum] == 4'bxx) begin
            $display ("%d tests completed with %d errors",
                vectornum, errors);
            $finish;
        end
    end
endmodule
```

```
000_1
001_0
010_0
011_0
100_1
101_1
110_0
111_0
```

Self- checking Testbench

**need to know the
expected correct outputs
for comparison with
the real hardware outputs**

```
module testbench2();  
  reg a, b, c;  
  wire y;  
  // instantiate device under test  
  sillyfunction dut(a, b, c, y);  
  // apply inputs one at a time  
  // checking results  
  initial begin  
    a = 0; b = 0; c = 0; #10;  
    if (y !== 1) $display("000 failed.");  
    c = 1; #10;  
    if (y !== 0) $display("001 failed.");  
    b = 1; c = 0; #10;  
    if (y !== 0) $display("010 failed.");  
    c = 1; #10;  
    if (y !== 0) $display("011 failed.");  
    a = 1; b = 0; c = 0; #10;  
    if (y !== 1) $display("100 failed.");  
    c = 1; #10;  
    if (y !== 1) $display("101 failed.");  
    b = 1; c = 0; #10;  
    if (y !== 0) $display("110 failed.");  
    c = 1; #10;  
    if (y !== 0) $display("111 failed.");  
  end  
endmodule
```


Testbench with Testvectors from files

- prepare testvectors file which could be from other Verilog codes or other high-level language like C
- Testbench:
 1. Instantiate Design (with specified inputs and outputs),
Generate clock
 2. Read testvectors file (including inputs and expected outputs)
 3. Assign inputs
 4. Compare outputs with expected

Testbench: 1.

Instantiate Design, Generate Clock

```
module testbench3();  
    reg      clk, reset;  
    reg      a, b, c, yexpected;  
    wire     y;  
    reg [31:0] vectornum, errors;  
    reg [3:0] testvectors[10000:0];  
  
    // instantiate device under test  
    sillyfunction dut (a, b, c, y);  
  
    // generate clock  
    always  
        begin  
            clk = 1; #5; clk = 0; #5;  
        end
```

```
module sillyfunction(input a, b, c,  
                    output y);  
  
    assign y = ~a & ~b & ~c |  
              a & ~b & ~c |  
              a & ~b &  c;  
  
endmodule
```

2. Read Testvectors

```
// at start of test, load vectors  
// and pulse reset
```

initial

begin

// system task \$readmemb reads binary data from file

\$readmemb ("example.tv", testvectors);

vectornum = 0; errors = 0;

reset = 1; #27; reset = 0;

end

```
// testvector  
// fine namej  
// example.tv
```

000_1

001_0

010_0

011_0

100_1

101_1

110_0

111_0

3. Assign Inputs

```
// apply inputs from test vectors on rising edge of clk
// device under test is the instantiated    sillyfunction dut (a, b, c, y);

always @(posedge clk)
begin
    #1; {a, b, c, yexpected} = testvectors[vectornum];
    // assign inputs a, b, c; get output y from sillyfunction dut (a, b, c, y);

end
```

4. Compare Outputs with Expected

```
// check results on falling edge of clk
always @(negedge clk) begin
  if (~reset) begin // skip during reset
    if (y !== yexpected) begin
      $display("Error: inputs = %b",
        {a, b, c});
      $display(" outputs = %b (%b expected)",
        y, yexpected);
      errors = errors + 1;
    end
    vectornum = vectornum + 1;
    if (testvectors[vectornum] === 4'bx) begin
      $display("%d tests completed with %d errors",
        vectornum, errors);
    finish;
  end
end // end of always @ (posedge clk)
endmodule
```

Test Patterns

- access files for inputs and expected outputs
 - \$fscanf, \$readmemb, \$fdisplay, ...
 - need other programs (e.g., C, Python) to generate the input files of test patterns
 - need other programs to compare the simulation results in the output file
 - the previous example read test patterns and expected results from a file, and make comparison in the testbench
- generate inputs in testbench module
 - randomly generate input test patterns (e.g., \$random, ...)
 - could use non-synthesizable codes to generate expected results (e.g., real x, y, z ' assign z=x+y; // floating-pt. add)
 - compare simulation results with expected ones

Another Example

- fixed-point signed adder
- instantiate hardware module
 - connection-by-name I/O pins
- testbench (next slide)
 - read input test patterns from files, or randomly generate inputs in testbench
 - generate expected results in testbench
 - make comparison in testbench

```
module FXP_adder (input signed [31:0] a, b, output signed [31:0] d);  
  
assign d = a + b;  
  
endmodule
```

```

... // instantiate hardware
FXP_adder test_module ( .a(input_a), .b(input_b), .d(outcome));
... // read test patterns from files
file_a = $fopen( "a.txt" , "r");
file_b = $fopen( "b.txt" , "r");
file_d = $fopen("c.txt" , "w");
for (i = 0; i < 100; i=i+1) begin ...
    garbage = $fscanf(file_a, "%X", data_a[i]); // hexa-decimal format
    garbage = $fscanf(file_b, "%X", data_b[i]); ... end
... // compute expected answer, get hardware outputs and write to a file
for (i=0; i< 100; i=i+1) begin ...
    input_a = data_a[i]; // apply test patterns to hardware inputs
    input_b = data_b[i];
    answer = $signed(input_a) + $signed(input_b); // expected results
    if (output != answer) .... // error occurs
    $fwrite(file_d, "%X\n", outcome); ... end
... // an alternative of generating input test patterns randomly
for (i=0; i< 100; i=i+1) begin ...
    input_a = $random % (2**31); // between -2^31 + 1 and 2^31 - 1
    input_b = $random % (2**31);
    answer = $signed(input_a) + $signed(input_b); ... end

```


System Task \$

- read from input
 - \$readmemb, \$readmemh
 - \$fscanf, \$fgetc. \$fread
- write to output
 - \$fopen, \$fclose
 - \$display, \$strobe, \$monitor, \$write
 - \$fdisplay, \$fstrobe, \$fmonitor, \$fwrite
- random generator
 - \$random
- suspend (\$stop) or finish (\$finish) simulation
- conversion functions
 - \$signed, \$unsigned

Compiler Directive

- start with back-quote symbol ```
 - cp. quote symbol, e.g., `8'b0101_0101`
- ``define`
 - define textmacro
 - e.g., ``define FILE_A "a.txt"`
 - ✓ ``FILE_A` is equivalent to `"a.txt"`
- ``ifdef ... `endif`
 - if some textmacro is defined, statements inside the ``ifdef` block will be executed
 - e.g., back-annotate wire delay information for simulation

```
`ifdef SDF_FILE  
    initial $sdf_annotate(`SDF_FILE, test_module)  
`endif
```

Verilog System Tasks

System Tasks **\$task_name**

- **\$display**
 - display values of variables or strings or expressions
 - \$display**("at time **%d** address is **%h**", **\$time**, addr);
- **\$monitor**
 - continuously monitor a signal *when its value is changed*
 - unlike **\$display**, **\$monitor** only needs to be invoked once
 - use **\$monitoroff** and **\$monitoron** to disable/enable
 - \$monitor** (**\$time**, "clock = **%b** reset = **%b**", clk, rst);
- **\$stop**
 - suspend the simulation for debug
- **\$finish**
 - terminate simulation

Some System Tasks

(see *IEEE std. 1364 document* for details)

- file output
 - **\$fopen, \$fdisplay, \$fmonitor, \$fwrite, \$fstrobe, \$fclose**
- display module hierarchy
 - **%m** option in \$display, \$monitor
- display signal values after all other events of that step
 - **\$strobe**
- random number generation
 - **\$random**
- initializing memory from file
 - **\$readmemb, \$readmemh**
- value change dump (vcd) file
 - **\$dumpvars, \$dumpfile, \$dumpon, \$dumpoff, \$dumpall**

\$strobe vs. \$display

- **\$display**

- if many other statements are executed in the same time unit as the task **\$display**, the execution order of the statements and **\$display** task is non-deterministic (depending on all the scheduled events at that time)

- **\$strobe**

- task **\$strobe** is always executed after all other assignment statements in the same time unit have executed
- provide synchronization mechanism to display data only after all other assignments are executed

Input, Output, Random, Conversion

- read from input
 - \$readmemb, \$readmemh
 - \$fscanf, \$fget. \$fread
- write to output
 - \$fopen, \$fclose
 - \$display, \$strobe, \$monitor, \$write
 - \$fdisplay, \$fstrobe, \$fmonitor, \$fwrite
- random generator
 - \$random
- suspend (\$stop) or finish (\$finish) simulation
- conversion functions
 - \$signed, \$unsigned

Escape character and string format

- %d
 - decimal
- %b
 - binary
- %o
 - octal
- %h
 - hexa-decimal
- %m
 - hierarchical name

Escaped Characters	Character Displayed
\n	newline
\t	tab
%%	%
\\	\
\"	"
\ooo	Character written in 1–3 octal digits

Format	Display
%d or %D	Display variable in decimal
%b or %B	Display variable in binary
%s or %S	Display string
%h or %H	Display variable in hex
%c or %C	Display ASCII character
%m or %M	Display hierarchical name (no argument required)
%v or %V	Display strength
%o or %O	Display variable in octal
%t or %T	Display in current time format
%e or %E	Display real number in scientific format (e.g., 3e10)
%f or %F	Display real number in decimal format (e.g., 2.13)
%g or %G	Display real number in scientific or decimal, whichever is shorter

opening file

```
// multichannel descriptor
```

```
integer handle1, handle2, handle3; // integers are 32-bit values
```

```
// standard output: descriptor=32'h0000_0001 (bit 0 is set to 1)
```

```
initial
```

```
begin
```

```
// one-hot encoding for file handlers, i.e., only one of the bits is 1
```

```
handle1 = $fopen("file1.out"); // handle1=32'h0000_0002 (bit 1 is set to 1)
```

```
handle2 = $fopen("file2.out"); // handle2=32'h0000_0004 (bit 2 is set to 1)
```

```
handle3 = $fopen("file3.out"); // handle3=32'h0000_0008 (bit 3 is set to 1)
```

```
end
```

writing to files, closing files

```
integer desc1, desc2, desc3;
```

```
initial
```

```
begin
```

```
desc1 = handle1 | 1; // desc1=32'h0000_0003
```

```
$fdisplay (desc1, "Display 1"); // write to files 'file1.out' & stdout
```

```
desc2 = handle2 | handle 1; // desc2=32'h0000_0006
```

```
$fdisplay (desc2, "Display 2"); // write to files 'file1.out' & 'file2.out'
```

```
desc3 = handle3;
```

```
$fdisplay (desc3, "Display 3"); // write to file 'file3.out' only
```

```
end
```

```
//closing files
```

```
$fclose (handle1);
```

Reading data from a file

```
// open a file for read type
```

```
// generate the 32-bit file descriptor fd
```

```
integer fd = $fopen("filename", "r");
```

```
// read a line at a time
```

```
// read characters into reg str
```

```
// return code = 0 if error, otherwise, code = # of characters read
```

```
integer code = $fgets (str, fd);
```

```
// read formatted data and place the result in variable args
```

```
integer code = $fscanf (fd, format, args);
```

Displaying Hierarchy

```
module M;  
...  
initial  
    $display ("Displaying in %m");  
endmodule  
  
// instantiate module M  
module top;  
    M m1(); // module instance m1 in top module M  
    M m2(); // module instance m2 in top module M  
    M m3(); // module instance m3 in top module M  
endmodule  
  
// output looks like  
// Displaying in top.m1  
// Displaying in top.m2  
// Displaying in top.m3
```

Random Number Generation (**\$random**)

- Seed can be either **reg**, **integer**, or **time** variable
- \$random** returns a 32-bit *signed* integer

```
module test;
integer r_seed;
reg [31:0] addr; // input to ROM
wire [31:0] data; // output from ROM
reg [23:0] rand1, rand2;
...
ROM rom1 (data, addr);
...
initial r_seed = 2; // arbitrarily define seed as 2, better use different seed values
always @(posedge clock)
    addr = $random (r_seed); // generate random numbers of signed integer
    rand1 = $random % 60; // generate random number between -59 and 59
    rand2 = {$random} % 60; // random number between 0 and 59
...
// check output of ROM against expected results
...
endmodule
```

Random Number Generation (**\$random**)

- Seed can be either **reg**, **integer**, or **time** variable
- \$random** returns a 32-bit *signed* integer

```
module test;
integer r_seed;
reg [31:0] addr; // input to ROM
wire [31:0] data; // output from ROM
reg [23:0] rand1, rand2;
...
ROM rom1 (data, addr);
...
initial r_seed = 2; // arbitrarily define seed as 2, better use different seed values
always @(posedge clock)
    addr = $random (r_seed); // generate random numbers of signed integer
    rand1 = $random % 60; // generate random number between -59 and 59
    rand2 = {$random} % 60; // random number between 0 and 59
...
// check output of ROM against expected results
...
endmodule
```

initializing memory from file

```
module test;
reg [7:0] memory [0:7];
integer i;

initial begin
// address in file init.dat is
// specified as @<address>
// and in hexadecimal numbers
$readmemb("init.dat", memory);

/* $readmemh is for reading in
   hexadecimal data */

for (i=0; i<8; i=i+1)
    $display("memory[%d]=%b", memory[i]);

end
endmodule
```

```
// content of file "init.dat"
// address in hexadecimal
@002
11111111 01010101
00000000 10101010
@006
1111zzzz 00001111
```

```
memory[0]=xxxxxxx
memory[1]=xxxxxxx
memory[2]=11111111
memory[3]=01010101
memory[4]=00000000
memory[5]=10101010
memory[6]=1111zzzz
memory[7]=00001111
```

System tasks

- Refer to Ch. 17 (System tasks and functions) in IEEE std. 1364-2005 document **IEEE Standard for Verilog® Hardware Description Language**
- system tasks are useful for writing testbench because most system tasks are non-synthesizable

Display tasks [\[17.1\]](#)

<code>\$display</code>	<code>\$write</code>
<code>\$displayb</code>	<code>\$writeb</code>
<code>\$displayh</code>	<code>\$writeh</code>
<code>\$displayo</code>	<code>\$wroteo</code>
<code>\$strobe</code>	<code>\$monitor</code>
<code>\$strobeb</code>	<code>\$monitorb</code>
<code>\$strobeh</code>	<code>\$monitorh</code>
<code>\$strobo</code>	<code>\$monitro</code>
	<code>\$monitoroff</code>
	<code>\$monitoron</code>

File I/O tasks [\[17.2\]](#)

<code>\$fclose</code>	<code>\$fopen</code>
<code>\$fdisplay</code>	<code>\$fwrite</code>
<code>\$fdisplayb</code>	<code>\$fwriteb</code>
<code>\$fdisplayh</code>	<code>\$fwriteh</code>
<code>\$fdisplayo</code>	<code>\$fwroteo</code>
<code>\$fstrobe</code>	<code>\$fmonitor</code>
<code>\$fstrobeb</code>	<code>\$fmonitorb</code>
<code>\$fstrobeh</code>	<code>\$fmonitorh</code>
<code>\$fstrobo</code>	<code>\$fmonitro</code>
<code>\$fwrite</code>	<code>\$sformat</code>
<code>\$fwriteb</code>	<code>\$fgetc</code>
<code>\$fwriteh</code>	<code>\$ungetc</code>
<code>\$swriteo</code>	<code>\$fgets</code>
<code>\$fscanf</code>	<code>\$sscanf</code>
<code>\$fread</code>	<code>\$rewind</code>
<code>\$fseek</code>	<code>\$ftell</code>
<code>\$fflush</code>	<code>\$ferror</code>
<code>\$feof</code>	<code>\$readmemb</code>
<code>\$sdf_annotate</code>	<code>\$readmemh</code>

Timescale tasks [\[17.3\]](#)

<code>\$prnttimescale</code>	<code>\$timeformat</code>
------------------------------	---------------------------

Simulation control tasks [\[17.4\]](#)

<code>\$finish</code>	<code>\$stop</code>
-----------------------	---------------------

PLA modeling tasks [\[17.5\]](#)

<code>\$asynce\$and\$array</code>	<code>\$asynce\$and\$plane</code>
<code>\$asynce\$and\$array</code>	<code>\$asynce\$and\$plane</code>
<code>\$asynce\$or\$array</code>	<code>\$asynce\$or\$plane</code>

<code>\$asynce\$nor\$array</code>	<code>\$asynce\$nor\$plane</code>
<code>\$synce\$and\$array</code>	<code>\$synce\$and\$plane</code>
<code>\$synce\$and\$array</code>	<code>\$synce\$and\$plane</code>
<code>\$synce\$or\$array</code>	<code>\$synce\$or\$plane</code>
<code>\$synce\$nor\$array</code>	<code>\$synce\$nor\$plane</code>

Stochastic analysis tasks [\[17.6\]](#)

<code>\$q_initialize</code>	<code>\$q_add</code>
<code>\$q_remove</code>	<code>\$q_full</code>
<code>\$q_exam</code>	

Simulation time functions [\[17.7\]](#)

<code>\$realtime</code>	<code>\$stime</code>
<code>\$time</code>	

Conversion functions [\[17.8\]](#)

<code>\$bitstoreal</code>	<code>\$realtobits</code>
<code>\$itor</code>	<code>\$rtol</code>
<code>\$signed</code>	<code>\$unsigned</code>

Probabilistic distribution functions [\[17.9\]](#)

<code>\$random</code>	<code>\$dist_chi_square</code>
<code>\$dist_erlang</code>	<code>\$dist_exponential</code>
<code>\$dist_normal</code>	<code>\$dist_poisson</code>
<code>\$dist_t</code>	<code>\$dist_uniform</code>

Command line input [\[17.10\]](#)

<code>\$test\$plusargs</code>	<code>\$value\$plusargs</code>
-------------------------------	--------------------------------

Math functions [\[17.11\]](#)

<code>\$clog2</code>	<code>\$asin</code>
<code>\$ln</code>	<code>\$acos</code>
<code>\$log10</code>	<code>\$atan</code>
<code>\$exp</code>	<code>\$atan2</code>
<code>\$sqrt</code>	<code>\$hypot</code>
<code>\$pow</code>	<code>\$sinh</code>
<code>\$floor</code>	<code>\$cosh</code>
<code>\$ceil</code>	<code>\$tanh</code>
<code>\$sin</code>	<code>\$asinh</code>
<code>\$cos</code>	<code>\$acosh</code>
<code>\$tan</code>	<code>\$atanh</code>

conditional execution **\$test\$plusargs**

- All codes are compiled but executed conditionally
- flag set at *run time* by the option **+DISPLAY_VAR** when running the simulator tool

```
module test;

initial
begin
    if ( $test$plusargs("DISPLAY_VAR") )
        $display("display=%b", {a,b,c});
    else
        $display("no display")
end
// the variables are displayed only if flag DISPLAY_VAR is set at run time

endmodule
```

invoke simulator with option **+DISPLAY_VAR** in the tool command line

conditional execution **\$value\$plusargs**

- **\$value\$plusargs** return 0 if a matching invocation is not found and nonzero if a matching option is found


```
module test;
reg [8*128-1:0] test_string;
integer clk_period;
initial
begin
    if ( $value$plusargs("testname=%s", test_string) )
        $readmemh (test_string, vectors);
    else
        $display("test name not specified");

    if ( $value$plusargs("clk_t=%d", clk_period) )
        forever #(clk_period/2) clk=~clk;
    else
        $display("clk period not specified");
endmodule
```

- invoke simulator with option **+testname=test1.vec +clk_t=10** in the tool command line


Value Change Dump (VCD) file

- A *VCD file* contains information about value changes on selected variables
- post-processing tools (such as Synopsys PrimeTime) can take the VCD file as input and visually display waveforms for easy debugging and analyzing
 - Synopsys PrimeTime is *dynamic timing analysis* tool that requires test input patterns to analyze the delay and power
 - c.p. Synopsys Design Compiler is static timing analysis (STA) tool which does not require any input test pattern
- VCD could be very large
 - only dump signals that need to be examined

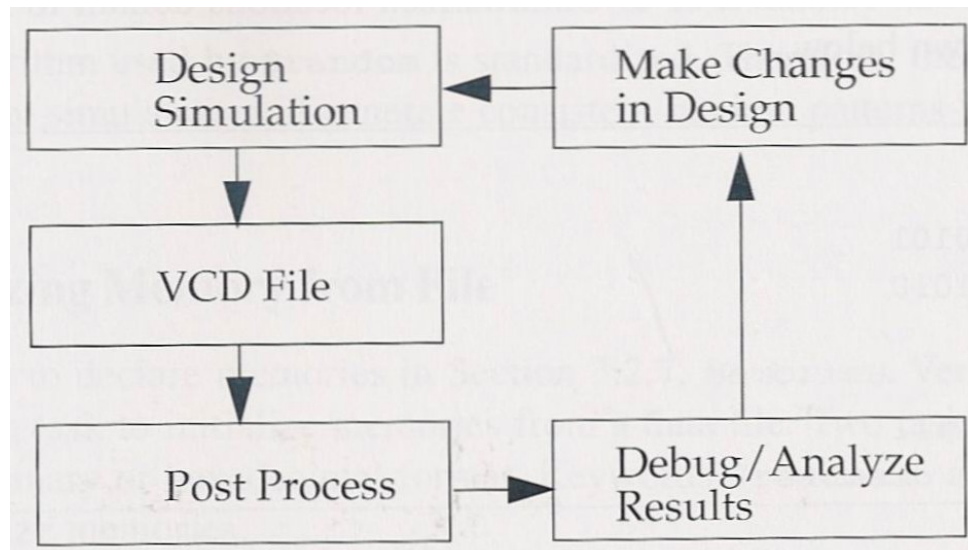

creating 4-state VCD file

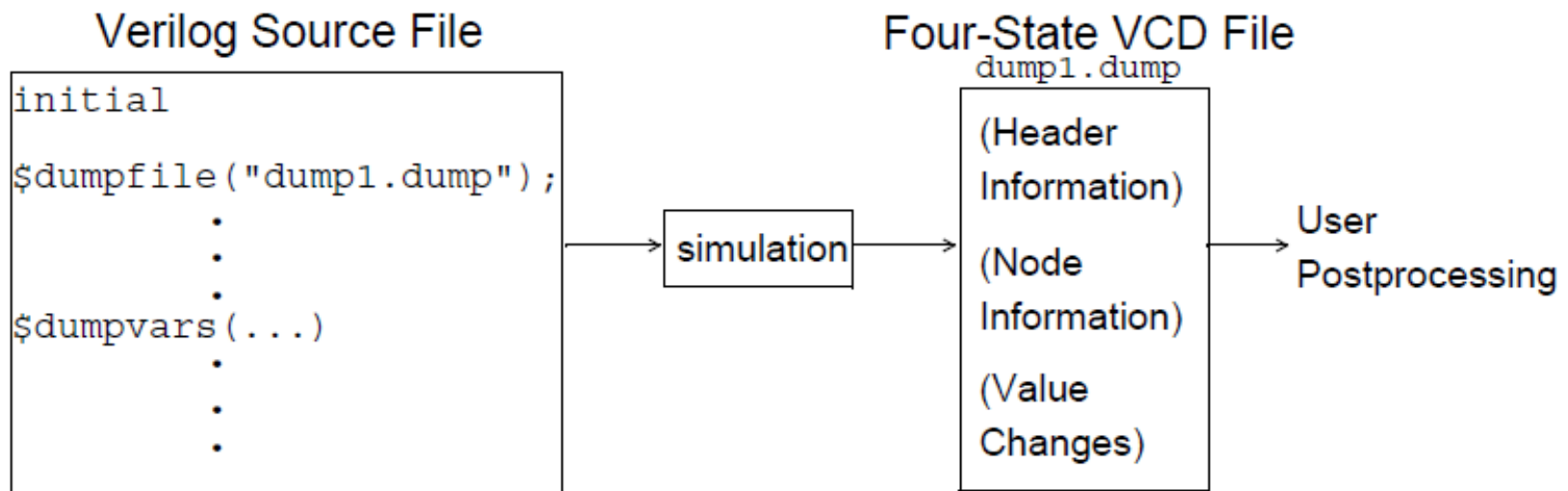- insert VCD system tasks in the Verilog source file to define the dump file name and to specify the variables to be dumped
- run the simulation
- 4-state VCD file
 - variable changes in 0, 1, x, z, with no strength information



system tasks for VCD

```
// dump simulation information into myfile.dmp
```

```
  initial $dumpfile ("myfile.dmp");
```

```
// select module instances or module instance signals to dump,
```

```
// cause dump to start at the end of current simulation time
```

```
  Initial $dumpvars; // no argument, dump all signals
```

```
// dump variables in module instance top, dump one hierarchy level below top
```

```
  initial $dumpvars (1, top);
```

```
// dump up to 2 levels of hierarchy below top.m1
```

```
  initial $dumpvars (2, top.m1);
```

```
// number 0 means dump the entire hierarchy below top.m1
```

```
  initial $dumpvars (0, top.m1);
```

```
initial
```

```
  begin
```

```
    $dumpoff; // suspend the dump
```

```
    #10000; $dumpson; // resume the dump
```

```
  end
```

```
initial // create a checkpoint. dump current values of all VCD variables
```

```
  $dumpall;
```

Compiler Derivatives

Compiler Directives ` (back quote)

- **`define**
 - define text macro for later text macro substitution

```
`define WORD_SIZE 32  
// used as `WORD_SIZE in the code such as  
// wire [`WORD_SIZE-1:0] a, b, c;
```
- **`include**
 - include another Verilog file, e.g.,
 - **`include** header.v //include the file header.v
- **`ifdef**
 - conditional compilation

```
`ifdef TEST module test;  
// compile module test only if text macro TEST  
// is defined using `define TEST
```
- **`timescale**

```
`timescale 100ns/1ns
```

`define` `ifdef` `else` `endif`

```
`define` TEXT_MACRO_NAME // comment out this line if do not want this definition
...
// do not confuse with if ... else in always procedure block which synthesize MUX
// compiler directive `ifdef` ... `else` ... does not synthesize MUX hardware
`ifdef` TEXT_MACRO_NAME // conditional compilation with `else
    // compile the following statements here if TEXT_MACRO_NAME is defined
    ...
`else` // `else` compiler directive is optional
    // compile the following statements here if TEXT_MACRO_NAME is not defined
    ...
`endif`

`ifdef` TEXT_MACRO_NAME // conditional compilation without `else
    // compile the following statements here if TEXT_MACRO_NAME is defined
    // the following statements are skipped if TEXT_MACRO_NAME is not defined
    ...
`endif`
```


conditional compilation

- the conditional compile flag can be set by using the **`define** statement inside the Verilog file

```
`ifdef TEST // compile module test only if text macro TEST is defined using `define  
    module test; .... endmodule  
`else // compile module stimulus by default  
    module stimulus; ... endmodule  
  
module top;  
  
    bus_master b1(); // instantiate module unconditionally  
`ifdef ADD_B2    bus_master b2(); // b2 is instantiated if text macro ADD_B2 is defined  
`elseif ADD_B3  bus_master b3(); // b3 is instantiated if text macro ADD_B3 is defined  
`else          bus_master b4(); // b4 is instantiated by default  
`endif  
  
`ifndef IGNORE_B5  bus_master b5();  
                    // b5 is instantiated only if text macro IGNORE_B5 is not defined  
`endif  
  
endmodule
```

Compiler Directives **`** (back quote)

- **`define**
 - define text macro for later text macro substitution

```
`define WORD_SIZE 32  
// used as `WORD_SIZE in the code such as  
// wire [`WORD_SIZE-1:0] a, b, c;
```
- **`include**
 - include a Verilog source file in another file

```
`include header.v //include the file header.v
```
- **`ifdef**
 - conditional compilation

```
`ifdef TEST module test;  
// compile module test only if text macro TEST  
// is defined using `define TEST
```
- **`timescale**

```
`timescale 100ns/1ns
```

`define`ifdef`else`endif

```
`define TEXT_MACRO_NAME
```

```
...
```

```
`ifdef TEXT_MACRO_NAME // conditional compilation with `else  
    statement_1;
```

```
...
```

```
`else // `else compiler directive is optional  
    alternative_statement_1;
```

```
...
```

```
`endif
```

```
`ifdef TEXT_MACRO_NAME // conditional compilation without `else  
    statement_1;
```

```
...
```

```
`endif
```

`timescale

- **`timescale** <time_unit> / <time_precision>
- Only 1, 10, 100 are valid integers

```
`timescale 100ns/1ns
```

```
module dummy;
```

```
reg toggle;
```

```
initial toggle=1'b0;
```

```
always #5
```

```
begin
```

```
    toggle = ~toggle;
```

```
    $display("%d, In %m toggle=%b", $time, toggle);
```

```
    // 5, in dummy toggle=1
```

```
    // 10, in dummy toggle=0
```

```
    // 15, in dummy toggle=1 ....
```

```
end
```

```
endmodule
```

```
`timescale 1us/10ns // change time scale for module dummy2
```

```
module dummy2;
```

Compiler Directive


- Refer to Ch. 19 (Compiler directives) in IEEE std. 1364-2005 document
IEEE Standard for Verilog® Hardware Description Language

<code>`begin_keywords</code>	[19.11]
<code>`celldefine</code>	[19.1]
<code>`default_nettype</code>	[19.2]
<code>`define</code>	[19.3]
<code>`else</code>	[19.4]
<code>`elsif</code>	[19.4]
<code>`end_keywords</code>	[19.11]
<code>`endcelldefine</code>	[19.1]
<code>`endif</code>	[19.4]
<code>`ifdef</code>	[19.4]
<code>`ifndef</code>	[19.4]
<code>`include</code>	[19.5]
<code>`line</code>	[19.7]
<code>`nounconnected_drive</code>	[19.9]
<code>`pragma</code>	[19.10]
<code>`resetall</code>	[19.6]
<code>`timescale</code>	[19.8]
<code>`unconnected_drive</code>	[19.9]
<code>`undef</code>	[19.3]

Verilog Operators, Data Types

Components of a Verilog Module

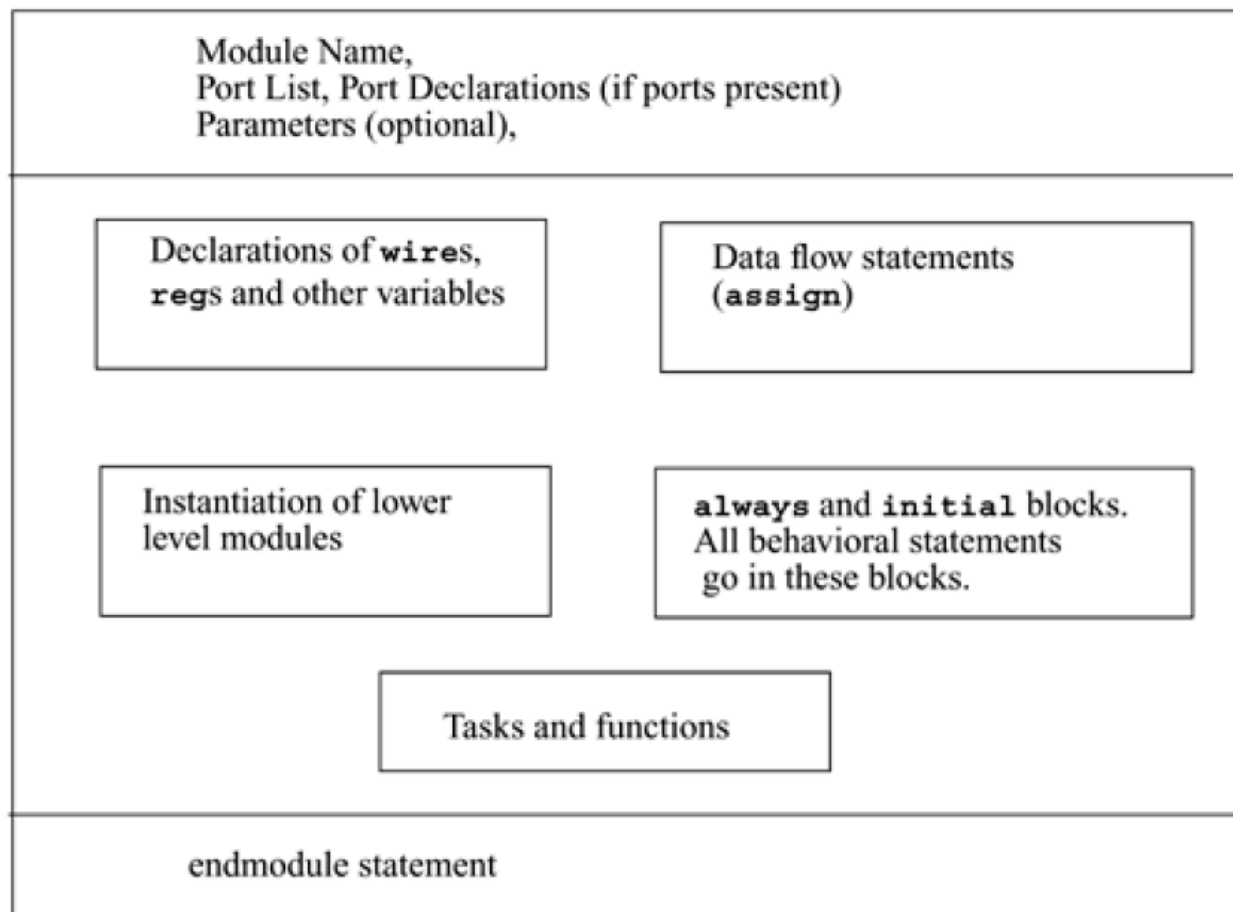- declaration
 - inputs, outputs
 - parameters
 - data types
- structure model
- module instantiation
- dataflow model
 - continuous assignment
- behavior model
 - procedural assignment



```

module M (P1, P2, P3, P4);
input P1, P2;
output [7:0] P3;
inout P4;

reg [7:0] R1, M1[0:1023];
wire W1, W2, W3, W4;
wire [3:0] W5;
parameter C1=const;

```

```

// non-synthesizable coding
// used in testbench
initial
begin : blockname
    // statements
end

```

```

// behavioral modeling
always
begin
    // statements
end

```

```

// dataflow: continuous assignment
assign W1 = expr ; // use operators

```

```

// module instances: structural modeling
COMP U1 (.PP2(W2), .PP1(W1);
COMP U2 (W3, W4);

```

```

task T1;
input A1, A2;
output A3, A4;
begin
    // statements
end
endtask


```

```

function [7:0] F1;
input A1;
begin
    // statements
end
endfunction

endmodule

```

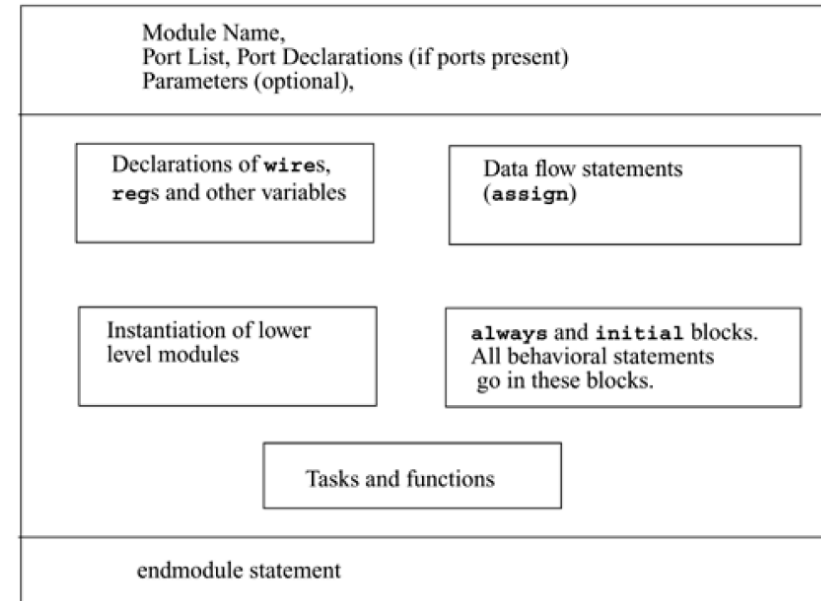

Verilog Operators

`a = ~b // not b (unary operator); only one operand: b`
`// output could be multiple bits, the same bit-width as the input`

`a = b && c; // logical AND operation (binary operator)`
`// two operands: b, c`
`// output a is either TRUE (logic 1) or FALSE (logic 0)`
`// cp. a = b & c; // bitwise (bit-by-bit) operator`
`// output of bit-wise operator could be multi-bit`
`// with the same bit-width as that of inputs`

`a = b ? c : d; // MUX2 (ternary operator)`
`// a=c if b=1,`
`// a=d if b=0`
`// three operands: b, c, d`

Other operators

- arithmetic operators (+, -, *, /, %, **)
- relational operators (<, >, <=, >=)
- equality operators (==, !=, ===, !==)
- logical operators (&&, ||, !)
- bitwise operators (~, &, |, ^, ~^)
- reduction operators (&, ~&, , |, ~|, , ^, ~^)
- shift operators (>>, <<, >>>, <<<)
- concatenation operator ({ })
- conditional operator (? :)

Operator Types and Symbols

Operator Type	Operator Symbol	Operation Performed	Number of Operands
Arithmetic	*	multiply	two
	/	divide	two
	+	add	two
	-	subtract	two
	%	modulus	two
	**	power (exponent)	two
Logical	!	logical negation	one
	&&	logical and	two
		logical or	two
Relational	>	greater than	two
	<	less than	two
	>=	greater than or equal	two
	<=	less than or equal	two
Equality	==	equality	two
	!=	inequality	two
	===	case equality	two
	!==	case inequality	two

Operator Type	Operator Symbol	Operation Performed	Number of Operands
Bitwise	~	bitwise negation	one
	&	bitwise and	two
		bitwise or	two
	^	bitwise xor	two
	^~ or ~^	bitwise xnor	two
Reduction	&	reduction and	one
	~&	reduction nand	one
		reduction or	one
	~	reduction nor	one
	^	reduction xor	one
	^~ or ~^	reduction xnor	one
Shift	>>	Right shift	Two
	<<	Left shift	Two
	>>>	Arithmetic right shift	Two
	<<<	Arithmetic left shift	Two
Concatenation	{ }	Concatenation	Any number
Replication	{ { } }	Replication	Any number
Conditional	?:	Conditional	Three

Equality Operator

- $A=4_{10}=0100_2$, $B=3_{10}=0011_2$,
 $A == B$ // results in FALSE, (logical 0)

$X=4'b1010$

$Y=4'b1101$

$Z=4'b1xxz$

$M=4'b1xxz$

$N=4'b1xxx$

$X != Y$ // result in TRUE (logical 1)

$X == Z$ // result in x

$Z === M$ // result in logical 1 TRUE (all bits match, including x and z)

$Z === N$ // result in logical 0 FALSE (LSB does not match)

$M !== N$ // result in logical 1 TRUE

$===, !==$ are in general non-synthesizable

Expression	Description	Possible Logical Value
$a == b$	a equal to b, result unknown if x or z in a or b	0, 1, x
$a != b$	a not equal to b, result unknown if x or z in a or b	0, 1, x
$a === b$	a equal to b, including x and z	0, 1
$a !== b$	a not equal to b, including x and z	0, 1

Equality Operator: Logical vs. Case

- logical equality operator (**==**)
 - 0, 1, x (unknown), z (floating)

==	0	1	X	Z
0	1	0	X	X
1	0	1	X	X
X	X	X	X	X
Z	X	X	X	X

- case equality operator (**===**)

===	0	1	X	Z
0	1	0	0	0
1	0	1	0	0
X	0	0	1	0
Z	0	0	0	1

reduction operator

- perform bitwise operator on all bits of a single vector and yield a 1-bit result

- e.g.

$X = 4'b1010$

$\&X \quad // = 1\&0\&1\&0 = 1'b0$

$|X \quad // = 1|0|1|0 = 1'b1$

$\^X \quad // = 1\^0\^1\^0 = 1'b0$

Concatenation Operator

Replication Operator

- $A=1'b1$, $B=2'b01$, $C=2'b10$
- concatenation operator
 $Y=\{B,C\} = 4'b0110$
- replication operator
 $Y=\{ 4\{A\}, 2\{B\} \}=8'b1111_0101$

Number

unsized numbers (decimal by default), e.g., $b=a+1$;
sized numbers:

<size>'<base format> <number>

<size>: the number of bits

'<base>: 'd (decimal),

'h (hexadecimal),

'b (binary),

'o (octal)

' is the single quote symbol, **not** back quote symbol ` which will be used in compiler directive such as **`include**

e.g.,

4'**b**1111 // 4-bit binary number $1111_2=15_{10}$

12'**h**abc // 12-bit hexadecimal number = $1010_1011_1100_2$

16'**d**255 // 16-bit decimal number = 0000000011111111_2

'**b**1111 // $1111_2=15_{10}$ extended to required bit-width

Data types: value set

- 4 values (0, 1, z, x), 8 strengths
 - strength is used when two data signals are conflicting

Value Level	Condition in Hardware Circuits
0	Logic zero, false condition
1	Logic one, true condition
x	Unknown logic value
z	High impedance, floating state

Strength Level	Type	Degree
supply	Driving	strongest
strong	Driving	▲
pull	Driving	
large	Storage	
weak	Driving	
medium	Storage	▼
small	Storage	
highz	High Impedance	weakest

Four-Valued Logic System

- Signal and variable values represented using a 4-valued logic system
 - 1'b0: 1-bit binary logic 0 value
 - 1'b1: 1-bit binary logic 1 value
 - 1'bx: 1-bit binary 'x' or 'X' value
 - ✓ Unknown value, produced for uninitialized values or values driven to conflicting values by more than one signal source
 - 1'bz: 1-bit binary 'z' or 'Z' value
 - ✓ High impedance value, produced when a wire is **disconnected** from all signal sources driving that wire, i.e., floating node

data types (**wire** and **reg**)

- Nets (**wire**): connections between hardware elements
 - nets have values continuously driven by outputs of devices they are connected to, using continuous assignment **assign**
 - e.g.: **wire** a, b, c;
wire a = b & c; // equivalent to **wire** a; **assign** a = b & c;
- Registers (**reg**): data storage element
 - a variable that can hold a value in procedural assignment blocks starting with **always** or **initial**
 - *not necessarily* mean a flip-flop (one-bit register) in real circuit
 - e.g.: **reg** q;
always @ (posedge clk) q <= d;
- SystemVerilog use **logic** to replace 4-value **wire** and **reg** to avoid confusion
 - not all **reg** data types synthesize into hardware registers

data types (vectors)

- Vectors: multiple bit widths (default is scalar)
`wire [7:0] bus;` // 8-bit signal, bus[7] is the MSB, bus[0] is the LSB
`wire [31:0] word;` // 32-bit word
`reg [255:0] data;` // 256-bit word register, data[255] is MSB
`reg [0:40] v_addr;` // v_addr[0] is MSB
 - Vector Part Select
word[7:0] // the least significant byte of the 32-bit vector word
v_addr[0:1] // two most significant bits of the vector v_addr
 - variable vector part select
[<starting_bit> +: width] : part-select *increments*
[<starting_bit> -: width] : part-select *decrements*
starting bit can be varied, but the width must be constant
- eg1.: `reg [255:0] data1;` // MSB->LSB with decreasing index order
`reg [0:255] data2;` // MSB->LSB with increasing index order
`reg [7:0] byte;`
- `byte=data1[31 -:8] // data1[31:24]`
`byte=data1[24 +:8] // data1[31:24]`
`byte=data2[31 -:8] // data2[24:31]`
`byte=data2[24 +:8] // data2[24:31]`
- e,g,. `reg [255:0] data1;`
`for (j=0; j<=31; j=j+1) byte = data1[(j*8)+:8] ;`
// sequence is [7:0], [15:8], [23:16], ..., [255:248]

register data types (**integer**, **real**, **time**)

- **integer**: register data type used for signed quantity
 - **reg** store a multi-bit signal which could mean a *unsigned* quantity, while **integer** store *signed* quantity
 - e.g., **integer** counter; counter = -1; // used as a counter
- **real**: real number constant or register data type
 - e.g. **real** delta;
 - delta = 4e10; delta = 2.14; // delta is a real variable
- **time**: register data type to store simulation time
 - e.g. **time** save_sim_time;
 - save_sim_time = **\$time**; // define a time variable
 - // system task **\$time** is invoked to get current simulation time
- **real** and **time** are *non-synthesizable* codes, for simulation only

signed vs. unsigned

- unsigned (default Verilog data type)

```
wire [3:0] x;  
wire [7:0] y;  
  
assign y = {4'b0000, x};
```

```
wire [3:0] x;  
wire [7:0] y;  
  
assign y = x; // zero padded
```

- signed (new data type added in 2001)

```
wire signed [3:0] x;  
wire signed [7:0] y;  
  
assign y = {4{x[3]}, x};
```

```
wire signed [3:0] x;  
wire signed [7:0] y;  
  
assign y = x; // sign-extended
```

```
wire [11:0] s1;  
wire signed [11:0] s2;  
  
assign s2 = $signed(s1); // convert to signed number  
// assign s1 = $unsigned(s2); // convert to unsigned number
```

Arithmetic (**unsigned** vs. **signed**)

- unsigned

```
wire [7:0] a, b, s;  
wire [8:0] s1;  
wire [15:0] p;  
wire c;  
  
assign s = a + b; // no overflow detection (e.g., 255+1 = 1111_1111+0000_0001 = 0000_0000 = 0)  
// assign s1 = {1'b0, a} + {1'b0, b}; // adding 1 bit of zero to prevent overflow  
// assign s1 = a + b; // implicit extension by Verilog  
assign p = a * b;
```

- signed

```
wire signed [7:0] a, b, s;  
wire signed [8:0] s1;  
wire signed [15:0] p;  
  
wire signed [8:0] s;  
  
assign s = a + b; // no overflow detection (e.g., (-1)+(-255) = 1111_1111+1000_000 = 0111_1111 = +127)  
// assign s1 = {a[7], a} + {b[7], b}; // sign extension by 1 bit to prevent overflow in 2's complement  
// assign s1 = a + b; // implicit sign extension by Verilog  
assign p = a * b;
```

- both unsigned and signed generate the same results in case of normal operation (without overflow or bit-width mis-match

Same Bit-Width in Assignment

- In most normal cases, LSH and RHS of assignments have the same bit-width
 - unsigned and signed types represent same hardware

```
wire [7:0] a, b, c;  
assign c = a+b;
```

```
wiresigned [7:0] a, b, c;  
assign c = a+b;
```

- avoid assignments with mis-matched bit-width
 - otherwise, synthesizer might expand bit-width which is not as you expect

```
wire [7:0] a, b;  
wire [8:0] c;  
assign c = a+b;  
// if a, b=8'b1000_0000=+128  
// c=9'b1_0000_0000=+256
```

```
wire [7:0] a, b;  
wire [8:0] c;  
assign c = a+b;  
// if a, b=8'b1000_0000= -128  
// c=9'b1_0000_0000= -256
```


data types (array and memory)

- Arrays

```
reg [4:0] port_id [0:7];
```

```
// array of 8 elements, with each element 5-bit wide
```

```
port_id[6] = 5`b00000; // the array element with index=6
```

```
reg [63:0] array_4d [15:0] [7:0] [7:0] [255:0];
```

```
// 4-d array, new Verilog, IEEE1364-2001
```

- Memory (register files, RAM, ROM)

```
reg [7:0] membyte [0:1023]; // 1K bytes (1024x8) memory
```

```
data = membyte[511] // fetch 1 byte whose address id=511
```

- Use tool-supported memory generator/compiler (instead of registers) to create area-efficient memory (instead of area-costly flip-flop-based array)

data type (parameter)

- Parameters
 - allows constants to be defined in a module
 - parameter values for each module instance can be overridden individually at compile time

parameter cache_line_width = 256;

// constant defined inside a module

// parameter values can be changed

// at module instantiation **#()** or by using **defparam**

localparam // parameter values cannot be changed

state1=4'b0001,

state2=4'b0010,

state3=4'b0100,

state4=4'b1000;

Overriding Parameters (**defparam**)

```
// module #(parameter id_num=0) hello_world;  
module hello_world;  
    parameter id_num = 0;  
    initial $display("hello _world id number=%d", id_num);  
endmodule
```

```
module top;  
    // defparam is considered a bad coding style !!!  
    // can use #() to overwrite the default parameter values  
    defparam w1.id_num=1, w2.id_num=2;  
    hello_world w1();      // hello_world #(1) w1();  
    hello_world w2();      // hello_world #(2) w2();  
endmodule
```

Module instance parameter values (#)

```
module #(parameter delay1=2, delay2=3, delay3=7);
```

```
module bus_master;
```

```
parameter delay1=2;
```

```
parameter delay2=3;
```

```
parameter delay3=7;
```

```
endmodule
```

```
module top;
```

```
bus_master #(4,5,6) b1(); // delay1=4, delay2=5, delay3=6
```

```
bus_master #(9,4) b2(); // delay1=9, delay2=4,
```

```
bus_master #(.delay2(4), .delay3(7)) b3();
```

```
                // delay2=4, delay3=7
```

```
endmoudle
```

data type (parameter)

- Parameters
 - allows constants to be defined in a module
 - parameter values for each module instance can be overridden individually at compile time

parameter cache_line_width = 256;

// constant defined inside a module

// parameter values can be changed

// at module instantiation **#()** or by using **defparam**

localparam // parameter values cannot be changed

state1=4'b0001,

state2=4'b0010,

state3=4'b0100,

state4=4'b1000;

Notes on Dataflow Statements (1/2)

- dataflow statements with continuous assignment usually describe “combinational logic”
 - pure feed-forward datapath
 - LHS signal should be different from the RHS signals
 - e.g., assign c=a+b; // describe an adder
 - e.g., assign d=c+1; // describe an adder with one input=1
 - e.g., assign c=c+1; // Not OK!!! , c in LHS and RHS
 - ✓ a loop in the datapath
 - use register in behavioral modeling to describe a counter
 - e.g.,

```
// behavioral statements are inside always block  
// draw the hardware of the following statements  
reg [7:0] c;  
always @ (posedge clk)  
    c <= c+1;
```

Notes on Dataflow Statements (2/2)

- all dataflow statements are concurrent
 - different order of statements results in same hardware
 - e.g.,

```
// an adder, a subtractor,  
// and a multiplier  
wire [7:0] a, b, c, d  
assign c=a+b;  
assign d=a-b;  
assign e=c*d;
```


```
// a subtractor, a multiplier,  
// and an adder  
wire [7:0] a, b, c, d  
assign d=a-b;  
assign e=c*d;  
assign c=a+b;
```
- similar behavioral statements could describe the same combinational logic
 - e.g., inside always block

```
reg [7:0] a, b, c, d;  
always @(a, b, c, d)  
begin  
    c=a+b;  
    d=a-b;  
    e=c*d;  
end
```

Modules and Ports

Components of a Verilog Module

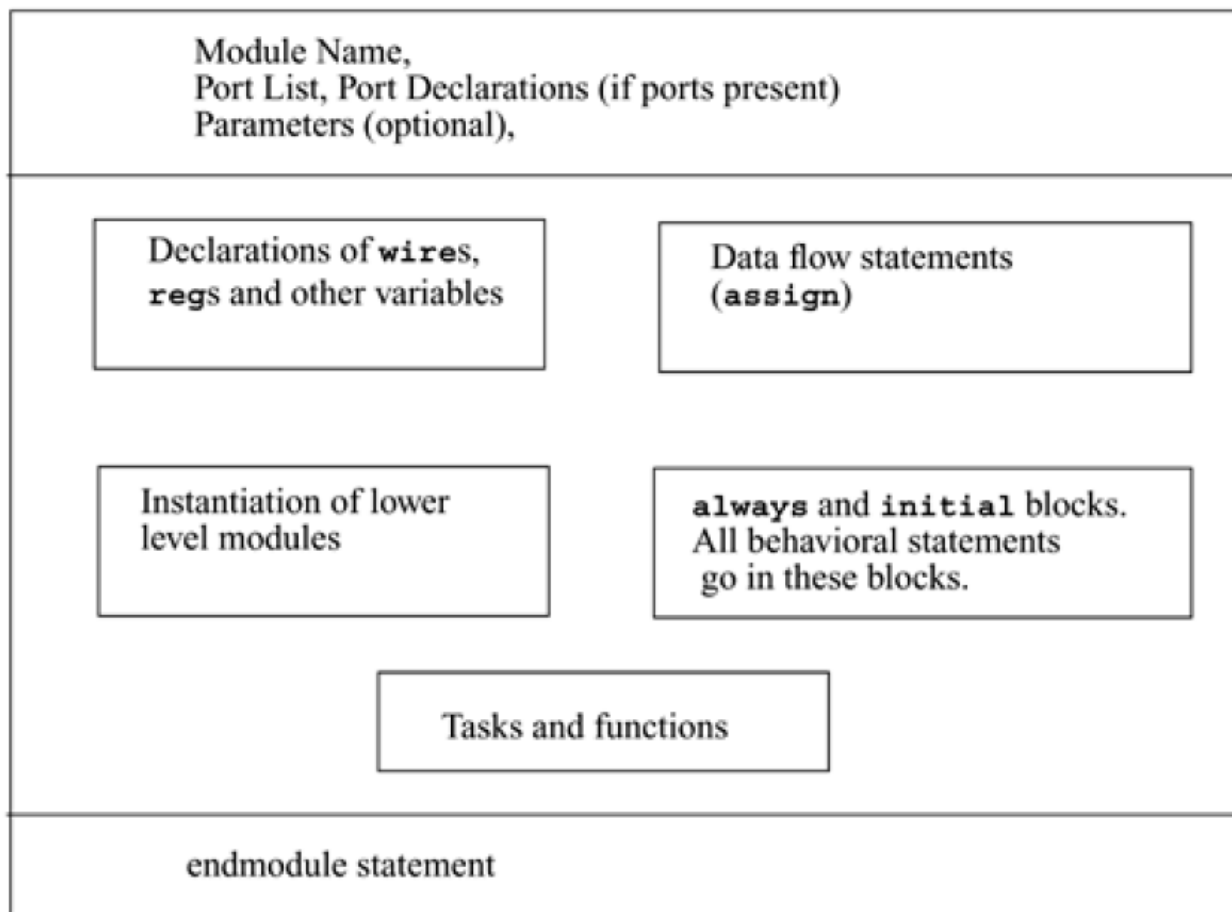- declaration
 - inputs, outputs
 - parameters
 - data types
- **structure** model
- module instantiation
- **dataflow** model
 - continuous assignment
- **behavior** model
 - procedural assignment



```
module M (P1, P2, P3, P4);
input P1, P2;
output [7:0] P3;
inout P4;
```

```
reg [7:0] R1, M1[0:1023];
wire W1, W2, W3, W4;
wire [3:0] W5;
parameter C1=const;
```

```
// non-synthesizable coding
// used in testbench
initial
begin : blockname
    // statements
end
```

```
// behavioral modeling
always
begin
    // statements
end
```


```
// dataflow: continuous assignment
assign W1 = expr ; // use operators
```

```
// module instances: structural modeling
COMP U1 (.PP2(W2), .PP1(W1);
COMP U2 (W3, W4);
```

```
task T1;
input A1, A2;
output A3, A4;
begin
    // statements
end
endtask
```

```
function [7:0] F1;
input A1;
begin
    // statements
end
endfunction

endmodule
```

 

Structural, Dataflow, Behavioral Modeling

- structural modeling
 - instantiation of other modules
 - e.g. FA instance_name (sum, cout, a, b, cin);
- dataflow modeling
 - continuous assignment **assign**
 - e.g., **assign** {cout, sum} = a + b + cin;
- behavioral modeling
 - procedural assignments inside **always @(...)** block
 - e.g.

```
reg [31:0] sum;  
reg cout;
```

```
always @ (a, b, cin)  
    {cout, sum} = a + b + cin;
```

Statements inside Behavioral Modeling

#delay // neglected during synthesis

wait (expression)

@(A **or** B **or** C)

@(**posedge** clk)

Reg = expression; // blocking assignment

Reg <= expression; // non-blocking assignment

if (condition1) ... **else if** (condition2) ... **else** ...

case (selection)

choice1 : **begin** ... **end**

choice2, choice 3: ...

...

default : ...

endcase

for (i=1; i<max; i=i+1) **begin** ... **end**

repeat (8) ...


while (condition) ...

```

module SR_latch (Q, Qbar, Sbar, Rbar);
output Q, Qbar;
input Sbar, Rbar;
    nand n1(Q, Sbar, Qbar);
    nand n2(Qbar, Rbar, Q);
endmodule

```

Example: SR latch

 

```

module top; // testbench for the SR_latch
wire q, qbar;
reg set reset;

```

```

SR_latch m1(q, qbar, ~set, ~reset);

```

```

initial
begin

```

```

    $monitor ($time, "set= %b  reset = %b, q= %b\n", set, reset, q);

```

```

    set = 0; reset = 0;

```

```

    #5 reset = 1;

```

```

    #5 reset = 0;

```

```

    #5 set = 1;

```

```

end
endmodule


```

- hierarchical name
 - top.qbar
 - top.m1
 - top.m1.n1

Port Declaration (1995 vs. 2001)


```
// IEEE 1364-1995 (old)
module fulladd4(sum, c_out, a, b, c_in);
parameter width = 4;
output [width-1:0] sum;
output c_out;
input [width-1:0] a, b;
input c_in;
reg [width-1:0] sum;
reg c_out;
...
endmodule
```
 
```
// ANSI C style (IEEE 1364-2001)
module
  # (parameter width =4)
  fulladd4 (
    output reg [width-1:0] sum,
    output reg c_out,
    input [width-1:0] a, b,
    input c_in
  );
  ...
endmodule
```




Port Connection Rules

- all port declarations are implicitly declared as net **wire**
- **input** and **inout** cannot be declared as **reg**
- **input**
 - internally (inside the module), always be of the type **wire**
 - externally (outside the module), can be connected to **reg** or **wire**
- **output**
 - internally, can be **reg** or **wire**
 - externally, always connected to **wire**
- **inout**
 - always be **wire** internally or externally

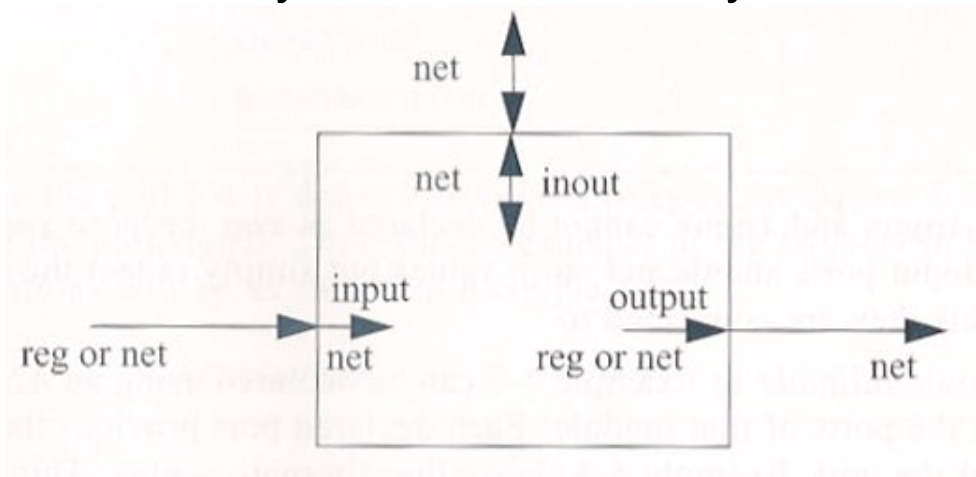

 **Latched module provides
Enough driving strength,
And break critical path**



Common Errors in Data Types

- a procedural assignment (inside **always** block) is made to a net (wire)
 - error message: “illegal left-hand-side assignment”
- signal (in the externally upper module) connected to an output port of a module instance is a register
 - error message: “illegal output port specification”
- an input of a module is declared as a register
 - error message: “incompatible declaration”
- signal of a primitive gate output is a register
 - error message: “gate has illegal output specification”

Connecting Ports to External Signals

- Module instantiation

- ✓ connecting by order list

```
// instantiate fulladd4 (output sum, c_out, input a, b, c_in)
```

```
// call it fa_ordered, signals are connected to ports in order (by position)
```

```
fulladd4 fa_ordered (EXT_SUM, EXT_C_OUT, EXT_A, EXT_B, EXT_C_IN);
```

- ✓ connecting by name

```
// instantiate module fa_byname and connect signals to ports by name
```

```
fulladd4 fa_byname
```

```
(.c_out(EXT_C_OUT), .sum(EXT_SUM), .b(EXT_B), .c_in(EXT_C_IN), .a(EXT_A));
```

```
module fulladd4 (sum, c_out, a, b, c);
```

```
output [3:0] sum;
```


```
output c_cout;
```

```
input [3:0] a, b;
```

```
input c_in;
```

```
....
```

```
endmodule
```

 

structural modeling

- component instantiation
 - Verilog *built-in* gate primitives (**not, and, or, nand, nor, xor, xnor, ...**)
 - module instantiation (from previously user defined modules)
- component connectivity
 - connecting by ordered lists (ordered by position)
fulladd4 fa_ordered (**EXT_SUM, EXT_C_OUT, EXT_A, EXT_B, EXT_C_IN**)
 - connecting by name (order by name)
fulladd4 fa_byname
(**.c_out(EXT_C_OUT), .sum(EXT_SUM), .b(EXT_B), .c_in(EXT_C_IN), .a(EXT_A)**);

array NOT allowed in I module I/O Ports

- module input/output ports could be data type of bit-vector, but not array
 - e.g., MUX4 (input [3:0] in, [1:0] s, output [3:0] out); // OK
 - e.g., MUX4 (input in [3:0], [1:0] s, output out); // NOTOK
- use long bit-vector as input/outputs and make conversion inside the module
 - e.g. MUX4 with 16-bit inputs/output

```
module MUX4 (input [4*16-1:0] in_bv, [1:0] s, output [15:0] out);  
  reg [15:0] in[0:3];  
  always@ (*) begin  
    for (i=0; i<4; i=i+1) in[i]= in_bv[16*i +:16]; // long bit-vector -> array  
    ...  
  endmodule
```

another example: DP4

- 4-D dot-product: $a[0]*b[0] + a[1]*b[1] + a[2]*b[2] + a[3]*b[3]$

```
module DP4 (input[16*4-1:0]in_a, in_b, output [31:0]out);  
  wire [15:0] a[3:0], b[3:0];
```

```
  // convert two long bit-vectors in_a, in_b into two arrays a, b  
  assign {a[3],a[2],a[1],a[0]}=in_a;  
  assign {b[3],b[2],b[1],b[0]}=in_b;
```

```
  integer i;  
  reg [31:0] tmp[0:3];  
  always @ (*) begin  
    tmp[0] = a[0]*b[0];  
    for (i=1; i<=3; i=i+1) tmp[i] = a[i]*b[i] + tmp[i-1];  
  end
```

```
  assign out = tmp[3];
```

```
endmodule
```

another example: DPn

- n-D dot-product


```
module #parameter n=4 DPn (input[16*n-1:0]in_a, in_b, output [31:0]out);
reg [15:0] a[n-1:0];
reg [15:0] b[n-1:0];
integer i;
always@ (*) begin // convert two long bit-vectors into two arrays
    for (i=0; i<n; i=i+1) begin
        a[i]= in_a[16*i +:16];
        b[i]= in_b[16*i +:16];
    end
end

reg [31:0] tmp[0:n];
always @ (*) begin
    tmp[0] = 0;
    for (i=0; i<=n-1; i=i+1) tmp[i+1] = a[i]*b[i] + tmp[i];
end
assign out = tmp[n];
endmodule
```

Structural-Level (Gate-Level) Modeling

Components of a Verilog Module

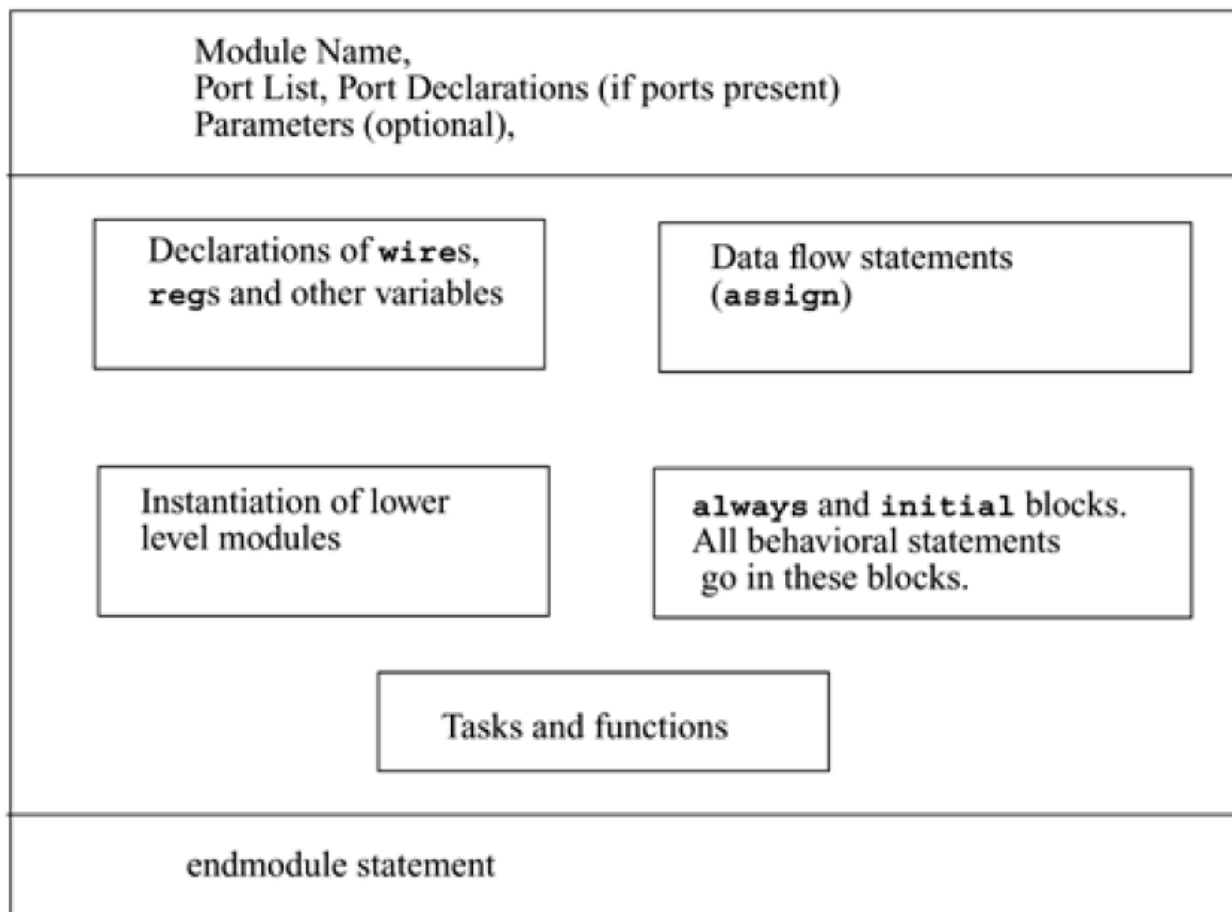- declaration
 - inputs, outputs
 - parameters
 - data types
- **structure** model
- module instantiation
- **dataflow** model
 - continuous assignment
- **behavior** model
 - procedural assignment



```
module M (P1, P2, P3, P4);
input P1, P2;
output [7:0] P3;
inout P4;
```

```
reg [7:0] R1, M1[0:1023];
wire W1, W2, W3, W4;
wire [3:0] W5;
parameter C1=const;
```

```
// non-synthesizable coding
// used in testbench
initial
begin : blockname
    // statements
end
```

```
// behavioral modeling
always
begin
    // statements
end
```


```
// dataflow: continuous assignment
assign W1 = expr ; // use operators
```

```
// module instances: structural modeling
COMP U1 (.PP2(W2), .PP1(W1);
COMP U2 (W3, W4);
```

```
task T1;
input A1, A2;
output A3, A4;
begin
    // statements
end
endtask
```

```
function [7:0] F1;
input A1;
begin
    // statements
end
endfunction

endmodule
```

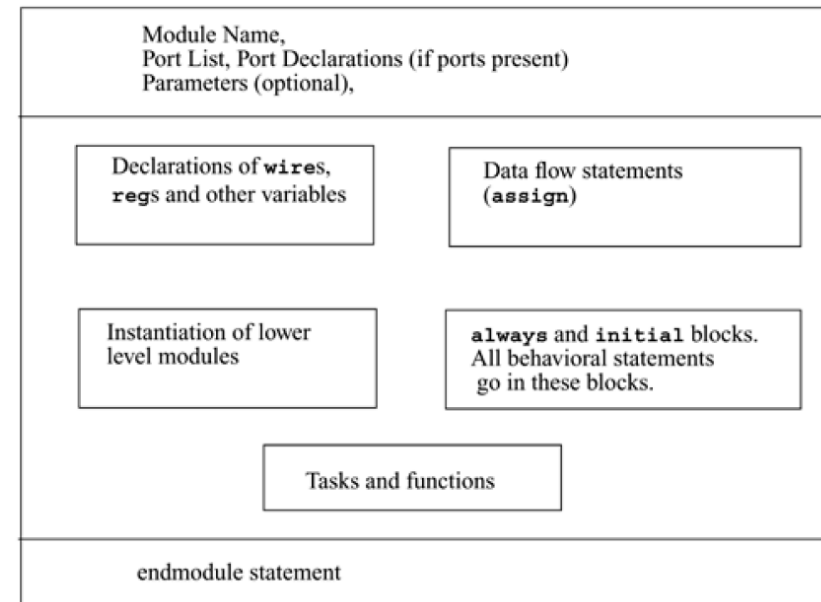

Verilog predefined (built-in) gates

- basic logic gate as predefined (built-in) gate primitives

- **and, or, nand, not, xor, xnor**


- ✓ eg., **and** a1(out, in1, in2);

- **buff, not**

- ✓ eg., **buff** b1(out1, in1);

- **bufif1, bufif0, notif1, notif0** // tristate buffers/inverters

- ✓ eg., **bufif1** b1(out, in, ctrl);

 

- array of instances

```
wire [7:0] out, in1, in2;
```

```
nand n_gate [7:0] (out, in1, in2);
```

```
/* equivalent to following 8 instances
```


```
nand n_gate0 (out[0], in1[0], in2[0];
```

```
nand n_gate1 (out[1], in1[1], in2[1];
```

```
...
```

```
nand n_gate7 (out[7], in1[7], in2[7]; */
```

4:1 Multiplexer (MUX4)

 

// structural level modeling of MUX

module mux4_to_1

(out, i0, i1, i2, i3, s1, s0);

output out;

input i0, i1, i2, i3, s0, s1;

wire s1n, s0n, y0, y1, y2, y3;

not (s1n, s1);

not (s0n, s0);

and (y0, i0, s1n, s0n);


and (y1, i1, s1n, s0);

and (y2, i2, s1, s0n);

and (y3, i3, s1, s0);

or (out, y0, y1, y2, y3);

endmodule

 

s1	s0	out
0	0	I0
0	1	I1
1	0	I2
1	1	I3

// behavioral level modeling of MUX

module mux4_to_1

(output reg out, input i0, i1, i2, i3, s1, s0);

// output wire out, **assign** out = s1 ? (s0 ? I3 : I2) : (s0 ? I1 : I0);

//

always @ (i0, i1, i2, i3, s0, s1) // sensitivity list

begin

case ({s1, s0})

2'b00: out = i0;

2'b01: out = i1;

2'b10: out = i2;

2'b11: out = i3;

default: \$display("invalid control signals");

endcase

end

endmodule


1-bit Full Adder

// *structural (gate)* level modeling

```
module fulladd(sum, c_out, a, b, c_in);  
output sum, c_out;  
input a, b, c_in;  
wire s1, c1, c2;
```

```
    xor (s1, a, b); // assign s1=a^b;  
    and (c1, a, b); // assign c1=a&b;  
    xor (sum, s1, c_in);  
    and (c2, s1, c_in)  
    xor (c_out, c2, c1);
```

```
endmodule
```

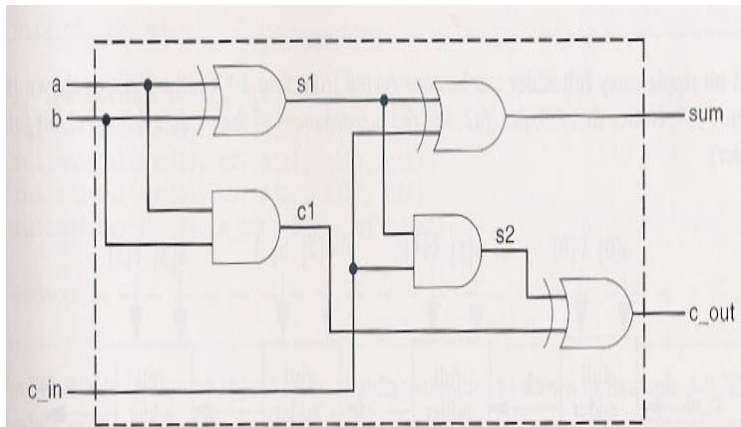

// *dataflow* modeling, continuous assignment

```
module fulladd (sum, c_out, a, b, c_in);  
output sum, c_out;  
input a, b, c_in;
```

```
    assign {c_out, sum} = a + b + c_in;  
    // synthesized gate netlist depends on  
    // area/delay constraints from users
```

```
endmodule
```

// *behavioral* level modeling

```
module fulladd (sum, c_out, a, b, c_in);  
output reg sum, c_out;  
input a, b, c_in;
```

```
    always @ (a or b or c_in)  
        {c_out, sum} = a + b + c_in;
```

```
endmodule
```

4-bit Ripple Carry Adder (RCA)


```
// structural level modeling
module fulladd4 (sum, c_out, a, b, c_in);

output [3:0] sum;
output c_out;
input [3:0] a, b;
input c_in

wire c1, c2, c3;
// construct 4-bit adder fulladd4 from
// previously defined module fulladd

    fulladd fa0 (sum[0], c1, a[0], b[0], c_in);
    fulladd fa1 (sum[1], c2, a[1], b[1], c1);
    fulladd fa2 (sum[2], c3, a[2], b[2], c2);
    fulladd fa3 (sum[3], c_out, a[3], b[3], c3);

endmodule
```

 

```
// dataflow level modeling
// using continuous assignment
module FA_dataflow
    (output [3:0] sum,
     output c_out,
     input [3:0] a, b,
     input c_in);

    assign {c_out, sum} = a+b+c_in;
// synthesized gate netlist depends on
// area/delay constraints from users

endmodule
```

```
// behavioral level modeling
module FA_behavior
    (output reg [3:0] sum,
     output reg c_out,
     input [3:0] a, b,
     input c_in);

    always @(a, b, c_in)
        {c_out, sum} = a+b+c_in;

endmodule
```

Stimulus for 4-bit RCA

```
module stimulus;
reg [3:0] A, B;
reg C_IN;
wire [3:0] SUM;
wire C_OUT;

fulladd4 FA1_4(SUM, C_OUT, A, B, C_IN);    // module instance of the hardware

initial
begin
$monitor ($time, "A=%b, B=%b, C_IN=%b, C_OUT=%b, SUM=%b", A, B, C_IN, C_OUT, SUM);
end

initial
begin
A = 4'd0; B=4'd0; C_IN=1'b0;
#5 A=4'd3; B=4'd4;
#5 A=4'd2; B=4'd5;
#5 A=4'd9; B=4'd9;
#5 A=4'd10; B=4'd15;
#5 A=4'd10; B=4'd5; C_IN=1'b1;
end
endmodule
```

RCA with **generate** loop

- use **generate** loop to duplicate module instances
 - e.g. in FA-cascaded RCA
- or simple
 - **array of instances**

```
// structural level modeling
module RCA (sum, c_out, a, b, c_in);

    output [3:0] sum;
    output c_out;
    input [3:0] a, b;
    input c_in;

    wire c1, c2, c3;

    // construct 4-bit adder fulladd4 from
    // previously defined module fulladd

    fulladd fa0 (sum[0], c1, a[0], b[0], c_in);
    fulladd fa1 (sum[1], c2, a[1], b[1], c1);
    fulladd fa2 (sum[2], c3, a[2], b[2], c2);
    fulladd fa3 (sum[3], c_out, a[3], b[3], c3);

endmodule
```

```
module RCA_generate (sum, c_out, a, b, c_in);
    parameter N=4;
    output [N-1:0] sum;
    output c_out;
    input [N-1:0] a, b;
    input c_in;
    wire [N:0] c;

    assign c[0]=c_in;

    genvar i;
    generate
        for (i=0; i<=N-1; i=i+1)
            begin: FA_loop // block named "FA_loop"
                fulladd fa (sum[i], c[i+1], a[i], b[i], c[i]);
                // fulladd FA_loop[0].fa ( sum[0], c[1], a[0], b[0], c[0] );
                // fulladd FA_loop[1].fa ( sum[1], c[2], a[1], b[1], c[1] );
                // fulladd FA_loop[2].fa ( sum[2], c[3], a[2], b[2], c[2] );
                // fulladd FA_loop[3].fa ( sum[3], c[4], a[3], b[3], c[3] );
            end
    endgenerate

    // fulladd FA_loop[0:3] (sum[0:3], c[1:4], a[0:3], b[0:3], c[0:3]);

    assign c_out = c[N];

endmodule
```

generate blocks

- allow Verilog code to be generated *dynamically* at the elaboration time (before simulation)
 - HDL compiler usually contain two stages: compilation and elaboration
- help the creation of parameterized models
- applications
 - same operation or module instance is repeated
 - ✓ eg., 64-b ripple carry adder (cascaded of 64 FA cells)
 - certain Verilog code is conditionally included based on parameter definitions
 - ✓ e.g., Booth or non-Booth multiplier based on bit-width

generate loop

- allow multiple instantiation, or duplication of statements
- note that **generate** should be used **outside** of procedural blocks (**always**, **initial**)

```
module bitwise_xor(out, i0, i1);
parameter N=32;
output [N-1:0] out;
input [N-1:0] i0, i1;

genvar j; // var. j is local
generate
    for (j=0; j<N; j=j+1)
        begin: xor_loop
            xor g(out[j], i0[j], i1[j]);
        end
// hierarchical name referencing:
// xor_loop[0].g, xor_loop[1].g, ...,
endgenerate
// xor xor_loop[0].g(out[0], i0[0], i1[0]);
// xor xor_loop[1].g(out[1], i0[1], i1[1]);
...
// xor xor_loop[31].g(out[31], i0[31], i1[31]);
endmodule
```

```
// alternate style (behavioral level)
reg [N-1:0] out;

genvar j;
generate
    for (j=0; j<N; j=j+1)
        begin: bit
            always @(i0[j] or i1[j]) out[j] = i0[j] ^ i1[j];
        end
// always @(i0[0], i1[0]) out[0]=i0[0]^i1[0];
// always @(i0[1], i1[1]) out[1]=i0[1]^i1[1];
...
// always @(i0[31], i1[31]) out[31]=i0[31]^i1[31];
endgenerate
```


Discussion of **generate** loop block

- before simulation, simulator elaborates (unrolls) the code in the generate loop blocks
- then, the unrolled code is simulated
 - a convenient way of replacing multiple repetitive Verilog statements with a single statement inside a loop
- **genvar** is to declare local variables used in the generate block, do not exist in simulation
- hierarchical name referencing:
xor_loop[0].g, xor_loop[1].g, ..., xor_loop[31].g

generated ripple carry adder

```

module ripple_adder(co, sum, a0, a1, ci);
parameter N=4;
output [N-1:0] sum;
output co;
input [N-1:0] a0, a1;
input ci;
wire [N:0] carry;

```

```

assign carry[0]=ci;

```

```

genvar i;
generate

```

```

    for (i=0; i<N; i=i+1)
    begin: r_loop

```

```

        wire s1, c1, t3;
        xor g1(s1, a0[i], a1[i]);
        xor g2(sum[i], s1, carry[i]);
        and g3(c1, a0[i], a1[i]);
        and g4(s2, s1, carry[i]);
        xor g5(carry[i+1], c1, s2);

```

```

    end

```

```

endgenerate

```

```


assign co = carry[N]

```

```

endmodule

```

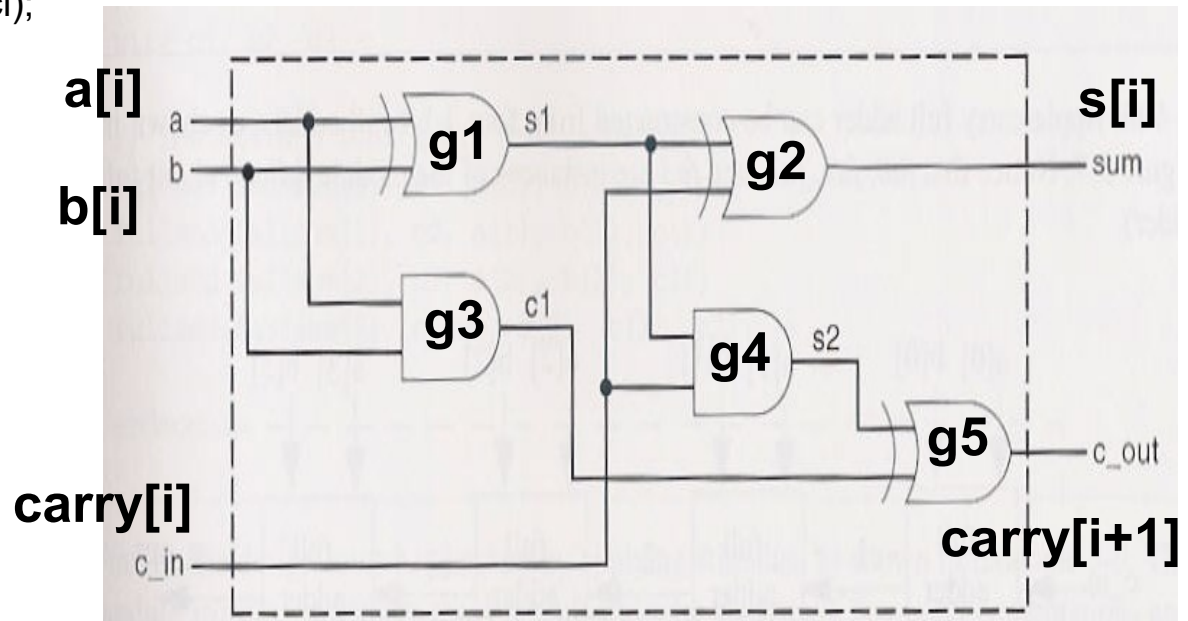




// the following hierarchical instance names are generated

```


// xor r_loop[0].g1(...); xor r_loop[1].g1(...); ...
// xor r_loop[0].g2(...); xor r_loop[1].g2(...); ...
// and r_loop[0].g3(...); and r_loop[1].g3(...); ...
// and r_loop[0].g4(...); and r_loop[1].g4(...); ...
// xor r_loop[0].g5(...); xor r_loop[1].g5(...); ...

```

Example: 4-b Ripple Carry Counter

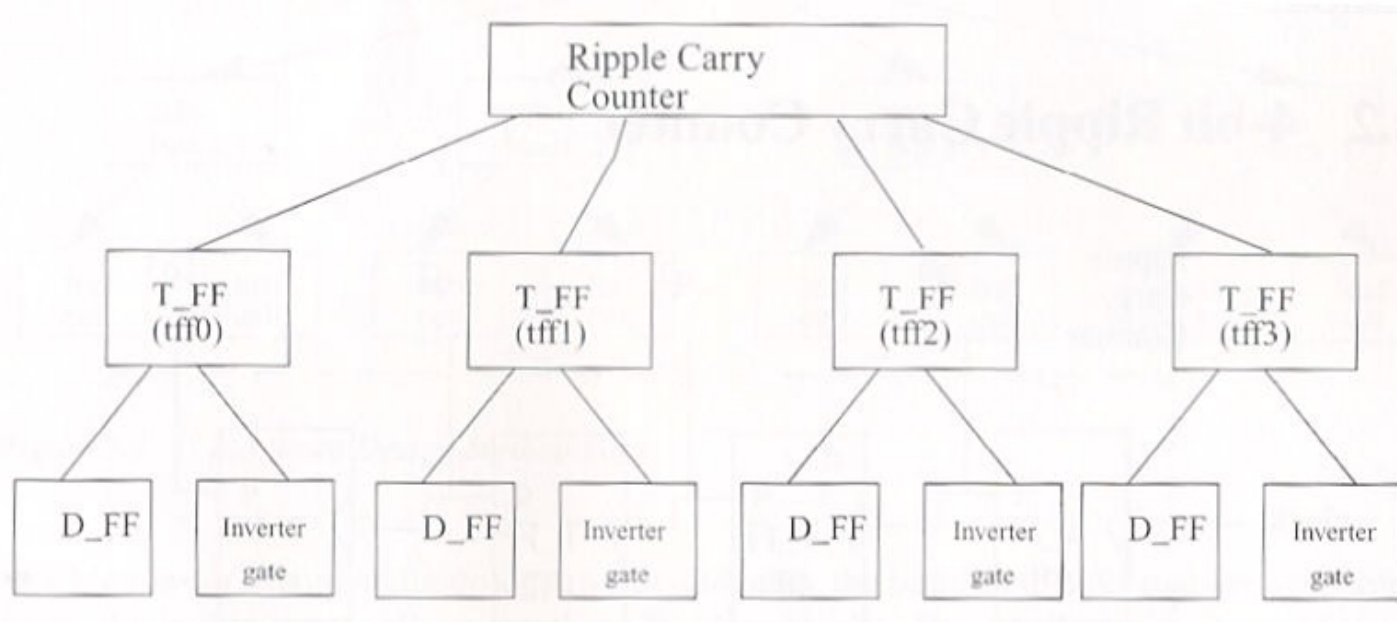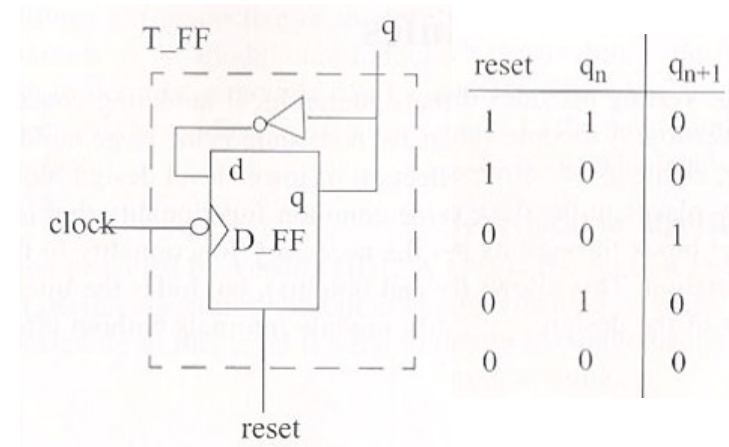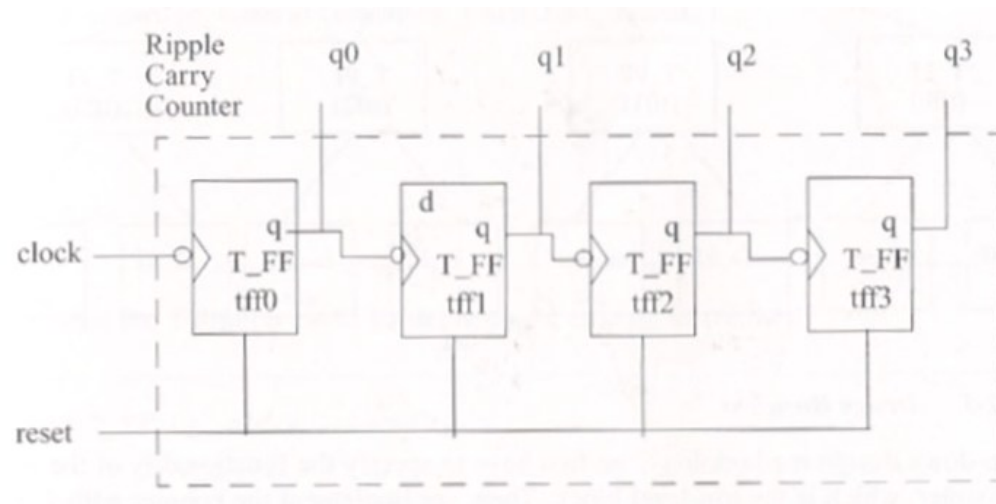

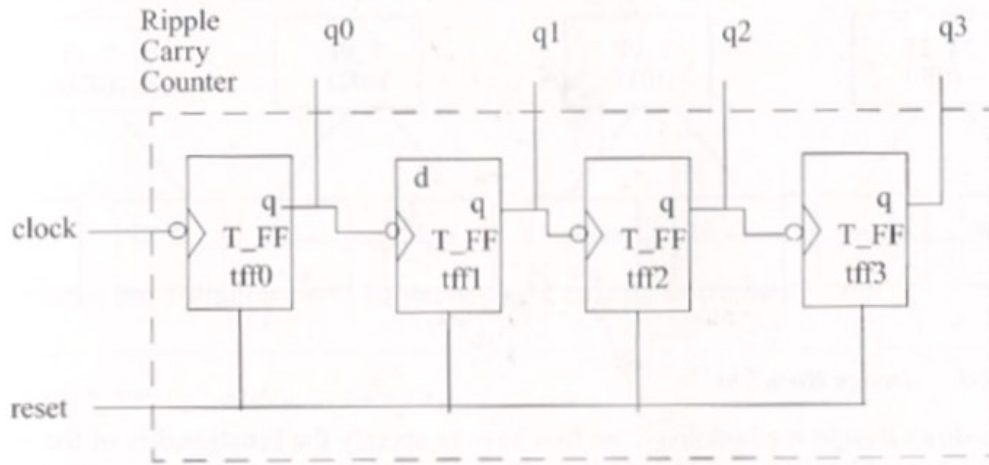Module Instantiation (structural modeling)




```
module ripple_carry_counter (q, clk, rst);
output [3:0] q;
input clk, rst;
```

```
// structural modeling
```

```
T_FF tff0 (q[0], clk, rst);
T_FF tff1 (q[1], q[0], rst);
T_FF tff2 (q[2], q[1], rst);
T_FF tff3 (q[3], q[2], rst);
```

```
endmodule
```

 

```
module T_FF (q, clk, rst);
output q;
input clk, rst;
```

```
wire d;
```

```
// instantiate a D_FF.
```

```
// call it dff0
```

```
D_FF dff0 (q, d, clk, rst);
not n1(d, q);
endmodule
```

structural vs. behavioral modeling

- structural modeling, eg. modules ripple_carry_counter, T_FF
- behavioral modeling, eg. module D_FF

```
module D_FF (q, d, clk, reset);  
output q;  
input d, clk, reset;  
reg q;  
  
// behavioral modeling  
always @(negedge clk or posedge reset)  
    if (reset )    q <= 1'b0;  
    else          q <= d;  
endmodule
```

```
module T_FF (q, clk, rst);  
output q;  
input clk, rst;  
  
wire d;  
  
// instantiate a D_FF.  
// call it dff0  
D_FF dff0 (q, d, clk, rst);  
not n1(d, q);  
endmodule
```

Behavioral Modeling of Generic Counter

- Much simpler than previous structural modeling
 - but structural RCC -> generic counter without explicitly specified structure of the counter

```
module counter_beh (q, clk, rst);  
Output reg [3:0] q;  
input clk, rst;  
  
// behavioral modeling  
always @(negedge clk or posedge reset)  
    if (reset )    q <= 4'b0;  
    else           q <= q+1;  
  
endmodule
```

```
module stimulus;
```

```
reg clk;
```

```
reg rst;
```

```
wire [3:0] q;
```

```
/* instantiate the design block */
```

```
/* positional port mapping */
```

```
ripple_carry_counter r1(q, clk, rst);
```

```
/* generate the input waveform */
```

```
initial clk = 1'b0;
```

```
always #5 clk = ~clk; // clock period=10
```

```
initial
```

```
begin
```

```
    rst = 1'b1;
```

```
    #15 rst = 1'b0;
```

```
    #180 rst = 1'b1;
```

```
    #10 rst = 1'b0;
```

```
    #20 $finish;
```

```
end
```

```
/* display the simulation results */
```

```
initial $monitor ($time, "Output q = %d", q);
```

```
endmodule
```

Simulation Example

```
// non-synthesizable
```

```
// statements are OK
```

```
module testfixture;
```


```
// data type declaration
```

```
// instantiate design block
```

```
// apply stimulus
```

```
// display results
```

```
endmodule
```

 

generate conditional

```
module multiplier (product, a0, a1);  
// 8-bit bus by default,  
// could be changed during instantiation using defparam or #  
parameter a0_width = 8;  
parameter a1_width = 8;  
// the following parameter cannot be modified using defparam  
localparam product_width = a0_width + a1_width;  
  
output [product_width-1:0] product;  
input [a0_width-1:0] a0;  
input [a1_width-1:0] a1;  
  
// instantiate different modules depending on input bitwidth  
generate  
  if (a0_width < 8) || (a1_width < 8)  
    cla_multiplier #(a0_width, a1_width) m0 (product, a0, a1);  
  else  
    tree_multiplier #(a0_width, a1_width) m0 (product, a0, a1);  
endgenerate  
  
endmodule
```

```
module top ( ....);  
...  
multiplier #(4,4) m1 (out1, a, b);  
// cla_multiplier #(4,4) m1 (out1, a, b);  
...  
multiplier #(16, 16) m2 (out2, c, d);  
// tree_multiplier #(16,16) m2 (out2, c, d);  
...  
multiplier #(4, 16) m3 (out3, e, f);  
// cla_multiplier #(4,16) m3 (out3, e, f);  
...  
endmodule
```


generate case

```
module adder (co, sum, a0, a1, ci);

parameter N=4;

output [N-1:0] sum;
output co;
input [N-1:0] a0, a1;
input ci;

// instantiate different modules depending on input bitwidth
generate
    case (N)
        1 : adder_1bit    adder1(co, sum, a0, a1, ci);
        2 : adder_2bit    adder2(co, sum, a0, a1, ci);
        default : adder_cla #(N) adder3(co, sum, a0, a1, ci);
    endcase
endgenerate


endmodule
```

```
module top ( ....);
...
adder #(1) add1 (co1, s1, a1, b1);
// adder_1bit add1 (co1, s1,, a1, b1);
...
adder #(2) add2 (co2, s2, a2, b2);
// adder_2bit add2 (co2, s2, a2, b2);
...
adder #(8) add3 (co3, s3, a3, b3);
// adder_cla add3 (co3, s3, a3, b3);
...
adder #(32) add4 (co4, s4, a4, b4);
// adder_cla #(32) add4 (co4, s4, a4, b4);
.....
endmodule
```

Gate Delays

- rise delay (t_{pdH})
 - output transition to 1
- fall delay (t_{pdL})
 - output transition to 0
- turn-off delay
 - output transition to z
- for simulation only
- gate delay will be ignored after logic synthesis
 - real timing delay depends on the hardware components from real standard cell library of a specified process technology during synthesis
 
```
and #(5) a1(out, i1, i2);  
// delay of 5 time units for all  
// transitions  
  
and #(4, 6) a2(out, i1, i2);  
// rise delay =4, fall delay=6  
  
bufif0 #(3,4,5) b1(out, in, cntl);  
// rise=3, fall=4, turn-off=5
```



Rise time: shape of a single waveform
Rise delay (propagation L→H delay):
Input to output delay

min/typ/max delays



```
// with Verilog-XL option +mindelays, delay=4  
// with Verilog-XL option +typdelays, delay=5  
// with Verilog-XL option +maxdelays, delay=6  
and #(4:5:6) a1(out, i1, i2);
```

```
// if +mindelays, rise=3, fall=5, turn-off=min(3,5)  
// if +typdelays, rise=4, fall=6, turn-off=min(4,6)  
// if +maxdelays, rise=5, fall=7, turn-off=min(5,7)  
and #(3:4:5, 5:6:7) a2(out, i1, i2);
```

```
// in fact, #() overwrite default parameters originally defined  
// in a module during module instantiation
```

Delay Example
 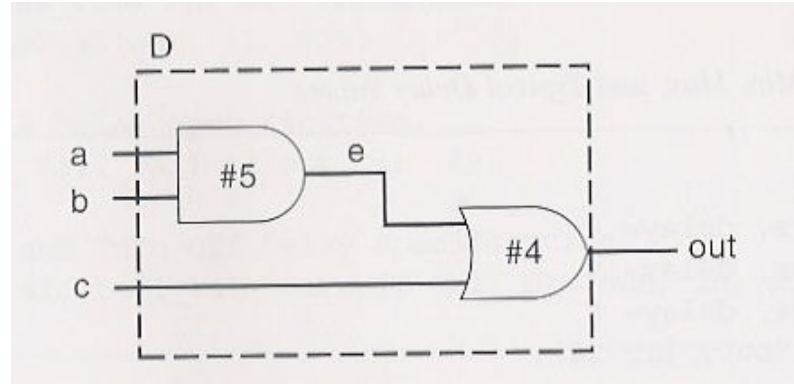
```
module D (out, a, b, c);  
  output out;  
  input a, b, c;  
  wire e;  
  and #(5) a1(e, a, b);  
  or #(4) o1(out, e, c);  
endmodule
```



Timing Analysis Tools


- Static timing analysis (STA)
 - Generate critical path delay without providing inputs
 - e.g., Synopsys Design
 - Might have false path delay which does not exist for any input combination
 - Can also generate power information, but not accurate for clock gating circuits
- Dynamic timing analysis
 - Generate the longest delay based on a sequence of user-specified inputs
 - e.g., Synopsys PrimeTime
 - Might not extract the critical path delay if the provided input changes does not activate the critical path
 - Could also generate power information with clock gating ¹²⁵

Dataflow Modeling

(continuous assignment: **assign**)

Components of a Verilog Module

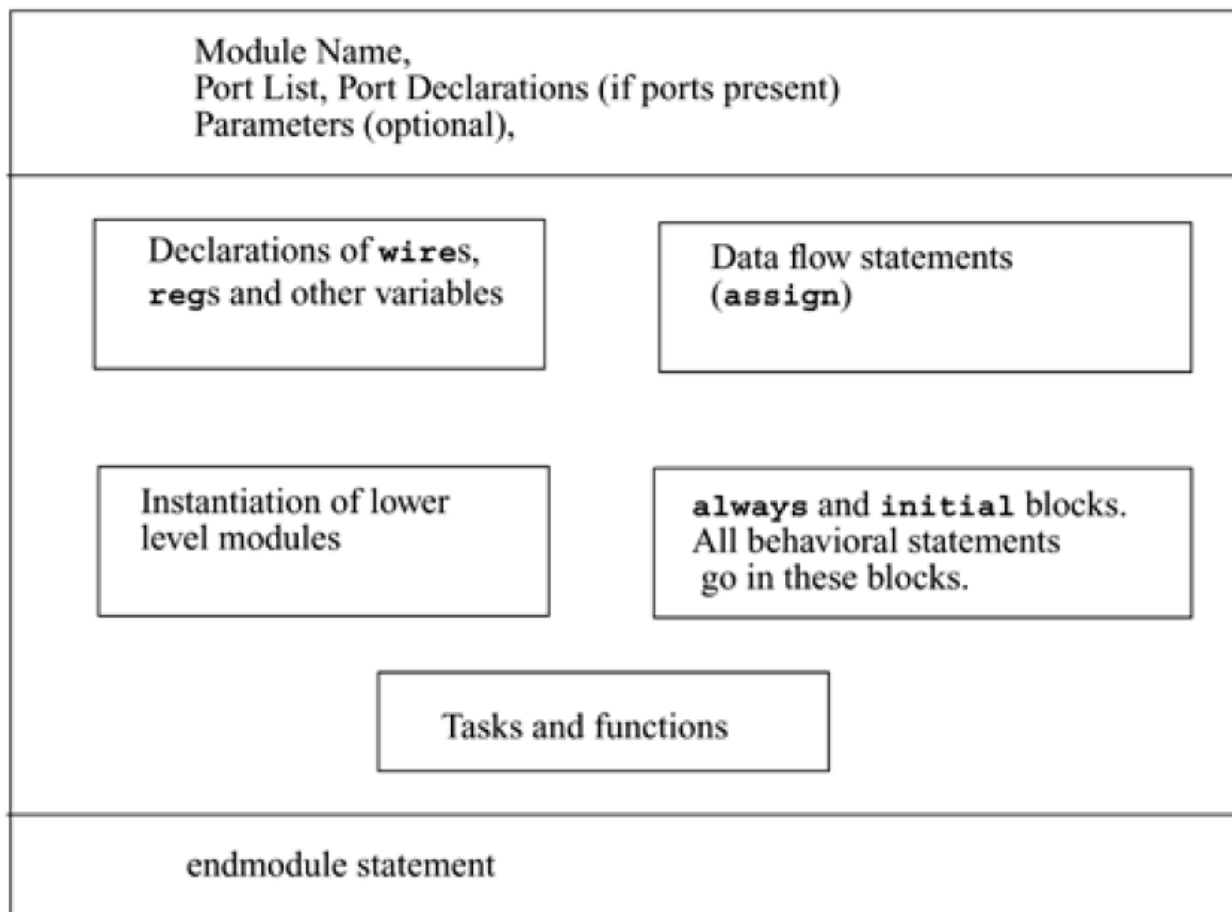- declaration
 - inputs, outputs
 - parameters
 - data types
- **structure** model
- module instantiation
- **dataflow** model
 - continuous assignment
- **behavior** model
 - procedural assignment



```
module M (P1, P2, P3, P4);
input P1, P2;
output [7:0] P3;
inout P4;
```

```
reg [7:0] R1, M1[0:1023];
wire W1, W2, W3, W4;
wire [3:0] W5;
parameter C1=const;
```

```
// non-synthesizable coding
// used in testbench
initial
begin : blockname
    // statements
end
```

```
// behavioral modeling
always
begin
    // statements
end
```


```
// dataflow: continuous assignment
assign W1 = expr ; // use operators
```

```
// module instances: structural modeling
COMP U1 (.PP2(W2), .PP1(W1);
COMP U2 (W3, W4);
```

```
task T1;
input A1, A2;
output A3, A4;
begin
    // statements
end
endtask
```

```
function [7:0] F1;
input A1;
begin
    // statements
end
endfunction

endmodule
```

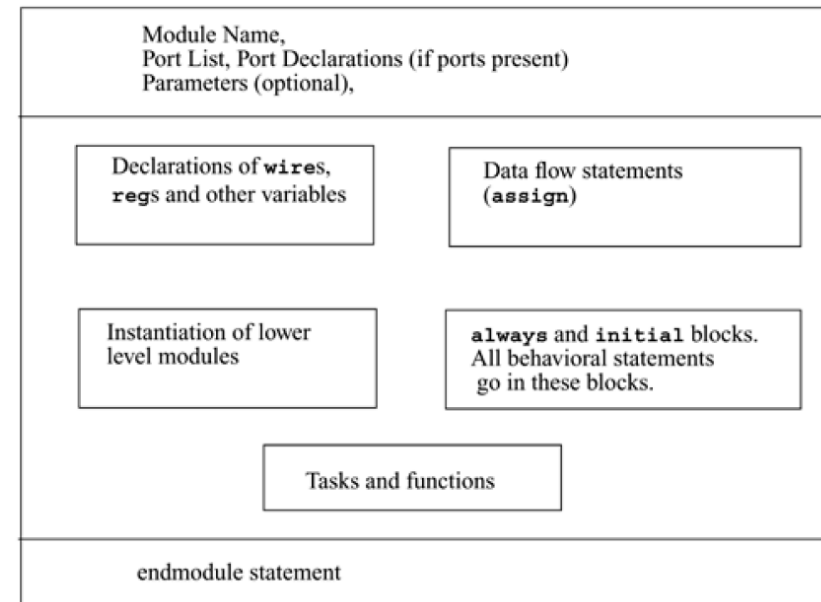

Continuous Assignment (**assign**)

- most basic statement in dataflow modeling
- Continuously drive a value onto a **net (wire)**
 - Compared with *procedural assignment* in a behavioral block (**always**)
- replace gates in the description of circuits at a higher level of abstraction (dataflow model)
 - Describe **combinational logic**

```
wire [31:0] i1, i2, out;  
assign out = i1 | i2; // LHS is wire data type  
// or (out, i1, i2)
```

```
// operator | denotes bitwise OR operation  
// out must be a net (wire)
```

Continuous Assignment (**assign**)

```
assign out = i1 & i2;    // out is a net; i1 and i2 are nets
```

```
assign addr[15:0] = addr1_bits[15:0] ^ addr2_bits[15:0];  
// addr is a vector net; addr1 and addr2 are vector registers
```

```
assign {c_out, sum[3:0]} = a[3:0] + b[3:0] + c_in;  
// left-hand side (LHS) is a concatenation of a scalar net and a vector net  
// {c_out, sum[3:0]} is equal to c_out & sum(3 downto 0) in VHDL
```

- *the left-hand side (LHS) must always be scalar or vector net (**wire**) (cannot be **reg**)*
- *evaluated as soon as the right-hand-side (RHS) operands changes (unlike the behavioral procedural assignments where the statements in a procedure are executed depending on the sensitivity list)*
- *expressions combine operators and operands*

Implicit Continuous Assignments

- // regular continuous assignment
wire out; // wire is default data type
assign out = in1 & in2;\
- // implicit continuous assignment
wire out = in1 & in2; // no keyword **assign**
- // implicit net declaration
wire in1, in2;
assign #10 out = in1 & in2;
// implicit net declaration of out as **wire**
// wait for 10 time units (#10, delay control), then
// sample values of in1, in2, calculate in1&in2,
// and assign to out

Operator Types

- arithmetic (+, -)
- logical (!, &&, ||)
- relational (>, <)
- equality (==, ===, !=, !==)
- bitwise (~, &, |, ^)
- reduction (&, ~&)
- shift (<<, <<<, >>, >>>)
- concatenation ({ })
- conditional (? :)

Operator Type	Operator Symbol	Operation Performed	Number of Operands
Arithmetic	*	multiply	two
	/	divide	two
	+	add	two
	-	subtract	two
	%	modulus	two
	**	power (exponent)	two
Logical	!	logical negation	one
	&&	logical and	two
		logical or	two
Relational	>	greater than	two
	<	less than	two
	>=	greater than or equal	two
	<=	less than or equal	two
Equality	==	equality	two
	!=	inequality	two
	===	case equality	two
	!==	case inequality	two
Bitwise	~	bitwise negation	one
	&	bitwise and	two
		bitwise or	two
	^	bitwise xor	two
	^~ or ~^	bitwise xnor	two
Reduction	&	reduction and	one
	~&	reduction nand	one
		reduction or	one
	~	reduction nor	one
	^	reduction xor	one
	^~ or ~^	reduction xnor	one

Shift	>>	Right shift	Two
	<<	Left shift	Two
	>>>	Arithmetic right shift	Two
	<<<	Arithmetic left shift	Two
Concatenation	{ }	Concatenation	Any number
Replication	{ { } }	Replication	Any number
Conditional	? :	Conditional	Three

Examples of operators

- if A=4'b0011; B=4'b0000
- A + B; // adding A and B equals 4'b1100
- A && B; // evaluate to false (0) because A=3; B=0 (logical AND)
- A || B; // evaluate to true (1) because A=3; B=0;
- A <= B; // evaluate to false (a logical 0) because A=3; B=0
- A == B; // results in logical 0 because A=3; B=0
- A & B; // bitwise AND operation, result is 4'b0000
- &A; // equivalent to 0&0&1&1. results in 1'b0;
- C = A >> 1; // logical right shift. results in 4'b0001
- C = {A, B}; // concatenation. C=8'b0011_0000
- C = {2{A}}; // replication. C=8'b0011_0011
- assign out = cntl ? in1 : in2; // conditional operator
- ! is logic operator, !A evaluates as false (or 1'b0)
- ~ is bit-wise operator, ~A evaluates as 4'b1100

Case equality operators (**===, !==**)

Non-synthesiable by Synopsys DC)

// A = 4, B=3

// X=4'b1010, Y=4'b1101

// Z=4'b1xxz, M=4'b1xxz, N=1'b1xxx

A == B // results in logical 0

X != Y // results in logical 1

Z === M // results in logical 1 (all bits match, including x and z)

Z === N // results in logical 0 (LSB does not match)

M !== N // results in logical 1

Expression	Description	Possible Logical Value
a == b	a equal to b, result unknown if x or z in a or b	0, 1, x
a != b	a not equal to b, result unknown if x or z in a or b	0, 1, x
a === b	a equal to b, including x and z	0, 1
a !== b	a not equal to b, including x and z	0, 1

Equality Operator: Logical vs. Case

- logical equality operator (**==**)

==	0	1	X	Z
0	1	0	X	X
1	0	1	X	X
X	X	X	X	X
Z	X	X	X	X

- case equality operator (**===**)

===	0	1	X	Z
0	1	0	0	0
1	0	1	0	0
X	0	0	1	0
Z	0	0	0	1

Logical Shift (<<, >>) versus Arithmetic Shift (<<<, >>>)

// Verilog-2001

```
integer data_value,  
        data_value_1995,  
        data_value_2001;  
  
...  
data_value = -9;                // stored as 1111_..._1111_0111  
  
...  
data_value_1995 = data_value >> 3; // stored as 0001_..._1111_1110 > 0  
  
...  
data_value_2001 = data_value >>> 3; // stored as 1111_..._1111_1110 = -2  
                                // repeat sign bit during arithmetic right shift  
  
...  
data_value_1995 = data_value << 3; // stored as 1111_..._1011_1000  
  
...  
data_value_2001 = data_value <<< 3; // stored as 1111_..._1011_1000 = -72  
                                // arithmetic left is equivalent to logical left shift  
                                // but arithmetic left will trigger overflow,  
                                // while logical left shift will not trigger overflow
```

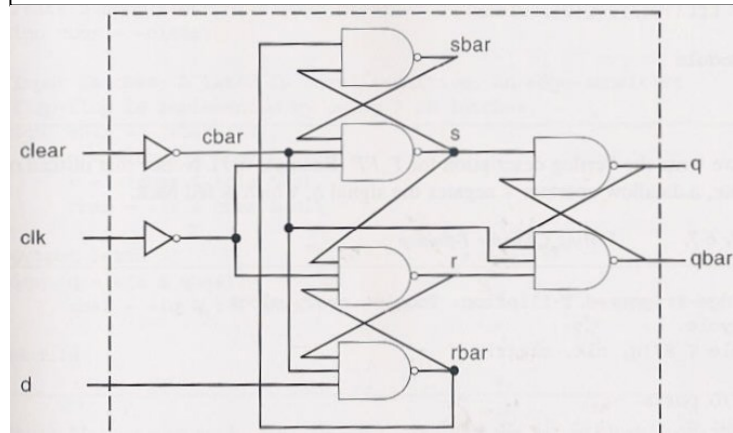

logical left shift vs. arithmetic left shift

- logical left shift is equivalent to arithmetic left shift if sign bit remains unchanged after a shift
 - multiplying positive integral power of 2
- but arithmetic left shift might trigger overflow
 - overflow occurs when the sign bit is changed
 - ✓ e.g., max positive number $0111\dots \lll 1 \Rightarrow 1111\dots$
 - ✓ e.g., mini negative number $1000\dots \lll 1 \Rightarrow 0000\dots$
- while logical left will NOT trigger overflow

behavioral (**always**) vs. dataflow (**assign**)

```
module D_FF (q, qbar, d, clk, clear);  
output q, qbar;  
input d, clk, clear;  
reg q, qbar;  
  
// DFF with asynchronous clear (reset)  
always @ (posedge clear or negedge clk)  
if (clear)  
    begin  
        q <= 1'b0;  
        qbar <= 1'b1;  
    end  
else  
    begin  
        q <= d;  
        qbar <= ~d;  
    end  
endmodule
```

```
module dff (q, qbar, d, clk, clear);  
output q, qbar;  
input d, clk, clear;  
  
// same signals appear in LHS and RHS  
// infer latch with loop in datapath  
assign cbar = ~clear;  
assign sbar = ~(rbar & s),  
        s = ~(sbar & cbar & ~clk),  
        r = ~(rbar & ~clk & s),  
        rbar = ~(r & cbar & d);  
assign q = ~(s & qbar),  
        qbar = ~(q & r & cbar);  
  
endmodule
```



Both **always** and **assign**
belong to RTL coding style

Example (4-to-1 Multiplexer)

```
// using logic equations  
module mux4_logic (out, i0,  
    i1, i2, i3, s1, s0);
```

```
output out;  
input i0, i1, i2, i3, s0, s1;
```

```
assign out =  
(~s1 & ~s0 & i0) |  
(~s1 & s0 & i1) |  
(s1 & ~s0 & i2) |  
(s1 & s0 & i3);
```


```
endmodule
```

```
// using conditional operator  
module mux4_cond (out, i0,  
    i1, i2, i3, s0, s1);
```

```
output out;  
input i0, i1, i2, i3, s0, s1;
```

```
assign out = s1 ?  
( s0 ? i3 : i2) : (s0 ? i1 : i0);
```

```
endmodule
```

 

Example (4-bit adder)

```
// using dataflow
// with proper synthesis constraint

module add4 (sum, c_out, a, b, c_in);
output [3:0] sum;
output c_out;
input [3:0] a, b;
input c_in;

// gate-level structure
// depends on synthesis constraints
assign {c_out, sum} = a + b + c_in;

endmodule
```

$$p_i = \oplus = = +$$

$$c_1 = +$$

$$c_2 = + +$$

$$c_3 = + + +$$

$$c_4 = + + + +$$

$$s_i = \oplus$$

```
// explicit carry lookahead adder using p and g

module add4 (sum, c_out, a, b, c_in);
output [3:0] sum;
output c_out;
input [3:0] a, b;
input c_in;
wire p0, g0, p1, g1, p2, g2, p3, g3;
wire c4, c3, c2, c1;

assign p0=a[0]^b[0], p1=a[1]^b[1], p2=a[2]^b[2],
        p3=a[3]^b[3];
assign g0=a[0]&b[0], g1=a[1]&b[1], g2=a[2]&b[2],
        g3=a[3]&b[3];
assign c1 = g0|(p0&c_in),
        c2=g1|(p1&g0)|(p1&p0&c_in),
        c3=g2|(p2&g1)|(p2&p1&g0)|(p2&p1&p0&c_in),
        c4=g3|(p3&g2)|(p3&p2&g1)|(p3&p2&p1&g0)
            |(p3&p2&p1&p0&c_in);
assign sum[0] = p0 ^ c_in, sum[1] = p1 ^ c1,
        sum[2]=p2 ^ c2, sum[3] = p3 ^ c3;
assign c_out = c4;

endmodule
```

n