

# **HDL HW2:**

## **Pipelined add/subtract and multiplier**

# HDL HW2 Outlines

- multiply-add  $d=a*c+b*c$  vs.  $d=(a+b)*c$
- 2-stage pipelined add/sub multiplier  $d=(a+/-b)*c$ 
  - add/sub in 1<sup>st</sup> stage
  - multiplier in 2<sup>nd</sup> stage
- clock gating to reduce power when  $c=0$ 
  - Prime Time dynamic analysis for power measurement
- RTL and gate-level simulation
  - Synopsys Design Compiler for logic synthesis
  - comparison of power report in static analysis and dynamic analysis with half of input  $c$  are zeros
- FPGA implementation
- Lab slides for EDA tools
  - PrimeTime
  - Xilinx vivado

# Synthesis of $d=a*c+b*c$ vs. $d=(a+b)*c$

- Synthesis results of two different multiply-add under the same constraint
  - check the synthesized circuits of gate-level netlists

```
module multiply_add (input [7:0] a, b, c, output d [15:0] d);  
    assign d=a*c+b*c; // two 8x8 multipliers ; one 16-bit adder  
endmodule
```

```
module multiply_add_common_factor ( input [7:0] a, b, c,  
                                   output [15:0] d );  
    assign d=(a+b)*c; // one 8x8 multiplier; one 16-bit adder  
endmodule
```

# Synthesis of adder/subtractor

- Synthesis results of two different adder/subtractor designs under the same constraint
  - check the synthesized circuits of gate-level netlists

```
module add_sub_1 (input [7:0] a, b, input s, output [15:0] d);  
wire [7:0] tmp;  
assign tmp = s ? b : -b; // one 2-to-1 multiplexer for possible negation of b  
assign d = a + tmp; // an adder  
endmodule
```

```
module add_sub_2 (input [7:0] a, b, input s, output [15:0] d);  
assign d = s ? a+b : a-b; // one adder, one subtractor, one 2-to-1 multiplexer  
endmodule
```

```
module add_sub_3 (input [7:0] a, b, input s, output reg [15:0] d);  
always @(a or b or s) // one adder, one subtractor, one 2-to-1 multiplexer  
    if (s == 1) d = a+b; else d=a-b;  
endmodule
```


# non-pipelined vs. pipelined

- $d=(a+b)*c$  if  $s=1$  and  $d=(a-b)*c$  if  $s=0$
- non-pipelined
  - using either continuous assignment in **assign** with ternary operator **? :**, or
  - using procedural assignments inside **always @(...)** begin ... end
- pipelined
  - 1<sup>st</sup> stage: conditional add/sub
  - 2<sup>nd</sup> stage: multiplier
  - use pipeline registers with asynchronous reset
  - identify the delays  $T_1, T_2$  in 1<sup>st</sup> and 2<sup>nd</sup> pipelined stages
    - ✓ throughput =  $1 / \max(T_1, T_2)$
    - ✓ latency =  $T_1 + T_2$
    - ✓ pipeline can increase throughput, but not latency
- area, delay, power reports from Synopsys DC

```
always @ (posedge clk or posedge rst)
if (rst) q <= 0; else ....
```

 
# clock gating

```
module dff(Q, D, clk);  
input D, clk;  
output Q;  
reg Q;  
wire gclk, en;  
// clock signal is from the output of AND  
// glitch might cause extra clock edges  
assign gclk = clk & en;  
always @(posedge gclk)  
    Q <= D;  
endmodule
```



**gclk might have glitches !!!  
cause unexpected latching**
 
```
module dff(Q, D, clk);  
input D, clk;  
output Q;  
reg Q;  
wire en;  
  
// data input from MUX  
always @(posedge clk)  
if (en) begin  
    Q <= D;  
end  
endmodule
```




**The clk port might still have  
switching power!  
not efficiently reduce dynamic  
power**
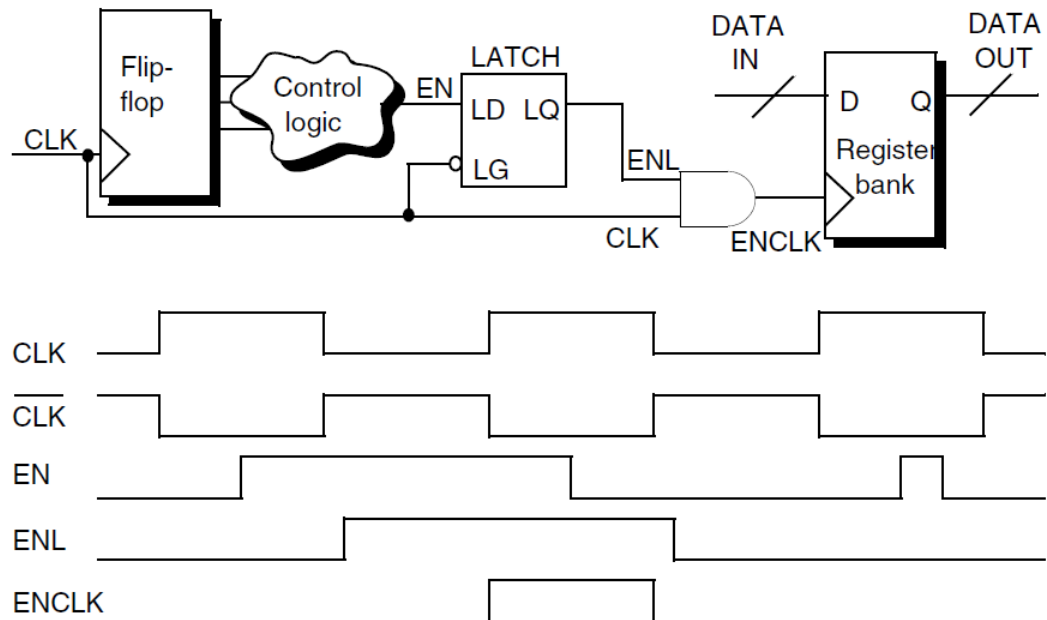
# Latch-based clock gating (Safe Design)


- avoid glitches in clock signals
  - glitches incur unwanted signal edges
- clock-gating signal is en is latched by a latch controlled by  $\sim\text{clk}$  before feeding into the AND gate
  - signal to the input of AND is stable when clk goes high

```
module safe_clock_gated_dff (Q, D, clk);  
input D, clk; output Q;  
reg tmp, Q;  
  
always @ (CLK or EN) // latch  
if (!CLK) tmp = EN;  
assign gclk = tmp1 & CLK; // AND gate  
always @(posedge gclk) // CG FF  
Q <= D;  
endmodule
```


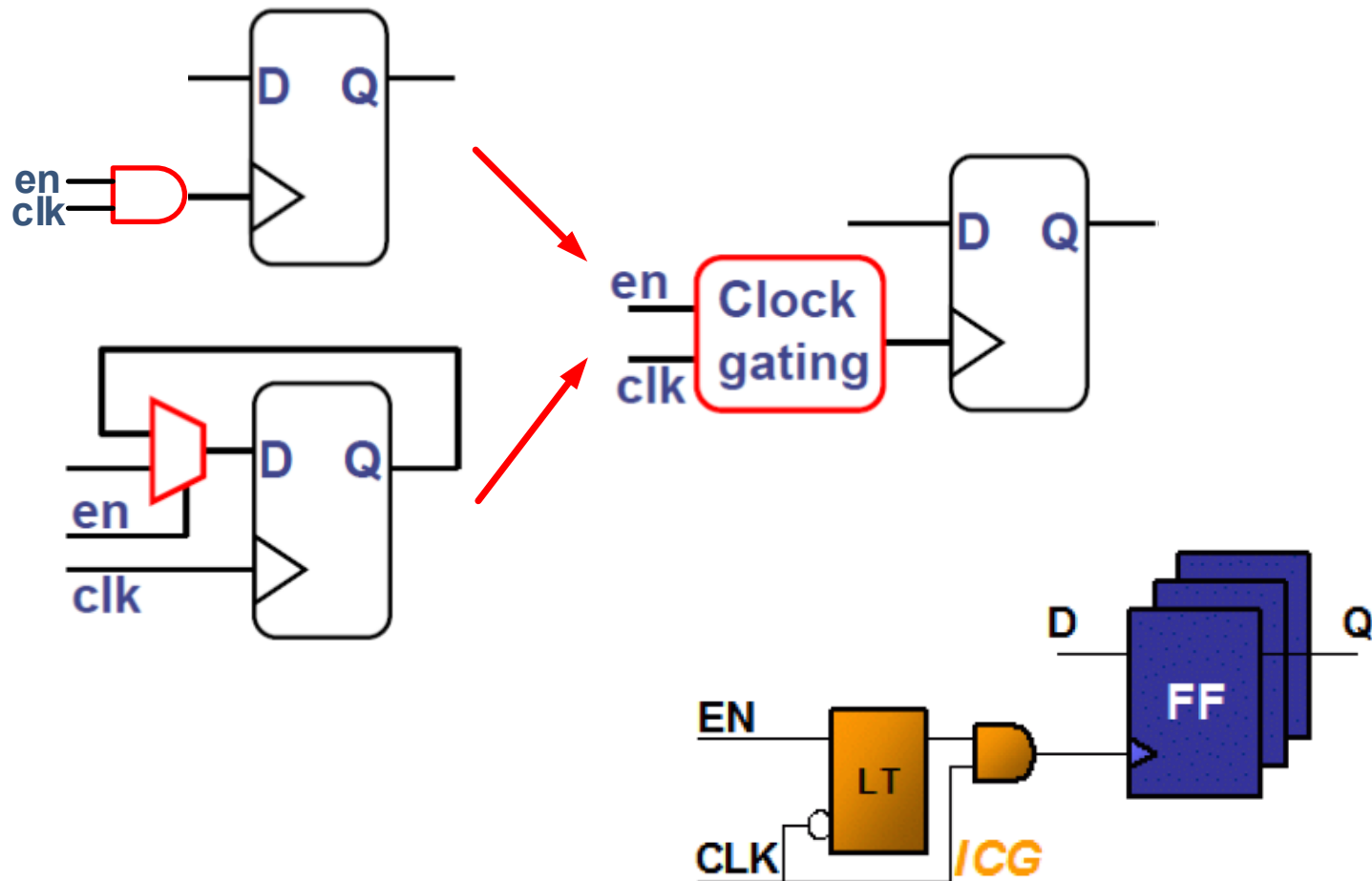
# Synthesized Clock Gating

- When synthesis is done with proper commands
  - Both design leads to safe clock gating circuit (with latch)






# Clock gating methods

- Method 1 (unsafe gclk with possible glitches)


```
assign gclk = clk && enable ;

 always@(posedge gclk or negedge nrst)
begin
    if(!nrst)
        Q <= 8'd0;
    else
        Q <= D ;
end
```



- Method2 (high switching activity of clk )
 
```
always@(posedge clk or negedge nrst)
begin
    if(!nrst)
        Q <= 8'd0;
    else if(enable)
        Q <= D ;
end
```



# Synthesized lock gating with Synopsys

- use Synopsys synthesis script ***set\_clock\_gating\_style*** (or other commands) which automatically find the gated clock signal and generate the safe clock-gating design



```
assign gclk = clk && enable ;

always@(posedge gclk or negedge nrst)
begin
    if(!nrst)
        Q <= 8'd0;
    else
        Q <= D ;
end
```

```
#set clock gating
set_clock_gating_style -sequential_cell latch -minimum_bitwidth 1 -max_fanout 1
propagate_constraints -gate_clock
current_design [get_designs Module_Name]
replace_clock_gates
```

```
always@(posedge clk or negedge nrst)
begin
    if(!nrst)
        Q <= 8'd0;
    else if(enable)
        Q <= D ;
end
```
 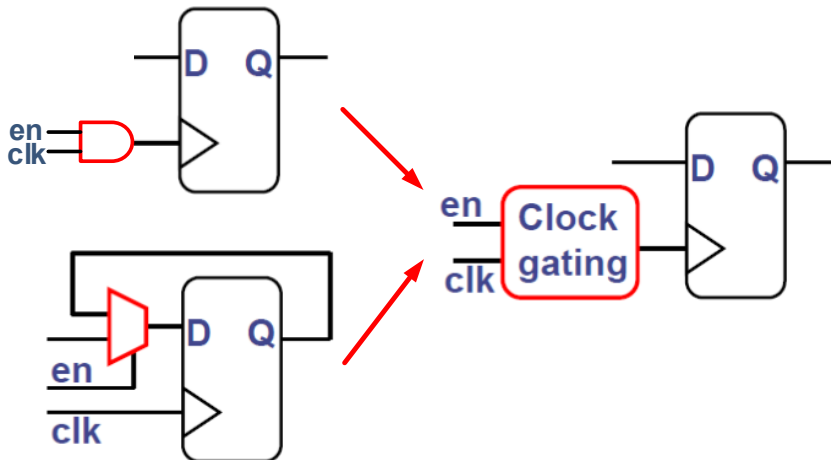
```
#set clock gating
set_clock_gating_style -sequential_cell latch -minimum_bitwidth 1 -max_fanout 1
propagate_constraints -gate_clock
current_design [get_designs Module_Name]
replace_clock_gates
```



# Static vs. Dynamic Analysis

- static timing analysis
  - e.g. reports from Synopsys Design Compiler
  - no need to provide inputs
  - possible false path delay
  - could not measure power due to clock gating at some condition of input signals
- dynamic timing analysis
  - e.g., Synopsys PrimeTime
  - need to provide input test patterns
  - maximum delay among all the provided inputs
  - could measure actual power due to clock gating

# summary table

- synthesis results
  - delay and power from DC and PrimeTime might be different


	Area (um <sup>2</sup> )			Delay (ns)	Latency (ns)	Power (W)		
	CL	SL	Total			dynamic	leakage	total
Non-pipelined (DC)								
Non-pipelined (PrimeTime)								
Pipelined (DC)								
Pipelined (PtimeTime)								
Clock-gated (DC)								
Clock-gated (PrimeTime)								

# FPGA

- Xilinx Vivado synthesis
  - similar to Synopsys DC logic synthesis
  - convert RTL to gate netlists for a selected FPGA chip
- Implementation
  - similar to placement-and-routing in ASIC cell-based design flow
  - map to the selected FPGA
- utilization rate of FPGA resources
  - LUT
  - DSP
  - BRAM
  - I/O
  - ...

 
# Xilinx design flow

- synthesis
- implementation
- programming




# Xilinx Virtex FPGA

- CLB (configurable logic block)

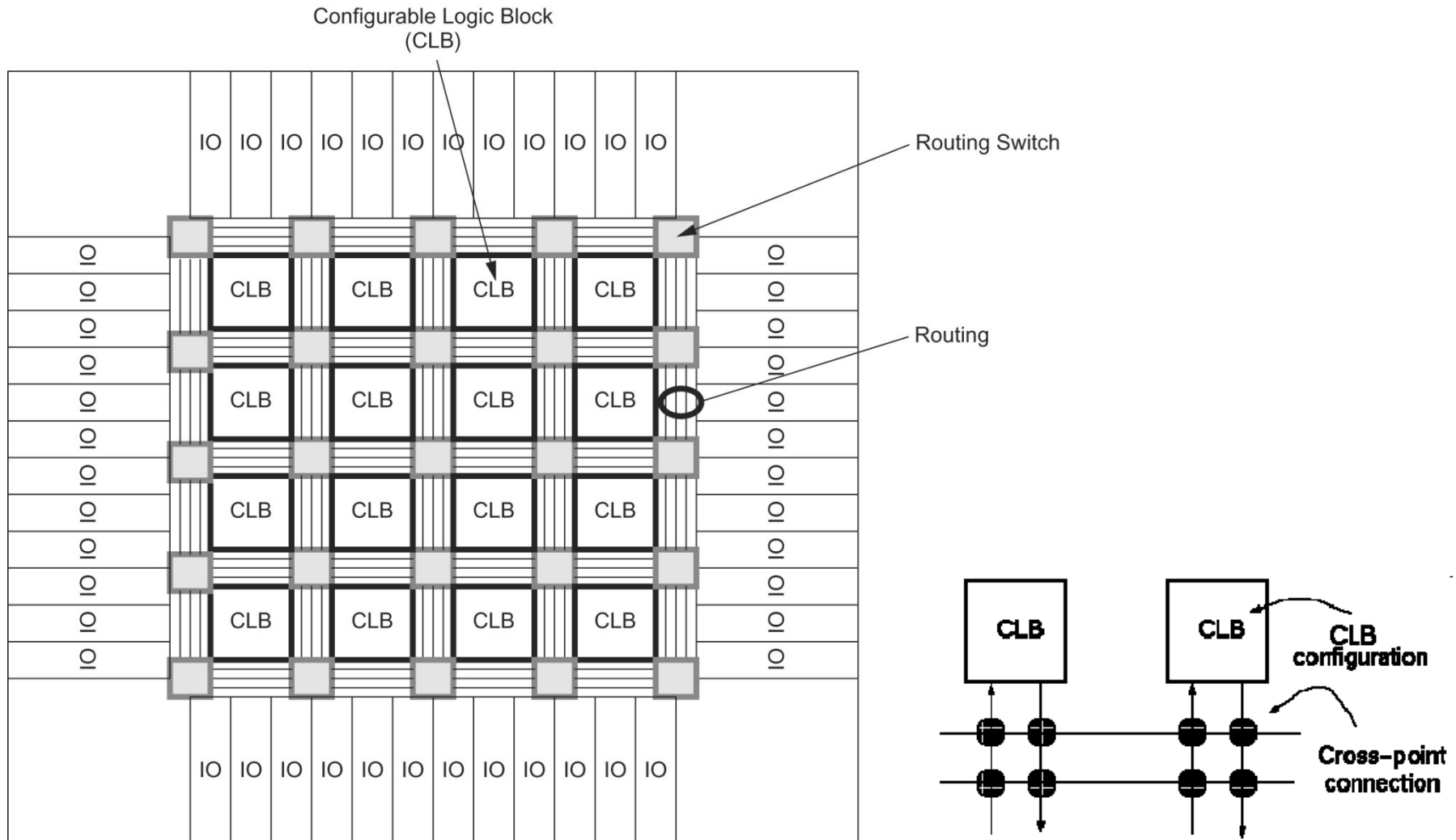
 
# FPGA (early vs. modern)

- early FPGA
  - programmable array logic (PAL)
  - I/O
- modern FPGA
  - CLB, LE, LB, ..
  - I/O
  - block RAM (BRAM)
  - DSP
  - other hard blocks
- all connected by bit-level routing





# FPGA Evaluation Flow

- Similar to cell-based design flow
  - logic synthesis
  - placement and routing
- But FPGA can be implemented on real FPGA chips
  - quick prototyping
  - reconfigurable
  - cell-based needs tape out to foundry and non-reconfigurable
- area in utilization rate of a particular FPGA chip
  - CLB, LE
  - I/O
  - LUT
  - DSP
  - BRAM
  - ...

