

Power Optimization (Clock Gating)

課程：算術處理器設計與實作、硬體描述語言

邱奕綸 chiu91523@gmail.com

大綱

OUTLINE

01

Introduction

02

Manual Methods




章節
Part

01

Introduction

Introduction

Clock Gating 介紹 (1/2)

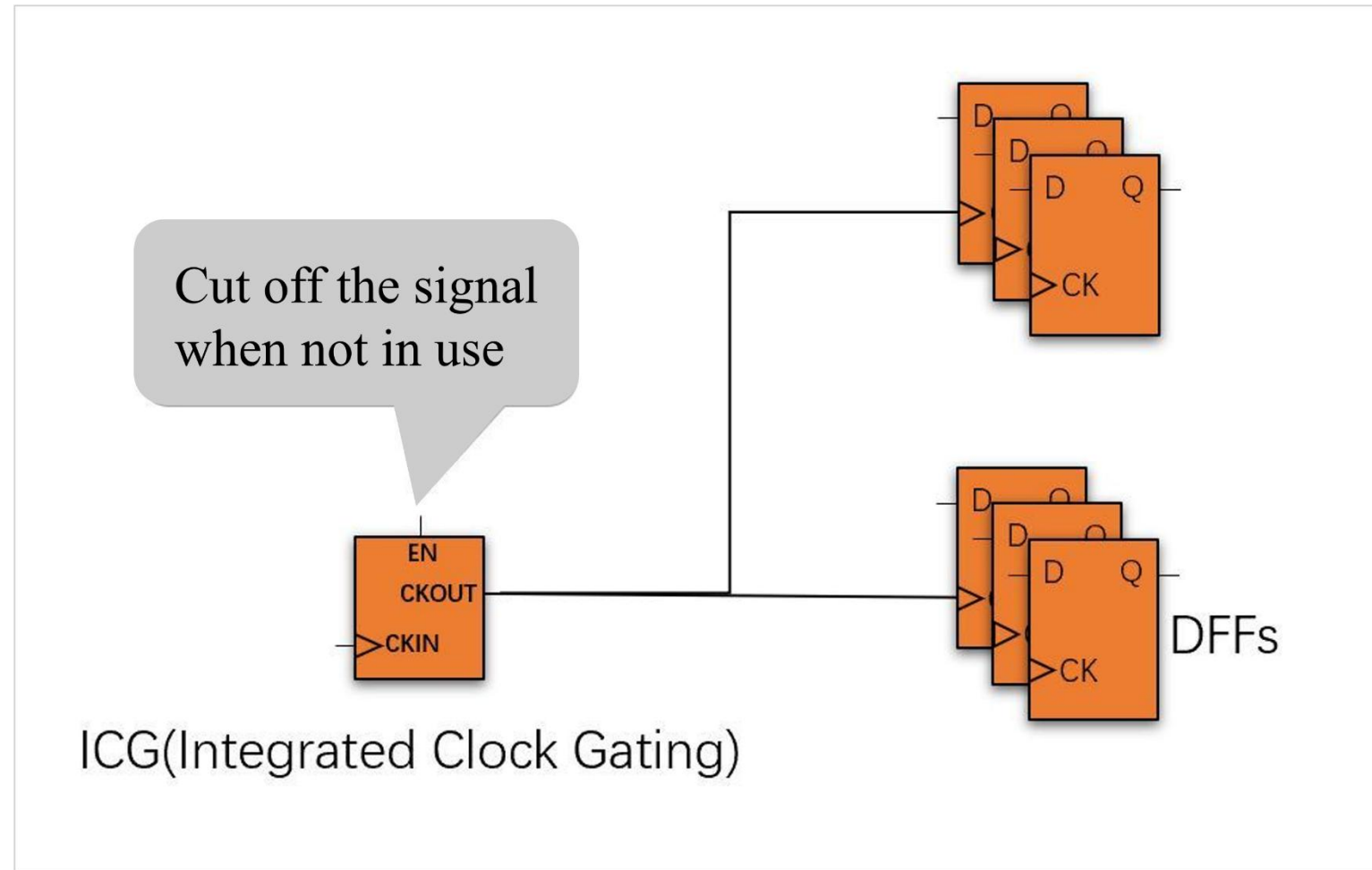


透過Enable訊號來控制各DFF的Clock，不用時將Clock切斷(維持0)，從而減少翻轉訊號(Toggle Rate)，使動態功耗有所下降。

Introduction

Clock Gating 介紹 (2/2)

 
```
// manual clock gating
module dff(Q, D, clk);
input D, clk;
output Q;
reg Q;
wire gclk, en;
// clock signal is from the output of AND
// glitch might cause extra clock edges
assign gclk = clk & en;
always @(posedge gclk)
    Q <= D;
endmodule
```



gclk might have glitches !!!
cause unexpected latching

```
// automatic clock gating
module dff(Q, D, clk);
input D, clk;
output Q;
reg Q;
wire en;

 
// data input from MUX
always @(posedge clk)
    if (en) begin
        Q <= D;
    end
endmodule
```



The clk port might still have switching power!
not efficiently reduce dynamic power

Introduction

Clock Gating (non-latch Version) (1/2)

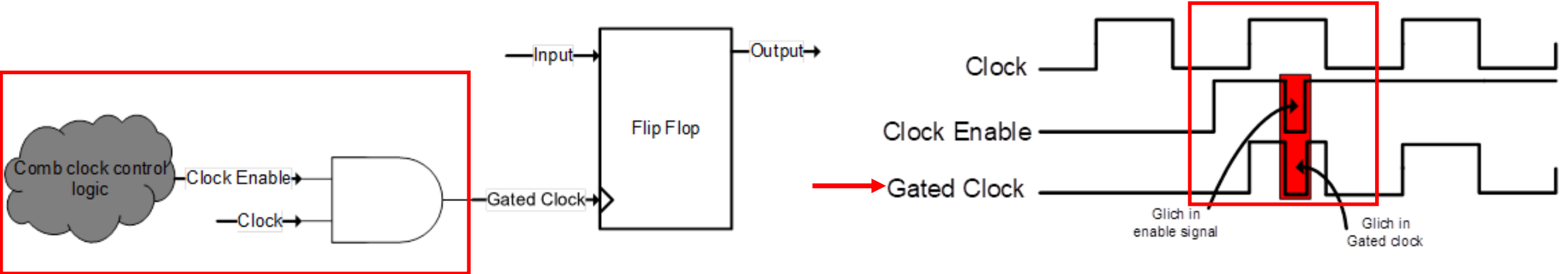


將**Clock Enable**(致能訊號)與**Clock**(時脈訊號)做**AND**並將訊號給予該DFF之Clock端即可達到Gating效果，如果使能訊號為0，Gated Clock將會維持0，該Gated DFF將不會有所動作，從而降低功耗。

如果只有AND去做Gating將會帶來一個問題，EN訊號通常為組合邏輯，因此當EN為1時Clock訊號才有用，如果EN在Clock為高準位時變為邏輯0將會有**Glitch**產生(如上右圖可以看到Gated Clock有**窄波**出現)，造成Data錯誤及功耗上升。

Clock Gating (non-latch Version) Verilog Code Example

 
```
module clock_gated_dff1 (Q, D, clk);  
  input D, clk;  output Q;  
  reg Q;  
  wire gclk, en;  
  
  assign gclk = clk & en;  
  always @(posedge gclk)  
    Q <= D;  
endmodule
```



non-latch Version代表只有 **AND Gate** 而已。

Introduction


Clock Gating (Latch-Based Version) (1/2)

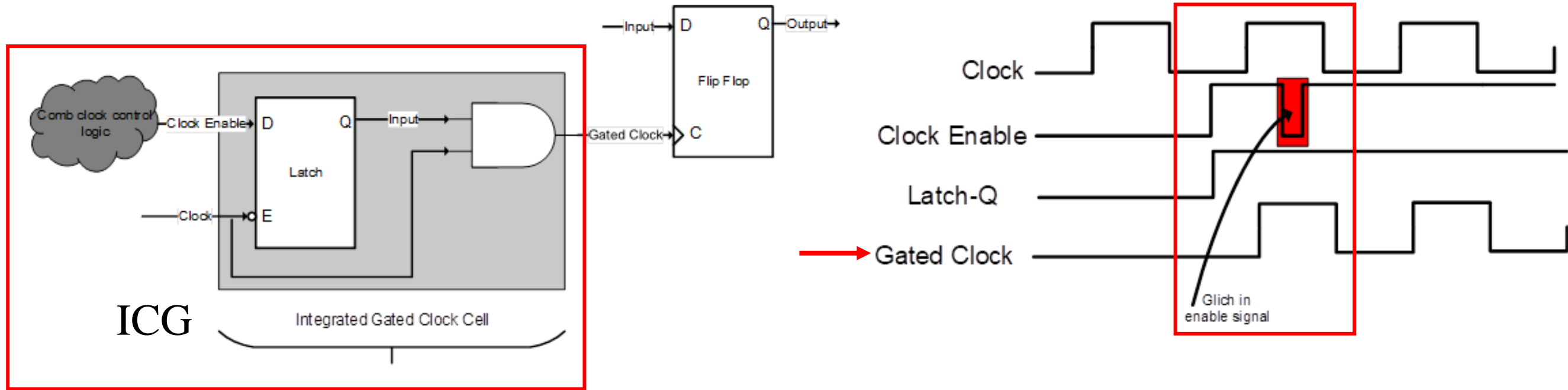

為了解決**Glitch**產生的問題，我們可以在AND Gate前加入**Latch** (Low-level sensitive)即可解決**Glitch**問題，使Gated Clock的波型為正確(無窄波問題產生)。

Clock Gating (Latch-Based Version) Verilog Code Example
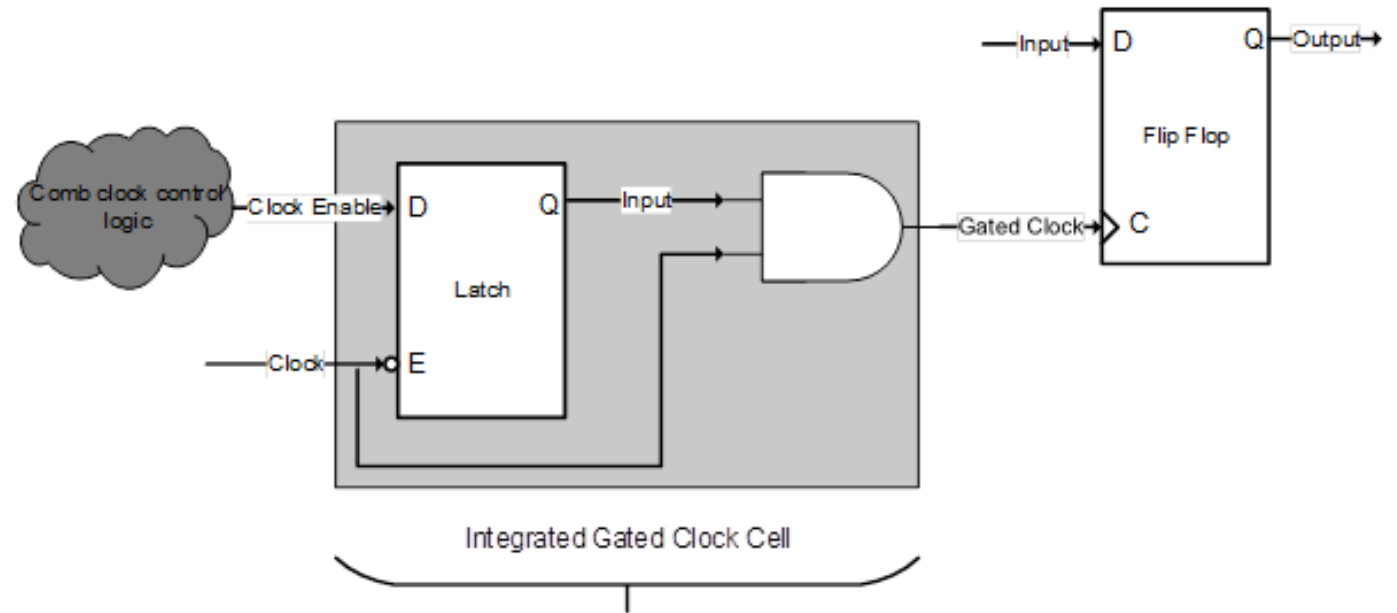
```
module safe_clock_gated_dff (Q, D, clk);  
input D, clk; output Q;  
reg tmp, Q;  
  
always @ (CLK or EN) // latch  
    if (!CLK) tmp = EN;  
assign gclk = tmp1 & CLK; // AND gate  
always @(posedge gclk) // CG FF  
    Q <= D;  
endmodule
```



Latch-Based Version代表有Latch及AND Gate形成之ICG Cell(如上圖)，RTL Code較為冗長，因此後面會教如何透過Tool(Design Compiler)將non-latch Clock Gating自動轉為Latch-Based Clock Gating。



章節
Part

02

Manual Methods

Manual Methods

Manual Clock Gating (1/4)

Method 1 : Auto Clock Gating (not recommend)


盡量不要用這種寫法，因為會產生如右圖上方電路。

RTL (Verilog Code):


```
always@(posedge clk or negedge rst_n) begin
    if(!rst_n) Q <= 0;
    else begin
        if(en) Q <= D;
    end
end
```

Design Compiler (TCL):

```
compile -gate_clock
```

 

by power compiler
Clock Gating

 

如果用以上寫法還是可以透過DC上方指令自動轉換成正確之Clock Gating電路。

Manual Methods

Manual Clock Gating (2/4)


Method 2 : Clock Gating (recommend)

RTL (Verilog Code):

```
assign gclk = clk & en;  
  
always @(posedge gclk or negedge rst_n) begin  
    if (!rst_n) Q <= 0;  
    else Q <= D;  
end
```

Design Compiler (TCL):

```
replace_clock_gates  
compile
```

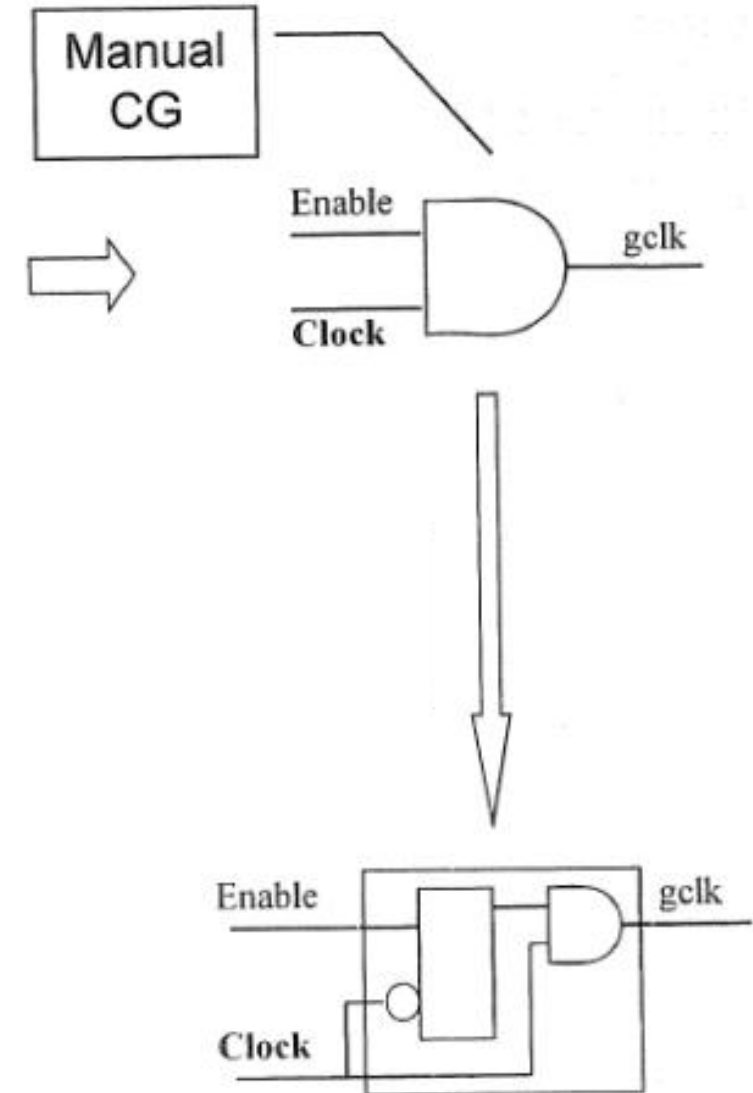

RTL使用(non-latch Version)寫法即可透過Design Compiler轉成Latch-based Clock Gating。

Design Compiler (TCL):

```
report_clock_gating -gating_elements
```

可透過以上指令回報Gating DFF之數量

Clock Gating Summary

Number of Clock gating elements	4
Number of Gated registers	64 (16.98%)
Number of Ungated registers	313 (83.02%)
Total number of registers	377


Manual Methods

Manual Clock Gating (4/4)

Design Compiler (TCL):


```
set_ideal_network [get_ports clk]
```

 透過以上指令可將clock訊號線視為理想狀況 (可忽略High Fanout Synthesis之問題)。




Manual Methods

GUI 介面顯示Clock Gating Cell (Example)

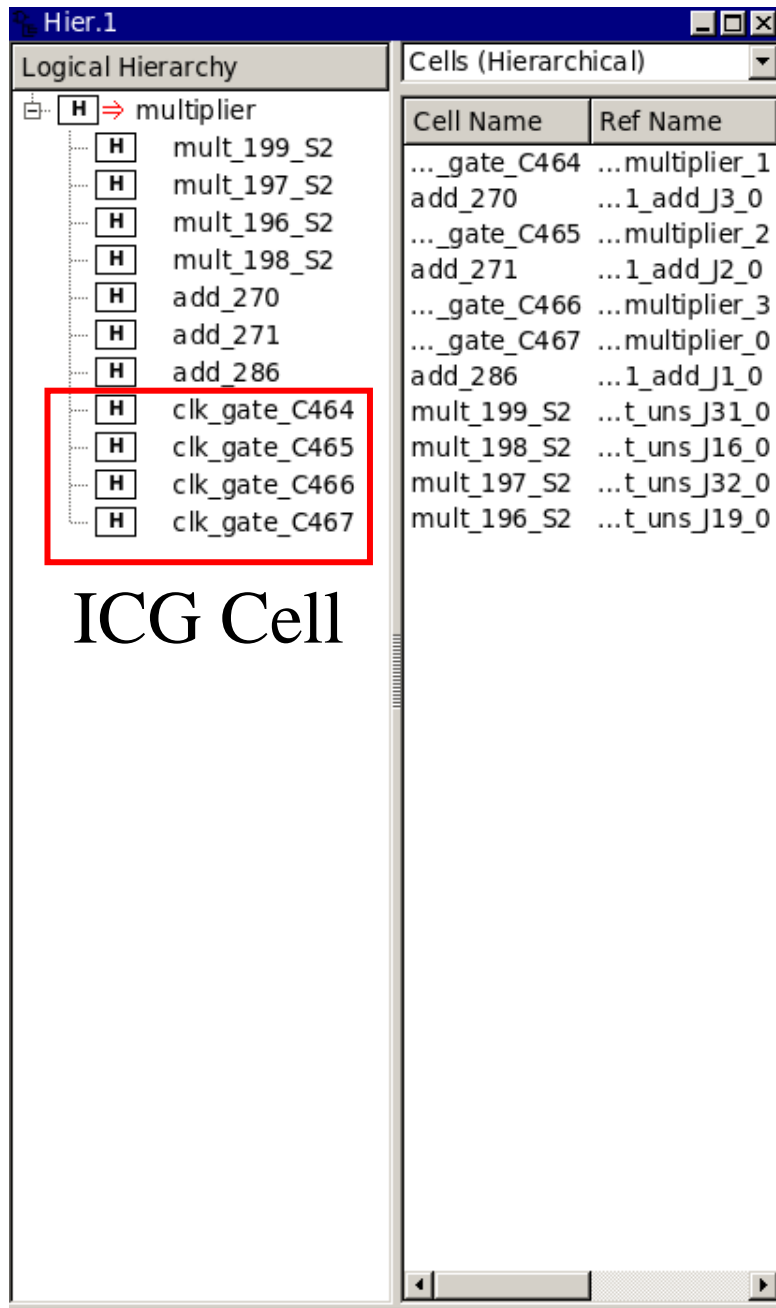

ICG Cell

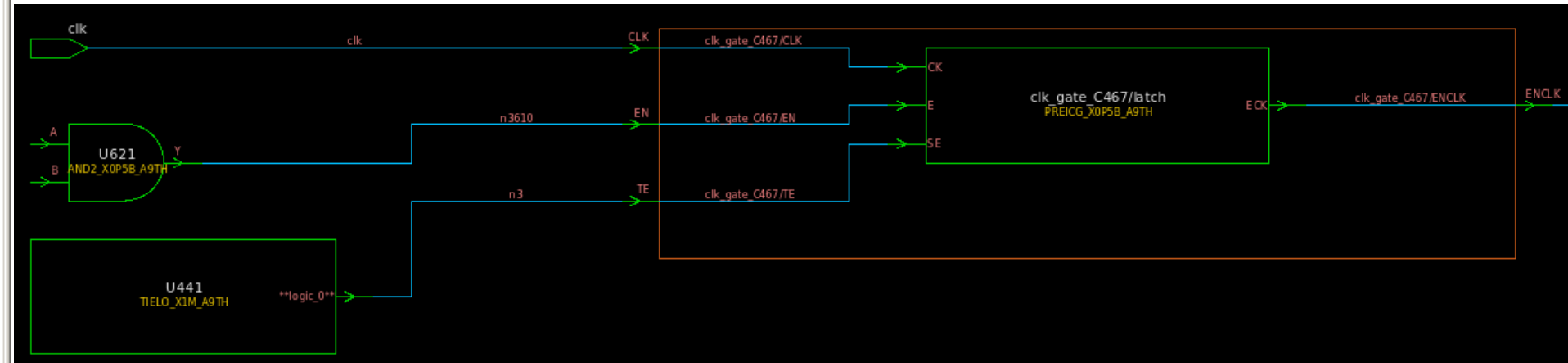



THANK YOU

感謝大家的聆聽