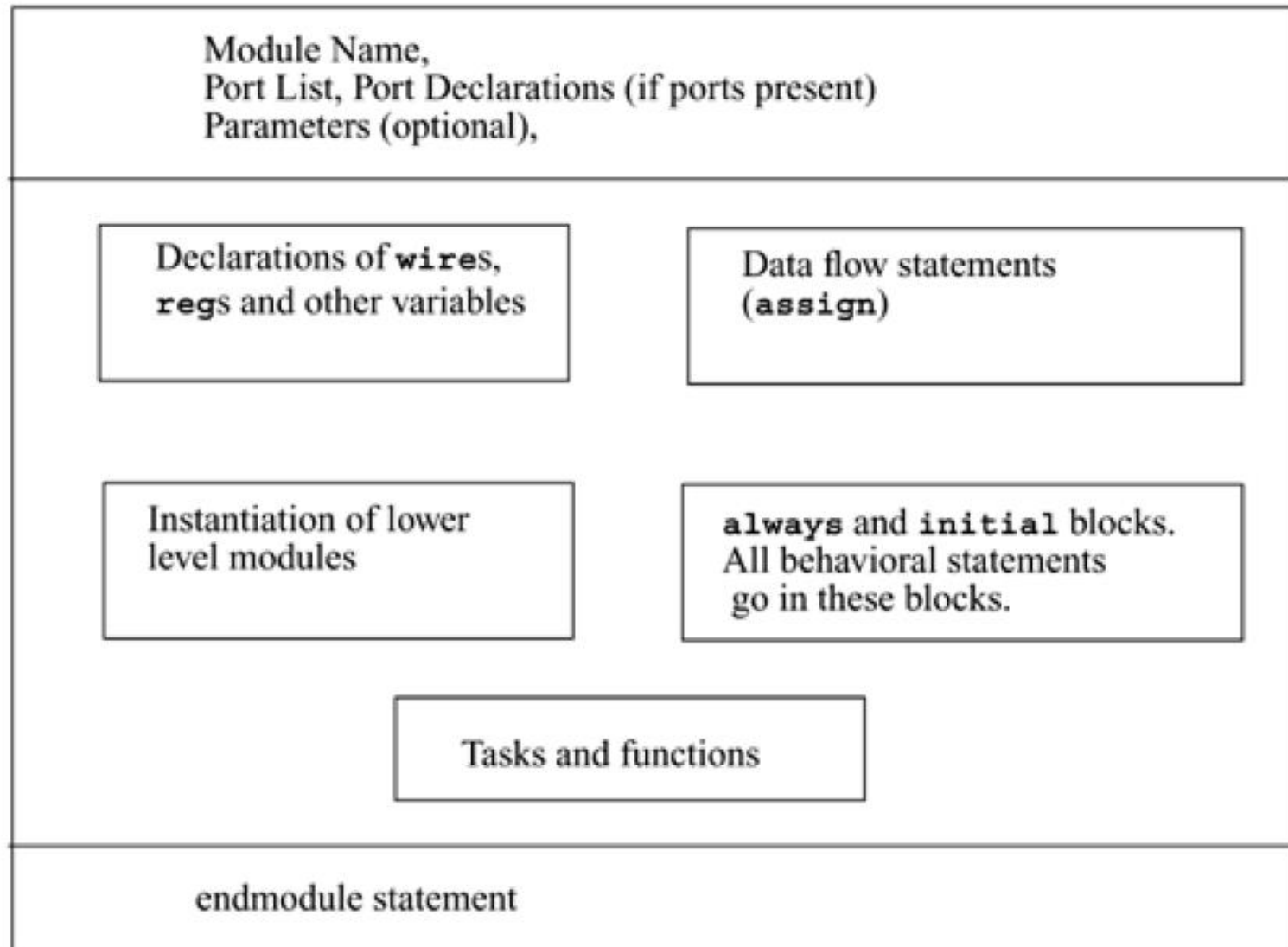


# **midterm exam. review**

S

# **Basic Concept of Verilog**

# Components of a Verilog Module



**module** M (P1, P2, P3, P4);  
**input** P1, P2;  
**output** [7:0] P3;  
**inout** P4;

**reg** [7:0] R1, M1[0:1023];  
**wire** W1, W2, W3, W4;  
**wire** [3:0] W5;  
**parameter** C1=const;

**initial**  
**begin** : blockname  
    // statements  
**end**

**always**  
**begin**  
    // behavioral level statements  
**end**

// dataflow level assignments  
// continuous assignment  
**assign** W1 = expr ;

// structural level statements  
// module instances  
**COMP U1** (.PP2(W2), .PP1(W1);  
**COMP U2** (W3, W4);

**task** T1; // common task in this module  
**input** A1;  
**inout** A2;  
**output** A3;  
**begin**  
    // statements  
**end**  
**endtask**

**function** [7:0] F1; // common function in this module  
**input** A1;  
**begin**  
    // statements  
**end**  
**endfunction**

**endmodule**

# Structural, Dataflow, Behavioral Modeling

- structural modeling
  - instantiation of other modules
  - e.g. FA instance\_name (sum, cout, a, b, cin);
- dataflow modeling
  - continuous assignment **assign**
  - e.g., **assign** {cout, sum} = a + b + cin;
- behavioral modeling
  - procedural assignments inside **always @(...)** block
  - e.g.

```
reg [31:0] sum;  
reg cout;
```

```
always @ (a, b, cin)  
    {cout, sum} = a + b + cin;
```

# Statements inside Behavioral Modeling

**#delay** // neglected during synthesis

**wait** (expression)

**@**(A **or** B **or** C)

**@**(**posedge** clk)

Reg = expression; // blocking assignment

Reg <= expression; // non-blocking assignment

**if** (condition1) ... **else if** (condition2) ... **else** ...

**case** (selection)

choice1 : **begin** ... **end**

choice2, choice 3: ...

...

**default** : ...

**endcase**

**for** (i=1; i<max; i=i+1) **begin** ... **end**

**repeat** (8) ...

**while** (condition) ...

# Verilog Operators

`a = ~b // not b (unary operator); only one operand: b`

`// output could be multiple bits, the same bit-width as the input`

`a = b && c; // logical AND operation (binary operator)`

`// two operands: b, c`

`// output a is either TRUE (logic 1) or FALSE (logic 0)`

`// cp. a = b & c; // bitwise (bit-by-bit) operator`

`// output of bit-wise operator could be multi-bit`

`// with the same bit-width as that of inputs`

`a = b ? c : d; // MUX2 (ternary operator)`

`// a=c if b=1,`

`// a=d if b=0`

`// three operands: b, c, d`

# Other operators

- arithmetic operators (+, -, \*, /, %, \*\*)
- relational operators (<, >, <=, >=)
- equality operators (==, !=, ===, !==)
- logical operators (&&, ||, !)
- bitwise operators (~, &, |, ^, ~^)
- reduction operators (&, ~&, , |, ~|, , ^, ~^)
- shift operators (>>, <<, >>>, <<<)
- concatenation operator ({ })
- conditional operator (? :)



# Equality Operator: Logical vs. Case

- logical equality operator (**==**)

<b>==</b>	0	1	X	Z
0	1	0	X	X
1	0	1	X	X
X	X	X	X	X
Z	X	X	X	X

- case equality operator (**===**)

<b>===</b>	0	1	X	Z
0	1	0	0	0
1	0	1	0	0
X	0	0	1	0
Z	0	0	0	1

# reduction operator

- perform bitwise operator on all bits of a single vector and yield a 1-bit result

- e.g.

$X = 4'b1010$

$\&X \quad // = 1\&0\&1\&0 = 1'b0$

$|X \quad // = 1|0|1|0 = 1'b1$

$\^X \quad // = 1\^0\^1\^0 = 1'b0$

# Concatenation Operator

## Replication Operator

- $A=1'b1$ ,  $B=2'b01$ ,  $C=2'b10$
- concatenation operator  
 $Y=\{B,C\} = 4'b0110$
- replication operator  
 $Y=\{ 4\{A\}, 2\{B\} \}=8'b1111\_0101$

# Number

unsized numbers (decimal by default)

sized numbers:

**<size>'<base format> <number>**

<size>: the number of bits

'<base>: 'd (decimal),

'h (hexadecimal),

'b (binary),

'o (octal)

' is the single quote symbol, **not** back quote symbol ` which will be used in compiler directive such as **`include**

e.g.

4'**b**1111 // 4-bit binary number  $1111_2 = 15_{10}$

12'**h**abc // 12-bit hexadecimal number =  $1010\_1011\_1100_2$

16'**d**255 // 16-bit decimal number =  $0000000011111111_2$

# Four-Valued Logic System

- Signal and variable values represented using a 4-valued logic system
  - 1'b0: 1-bit binary logic 0 value
  - 1'b1: 1-bit binary logic 1 value
  - 1'bx: 1-bit binary 'x' or 'X' value
    - ✓ Unknown value, produced for uninitialized values or values driven to conflicting values by more than one signal source
  - 1'bz: 1-bit binary 'z' or 'Z' value
    - ✓ High impedance value, produced when a wire is **disconnected** from all signal sources driving that wire, i.e., floating node

# data types (**wire** and **reg**)

- Nets (**wire**): connections between hardware elements
  - nets have values continuously driven by the outputs of devices that they are connected toeg.: **wire** a, b, c;  
**wire** a = b & c; // equivalent to **wire** a; **assign** a = b & c;
- Registers (**reg**): data storage element
  - a variable that can hold a value in procedural blocks starting with **always** or **initial**
  - *not necessarily* mean a flip-flop (one-bit register) in real circuiteg.: **reg** reset;
- SystemVerilog use **logic** to replace 4-value **wire** and **reg** to avoid confusion
  - not all **reg** data types synthesize into hardware registers

# data types (vectors)

- Vectors: multiple bit widths (default is scalar)
    - wire [7:0]** bus; // 8-bit signal, bus[7] is the MSB, bus[0] is the LSB
    - wire [31:0]** word; // 32-bit word
    - reg [255:0]** data; // 256-bit word register, data[255] is MSB
    - reg [0:40]** v\_addr; // v\_addr[0] is MSB
  - Vector Part Select
    - word[7:0] // the least significant byte of the 32-bit vector word
    - v\_addr[0:1] // two most significant bits of the vector v\_addr
  - variable vector part select
    - [<starting\_bit> +: width]** : part-select *increments*
    - [<starting\_bit> -: width]** : part-select *decrements*
    - starting bit can be varied, but the width must be constant***
- eg1.: **reg** [255:0] data1; // MSB->LSB with decreasing index order  
      **reg** [0:255] data2; // MSB->LSB with increasing index order  
      **reg** [7:0] byte;
- byte=data1[31 -:8] // data1[31:24]  
      byte=data1[24 +:8] // data1[31:24]  
      byte=data2[31 -:8] // data2[24:31]  
      byte=data2[24 +:8] // data2[24:31]
- eg2. **reg** [255:0] data1;  
      **for** (j=0; j<=31; j=j+1) byte = **data1[(j\*8)+:8]** ;  
      // sequence is [7:0], [15:8], [23:16], ..., [255:248]

# register data types (**integer**, **real**, **time**)

- **integer**: register data type used for signed quantity
  - **reg** store a multi-bit signal which could mean a *unsigned* quantity, while **integer** store *signed* quantity
  - eg., **integer** counter; counter = -1; // used as a counter
- **real**: real number constant or register data type
  - eg. **real** delta;
  - delta = 4e10; delta = 2.14; // delta is a real variable
- **time**: register data type to store simulation time
  - eg. **time** save\_sim\_time;
  - save\_sim\_time = **\$time**; // define a time variable
  - // system task **\$time** is invoked to get current simulation time
- **real** and **time** are non-synthesizable codes for simulation only



# signed vs. unsigned

- unsigned (default Verilog data type)

```
wire [3:0] x;  
wire [7:0] y;  
  
assign y = {4'b0000, x};
```

```
wire [3:0] x;  
wire [7:0] y;  
  
assign y = x; // zero padded
```

- signed (new data type added in 2001)

```
wire signed [3:0] x;  
wire signed [7:0] y;  
  
assign y = {4{x[3]}, x};
```

```
wire signed [3:0] x;  
wire signed [7:0] y;  
  
assign y = x; // sign-extended
```

```
wire [11:0] s1;  
wire signed [11:0] s2;  
  
assign s2 = $signed(s1); // convert to signed number  
// assign s1 = $unsigned(s2); // convert to unsigned number
```

# data types (array and memory)

- Arrays

```
reg [4:0] port_id [0:7];
```

```
// array of 8 elements, with each element 5-bit wide
```

```
port_id[6] = 5`b00000; // the array element with index=6
```

```
reg [63:0] array_4d [15:0] [7:0] [7:0] [255:0];
```

```
// 4-d array, new Verilog, IEEE1364-2001
```

- Memory (register files, RAM, ROM)

```
reg [7:0] membyte [0:1023]; // 1K bytes (1024x8) memory
```

```
data = membyte[511] // fetch 1 byte whose address id=511
```

- Use tool-supported memory generator/compiler (instead of registers) to create hardware SRAM memory instead of flip-flop-based memory array

# bit-vector vs. array

- `wire [31:0] x;`
  - declare a 32-bit signal `x`
  - all 32 bits are packed into a word `x`
  - more efficient in simulation
- `wire x [31:0];`
  - declare an array `x` with 32 elements `x[31]`, `x[30]`, ..., `x[1]`, `x[0]` where each element is 1-bit
  - not efficient in simulation
- `wire [31:0] x[31:0];`
  - declare an array `x` with 32 elements `x[31]`, `x[30]`, ..., `x[1]`, `x[0]` where each element is 32-bit

# data type (parameter)

- Parameters
  - allows constants to be defined in a module
  - parameter values for each module instance can be overridden individually at compile time

**parameter** cache\_line\_width = 256;

// constant defined inside a module

// parameter values can be changed

// at module instantiation **#()** or by using **defparam**

**localparam** // parameter values cannot be changed

state1=4'b0001,

state2=4'b0010,

state3=4'b0100,

state4=4'b1000;

# Notes on Dataflow Statements (1/2)

- dataflow statements with continuous assignment usually describe “combinational logic”
  - pure feed-forward datapath
  - LHS signal should be different from the RHS signals
  - e.g., assign c=a+b; // describe an adder
  - e.g., assign d=c+1; // describe an adder with one input=1
  - e.g., assign c=c+1; // c in LHS and RHS !!! not OK
    - ✓ a loop in the datapath
  - use register in behavioral modeling to describe a counter
  - e.g.,

```
// behavioral statements are inside always block  
// draw the hardware of the following statements  
reg [7:0] c;  
always @ (posedge clk)  
    c <= c+1;
```

# Notes on Dataflow Statements (2/2)

- all dataflow statements are concurrent
  - different order of statements results in same hardware
  - e.g.,

```
// an adder, a subtractor,  
// and a multiplier  
wire [7:0] a, b, c, d  
assign c=a+b;  
assign d=a-b;  
assign e=c*d;
```

```
// a subtractor, a multiplier,  
// and an adder  
wire [7:0] a, b, c, d  
assign d=a-b;  
assign e=c*d;  
assign c=a+b;
```
- similar behavioral statements could describe the same combinational logic
  - e.g., inside always block

```
reg [7:0] a, b, c, d;  
always @(a, b, c, d)  
begin  
    c=a+b;  
    d=a-b;  
    e=c*d;  
end
```

# **Verilog System Tasks**

# System Tasks **\$task\_name**

- **\$display**
  - display values of variables or strings or expressions
  - \$display**("at time **%d** address is **%h**", **\$time**, addr);
- **\$monitor**
  - continuously monitor a signal *when its value is changed*
  - unlike **\$display**, **\$monitor** only needs to be invoked once
  - use **\$monitoroff** and **\$monitoron** to disable/enable
  - \$monitor** ( **\$time**, "clock = **%b** reset = **%b**", clk, rst);
- **\$stop**
  - suspend the simulation for debug
- **\$finish**
  - terminate simulation



# **\$strobe vs. \$display**

- **\$display**

- if many other statements are executed in the same time unit as the task **\$display**, the execution order of the statements and **\$display** task is non-deterministic (depending on all the scheduled events at that time)

- **\$strobe**

- task **\$strobe** is always executed after all other assignment statements in the same time unit have executed
- provide synchronization mechanism to display data only after all other assignments are executed

# Compiler Directives ` (back quote)

- **`define**
  - define text macro for later text macro substitution

```
`define WORD_SIZE 32  
// used as `WORD_SIZE in the code such as  
// wire [`WORD_SIZE-1:0] a, b, c;
```
- **`include**
  - include a Verilog source file in another file

```
`include header.v //include the file header.v
```
- **`ifdef**
  - conditional compilation

```
`ifdef TEST module test;  
// compile module test only if text macro TEST  
// is defined using `define TEST
```
- **`timescale**

```
`timescale 100ns/1ns
```

# **`define`ifdef`else`endif**

```
`define TEXT_MACRO_NAME // comment out this line if do not want this definition
...
// do not confuse with if ... else in always procedure block which synthesize MUX
// compiler directive `ifdef ... `else ... does not synthesize MUX hardware
`ifdef TEXT_MACRO_NAME // conditional compilation with `else
    // compile the following statements here if TEXT_MACRO_NAME is defined
    ...
`else // `else compiler directive is optional
    // compile the following statements here if TEXT_MACRO_NAME is not defined
    ...
`endif

`ifdef TEXT_MACRO_NAME // conditional compilation without `else
    // compile the following statements here if TEXT_MACRO_NAME is defined
    // the following statements are skipped if TEXT_MACRO_NAME is not defined
    ...
`endif
```

# **Structural-Level (Gate-Level) Modeling**


# structural modeling

- component instantiation
  - Verilog *built-in* gate primitives (**not, and, or, nand, nor, xor, xnor, ...**)
  - module instantiation (from previously user defined modules)
- component connectivity
  - connecting by ordered lists (ordered by position)  
fulladd4 fa\_ordered (**EXT\_SUM, EXT\_C\_OUT, EXT\_A, EXT\_B, EXT\_C\_IN**)
  - connecting by name (order by name)  
fulladd4 fa\_byname  
(**.c\_out(EXT\_C\_OUT), .sum(EXT\_SUM), .b(EXT\_B), .c\_in(EXT\_C\_IN), .a(EXT\_A)**);
 
# Port Declaration (1995 vs. 2001)


```
// IEEE 1364-1995 (old)
module fulladd4(sum, c_out, a, b, c_in);
parameter width = 4;
output [width-1:0] sum;
output c_out;
input [width-1:0] a, b;
input c_in;
reg [width-1:0] sum;
reg c_out;
...
endmodule
```

```
// ANSI C style (IEEE 1364-2001)
module
  # (parameter width =4)
  fulladd4 (
    output reg [width-1:0] sum,
    output reg c_out,
    input [width-1:0] a, b,
    input c_in
  );
  ...
endmodule
```



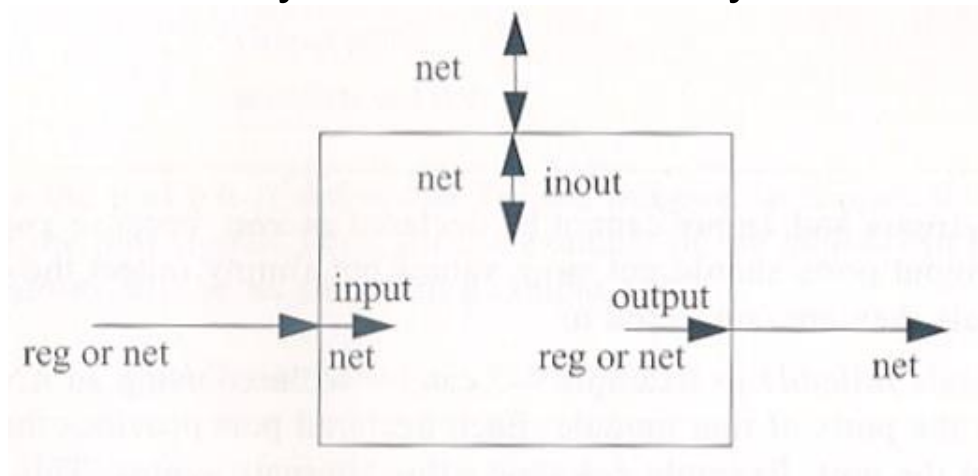
# Port Connection Rules

- all port declarations are implicitly declared as net **wire**
- **input** and **inout** cannot be declared as **reg**
- **input**
  - internally (inside the module), always be of the type **wire**
  - externally (outside the module), can be connected to **reg** or **wire**
- **output**
  - internally, can be **reg** or **wire**
  - externally, always connected to **wire**
- **inout**
  - always be **wire** internally or externally



 **Latched module provides  
Enough driving strength,  
And break critical path**



# Verilog predefined gates

- basic logic gate as predefined (built-in) gate primitives

- **and, or, nand, not, xor, xnor**


- ✓ eg., **and** a1(out, in1, in2);

- **buff, not**

- ✓ eg., **buff** b1(out1, in1);

- **bufif1, bufif0, notif1, notif0** // tristate buffers/inverters

- ✓ eg., **bufif1** b1(out, in, ctrl);

 

- array of instances

```
wire [7:0] out, in1, in2;
```

```
nand n_gate [7:0] (out, in1, in2);
```

```
/* equivalent to following 8 instances
```

```
nand n_gate0 (out[0], in1[0], in2[0];
```


```
nand n_gate1 (out[1], in1[1], in2[1];
```

```
...
```

```
nand n_gate7 (out[7], in1[7], in2[7]; */
```




# 4:1 Multiplexer (MUX4)

 

// structural level modeling of MUX
 
```
module mux4_to_1
    (out, i0, i1, i2, i3, s1, s0);
output out;
input i0, i1, i2, i3, s0, s1;
wire s1n, s0n, y0, y1, y2, y3;
    not (s1n, s1);
    not (s0n, s0);
    and (y0, i0, s1n, s0n);
    and (y1, i1, s1n, s0);
    and (y2, i2, s1, s0n);
    and (y3, i3, s1, s0);
    or (out, y0, y1, y2, y3);
endmodule
```



s1	s0	out
0	0	I0
0	1	I1
1	0	I2
1	1	I3

// behavioral level modeling of MUX

```
module mux4_to_1
    (output reg out, input i0, i1, i2, i3, s1, s0);

    // output wire out, assign out = s1 ? (s0 ? I3 : I2) : (s0 ? I1 : I0);
    //
    always @ (i0, i1, i2, i3, s0, s1) // sensitivity list
    begin
        case ({s1, s0})
            2'b00: out = i0;
            2'b01: out = i1;
            2'b10: out = i2;
            2'b11: out = i3;
            default: $display("invalid control signals");
        endcase
    end
endmodule
```

# structural MUX4 using bufit1

- use Verilog built-in gate primitives bufif1 and bufif0 to construct MUX2
- use three MUX2 to construct MUX4


# 1-bit Full Adder

// *structural (gate)* level modeling

```
module fulladd(sum, c_out, a, b, c_in);  
output sum, c_out;  
input a, b, c_in;  
wire s1, c1, c2;
```

```
    xor (s1, a, b); // assign  $s1 = a \oplus b$ ;  
    and (c1, a, b); // assign  $c1 = a \& b$ ;  
    xor (sum, s1, c_in);  
    and (c2, s1, c_in);  
    xor (c_out, c2, c1);
```

**endmodule**

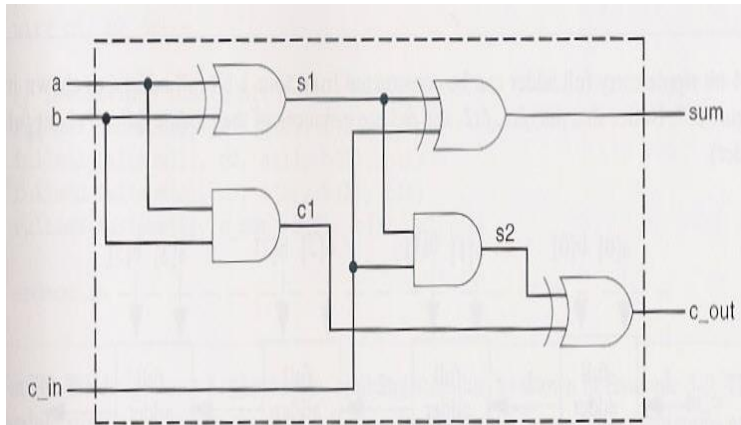

// *dataflow* modeling, continuous assignment

```
module fulladd (sum, c_out, a, b, c_in);  
output sum, c_out;  
input a, b, c_in;
```

```
    assign {c_out, sum} = a + b + c_in;  
    // synthesized gate netlist depends on  
    // area/delay constraints from users
```

**endmodule**

// *behavioral* level modeling

```
module fulladd (sum, c_out, a, b, c_in);  
output reg sum, c_out;  
input a, b, c_in;
```

```
    always @ (a or b or c_in)  
        {c_out, sum} = a + b + c_in;
```

**endmodule**

# 4-bit Ripple Carry Adder (RCA)


```
// structural level modeling
module fulladd4 (sum, c_out, a, b, c_in);

output [3:0] sum;
output c_out;
input [3:0] a, b;
input c_in

wire c1, c2, c3;
// construct 4-bit adder fulladd4 from
// previously defined module fulladd

    fulladd fa0 (sum[0], c1, a[0], b[0], c_in);
    fulladd fa1 (sum[1], c2, a[1], b[1], c1);
    fulladd fa2 (sum[2], c3, a[2], b[2], c2);
    fulladd fa3 (sum[3], c_out, a[3], b[3], c3);

endmodule
```

 

```
// dataflow level modeling
// using continuous assignment
module FA_dataflow
    (output [3:0] sum,
     output c_out,
     input [3:0] a, b,
     input c_in);

    assign {c_out, sum} = a+b+c_in;
// synthesized gate netlist depends on
// area/delay constraints from users

endmodule
```

```
// behavioral level modeling
module FA_behavior
    (output reg [3:0] sum,
     output reg c_out,
     input [3:0] a, b,
     input c_in);

    always @(a, b, c_in)
        {c_out, sum} = a+b+c_in;

endmodule
```

# RCA with **generate** loop

- use **generate** loop to duplicate module instances
  - e.g. in FA-cascaded RCA
- or simple
  - **array of instances**

```
// structural level modeling
module RCA (sum, c_out, a, b, c_in);

output [3:0] sum;
output c_out;
input [3:0] a, b;
input c_in;

wire c1, c2, c3;
// construct 4-bit adder fulladd4 from
// previously defined module fulladd

fulladd fa0 (sum[0], c1, a[0], b[0], c_in);
fulladd fa1 (sum[1], c2, a[1], b[1], c1);
fulladd fa2 (sum[2], c3, a[2], b[2], c2);
fulladd fa3 (sum[3], c_out, a[3], b[3], c3);

endmodule
```

```
module RCA_generate (sum, c_out, a, b, c_in);
parameter N=4;
output [N-1:0] sum;
output c_out;
input [N-1:0] a, b;
input c_in;
wire [N:0] c;

assign c[0]=c_in;

genvar i;
generate
  for (i=0; i<=N-1; i=i+1)
    begin: FA_loop // block named "FA_loop"
      fulladd fa (sum[i], c[i+1], a[i], b[i], c[i]);
      // fulladd FA_loop[0].fa ( sum[0], c[1], a[0], b[0], c[0] );
      // fulladd FA_loop[1].fa ( sum[1], c[2], a[1], b[1], c[1] );
      // fulladd FA_loop[2].fa ( sum[2], c[3], a[2], b[2], c[2] );
      // fulladd FA_loop[3].fa ( sum[3], c[4], a[3], b[3], c[3] );
    end
endgenerate

// fulladd FA_loop[0:3] (sum[0:3], c[1:4], a[0:3], b[0:3], c[0:3]);

assign c_out = c[N];

endmodule
```

# generate blocks

- allow Verilog code to be generated *dynamically* at the elaboration time (before simulation)
  - HDL compiler usually contain two stages: compilation and elaboration
- help the creation of parameterized models
- applications
  - same operation or module instance is repeated
    - ✓ eg., 64-b ripple carry adder (cascaded of 64 FA cells)
  - certain Verilog code is conditionally included based on parameter definitions
    - ✓ e.g., Booth or non-Booth multiplier based on bit-width

# generate loop

- allow multiple instantiation, or duplication of statements
- note that **generate** should be used **outside** of procedural blocks (**always**, **initial**)

```
module bitwise_xor(out, i0, i1);
parameter N=32;
output [N-1:0] out;
input [N-1:0] i0, i1;

genvar j; // var. j is local
generate
    for (j=0; j<N; j=j+1)
        begin: xor_loop
            xor g(out[j], i0[j], i1[j]);
        end
// hierarchical name referencing:
// xor_loop[0].g, xor_loop[1].g, ...,
endgenerate
// xor xor_loop[0].g(out[0], i0[0], i1[0]);
// xor xor_loop[1].g(out[1], i0[1], i1[1]);
...
// xor xor_loop[31].g(out[31], i0[31], i1[31]);
endmodule
```

```
// alternate style (behavioral level)
reg [N-1:0] out;

genvar j;
generate
    for (j=0; j<N; j=j+1)
        begin: bit
            always @(i0[j] or i1[j]) out[j] = i0[j] ^ i1[j];
        end
// always @(i0[0], i1[0]) out[0]=i0[0]^i1[0];
// always @(i0[1], i1[1]) out[1]=i0[1]^i1[1];
...
// always @(i0[31], i1[31]) out[31]=i0[31]^i1[31];
endgenerate
```

# generated ripple carry adder

```

module ripple_adder(co, sum, a0, a1, ci);
parameter N=4;
output [N-1:0] sum;
output co;
input [N-1:0] a0, a1;
input ci;
wire [N:0] carry;

```

```

assign carry[0]=ci;

```

```

genvar i;
generate

```

```

    for (i=0; i<N; i=i+1)
    begin: r_loop

```

```

        wire s1, c1, t3;
        xor g1(s1, a0[i], a1[i]);
        xor g2(sum[i], s1, carry[i]);
        and g3(c1, a0[i], a1[i]);
        and g4(s2, s1, carry[i]);
        xor g5(carry[i+1], c1, s2);

```

```

    end

```

```

endgenerate

```

```


assign co = carry[N]

```

```

endmodule

```

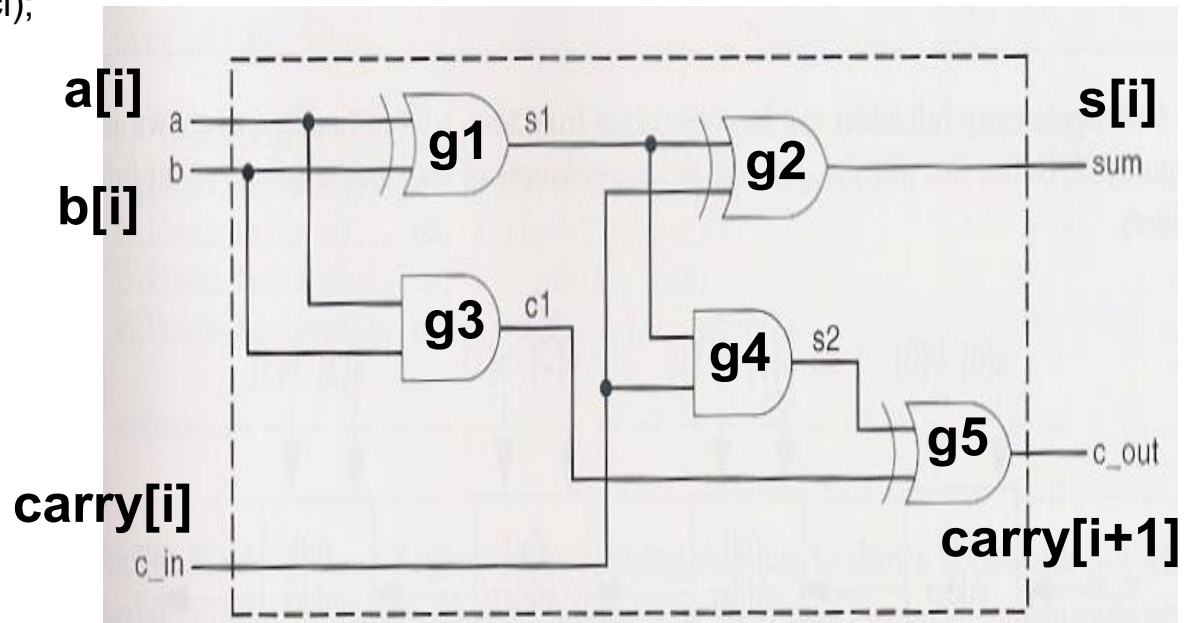

// the following hierarchical instance names are generated

```

// xor r_loop[0].g1(...); xor r_loop[1].g1(...); ...
// xor r_loop[0].g2(...); xor r_loop[1].g2(...); ...
// and r_loop[0].g3(...); and r_loop[1].g3(...); ...
// and r_loop[0].g4(...); and r_loop[1].g4(...); ...
// xor r_loop[0].g5(...); xor r_loop[1].g5(...); ...

```



# RCA with **generate** loop

- use **generate** loop to duplicate module instances
  - e.g. in FA-cascaded RCA
- or simple
  - **array of instances**

```
// structural level modeling
module RCA (sum, c_out, a, b, c_in);

    output [3:0] sum;
    output c_out;
    input [3:0] a, b;
    input c_in;

    wire c1, c2, c3;

    // construct 4-bit adder fulladd4 from
    // previously defined module fulladd

    fulladd fa0 (sum[0], c1, a[0], b[0], c_in);
    fulladd fa1 (sum[1], c2, a[1], b[1], c1);
    fulladd fa2 (sum[2], c3, a[2], b[2], c2);
    fulladd fa3 (sum[3], c_out, a[3], b[3], c3);

endmodule
```

```
module RCA_generate (sum, c_out, a, b, c_in);
    parameter N=4;
    output [N-1:0] sum;
    output c_out;
    input [N-1:0] a, b;
    input c_in;
    wire [N:0] c;

    assign c[0]=c_in;

    genvar i;
    generate
        for (i=0; i<=N-1; i=i+1)
            begin: FA_loop // block named "FA_loop"
                fulladd fa (sum[i], c[i+1], a[i], b[i], c[i]);
                // fulladd FA_loop[0].fa ( sum[0], c[1], a[0], b[0], c[0] );
                // fulladd FA_loop[1].fa ( sum[1], c[2], a[1], b[1], c[1] );
                // fulladd FA_loop[2].fa ( sum[2], c[3], a[2], b[2], c[2] );
                // fulladd FA_loop[3].fa ( sum[3], c[4], a[3], b[3], c[3] );
            end
    endgenerate

    // fulladd FA_loop[0:3] (sum[0:3], c[1:4], a[0:3], b[0:3], c[0:3]);

    assign c_out = c[N];

endmodule
```

# generate case

```
module adder (co, sum, a0, a1, ci);

parameter N=4;

output [N-1:0] sum;
output co;
input [N-1:0] a0, a1;
input ci;

// instantiate different modules depending on input bitwidth
generate
    case (N)
        1 : adder_1bit    adder1(co, sum, a0, a1, ci);
        2 : adder_2bit    adder2(co, sum, a0, a1, ci);
        default : adder_cla #(N) adder3(co, sum, a0, a1, ci);
    endcase
endgenerate

endmodule
```

```
module top ( ....);
...
adder #(1) add1 (co1, s1, a1, b1);
// adder_1bit add1 (co1, s1,, a1, b1);
...
adder #(2) add2 (co2, s2, a2, b2);
// adder_2bit add2 (co2, s2, a2, b2);
...
adder #(8) add3 (co3, s3, a3, b3);
// adder_cla add3 (co3, s3, a3, b3);
...
adder #(32) add4 (co4, s4, a4, b4);
// adder_cla #(32) add4 (co4, s4, a4, b4);
.....
endmodule
```

# min/typ/max delays



```
// with Verilog-XL option +mindelays, delay=4  
// with Verilog-XL option +typdelays, delay=5  
// with Verilog-XL option +maxdelays, delay=6  
and #(4:5:6) a1(out, i1, i2);
```

```
// if +mindelays, rise=3, fall=5, turn-off=min(3,5)  
// if +typdelays, rise=4, fall=6, turn-off=min(4,6)  
// if +maxdelays, rise=5, fall=7, turn-off=min(5,7)  
and #(3:4:5, 5:6:7) a2(out, i1, i2);
```

```
// in fact, #() overwrite default parameters originally defined  
// in a module during module instantiation
```
 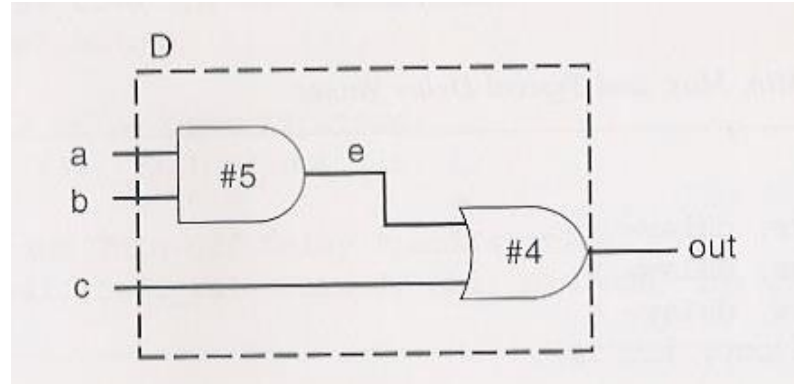
# Delay Example

```
module D (out, a, b, c);  
  output out;  
  input a, b, c;  
  wire e;  
  and #(5) a1(e, a, b);  
  or #(4) o1(out, e, c);  
endmodule
```



# Timing Analysis Tools

- Static timing analysis (STA)
  - Generate critical path delay without providing inputs
  - e.g., Synopsys Design
  - Might have false path delay which does not exist for any input combination
  - Can also generate power information, but not accurate for clock gating circuits
- Dynamic timing analysis
  - Generate the longest delay based on a sequence of user-specified inputs
  - e.g., Synopsys PrimeTime
  - Might not extract the critical path delay if the provided input changes does not activate the critical path
  - Could also generate power information with clock gating

# Dataflow Modeling

(continuous assignment: **assign**)

# Continuous Assignment (**assign**)

- most basic statement in dataflow modeling
- Continuously drive a value onto a **net (wire)**
  - Compared with *procedural assignment* in a behavioral block (**always**)
- replace gates in the description of circuits at a higher level of abstraction (dataflow model)
  - Describe **combinational logic**

```
wire [31:0] i1, i2, out;  
assign out = i1 | i2; // LHS is wire data type  
// or (out, i1, i2)
```

```
// operator | denotes bitwise OR operation  
// out must be a net (wire)
```

# Implicit Continuous Assignments

- // regular continuous assignment  
**wire** out; // wire is default data type  
**assign** out = in1 & in2;\
- // implicit continuous assignment  
**wire** out = in1 & in2; // no keyword **assign**
- // implicit net declaration  
**wire** in1, in2;  
**assign** #10 out = in1 & in2;  
// implicit net declaration of out as **wire**  
// wait for 10 time units (#10, delay control), then  
// sample values of in1, in2, calculate in1&in2,  
// and assign to out



# Operator Types

- arithmetic (+, -)
- logical (!, &&, ||)
- relational (>, <)
- equality (==, ===, !=, !==)
- bitwise (~, &, |, ^)
- reduction (&, ~&)
- shift (<<, <<<, >>, >>>)
- concatenation ({ })
- conditional (? :)

Operator Type	Operator Symbol	Operation Performed	Number of Operands
Arithmetic	*	multiply	two
	/	divide	two
	+	add	two
	-	subtract	two
	%	modulus	two
Logical	**	power (exponent)	two
	!	logical negation	one
	&& 	logical and logical or	two two
Relational	>	greater than	two
	<	less than	two
	>=	greater than or equal	two
	<=	less than or equal	two
Equality	==	equality	two
	!=	inequality	two
	===	case equality	two
	!==	case inequality	two
Bitwise	~	bitwise negation	one
	&	bitwise and	two
		bitwise or	two
	^	bitwise xor	two
	^~ or ~^	bitwise xnor	two
Reduction	&	reduction and	one
	~&	reduction nand	one
		reduction or	one
	~	reduction nor	one
	^ or ~^	reduction xor reduction xnor	one one

Shift	>>	Right shift	Two
	<<	Left shift	Two
	>>>	Arithmetic right shift	Two
	<<<	Arithmetic left shift	Two
Concatenation	{ }	Concatenation	Any number
Replication	{ { } }	Replication	Any number
Conditional	? :	Conditional	Three

# Logical Shift (<<, >>) versus Arithmetic Shift (<<<, >>>)

```
// Verilog-2001
```

```
integer data_value,  
        data_value_1995,  
        data_value_2001;
```

```
...  
data_value = -9;                // stored as 1111_..._1111_0111
```

```
...  
data_value_1995 = data_value >> 3; // stored as 0001_..._1111_1110
```

```
...  
data_value_2001 = data_value >>> 3; // stored as 1111_..._1111_1110  
                                   // repeat sign bit during arithmetic right shift
```

```
...  
data_value_1995 = data_value << 3; // stored as 1111_..._1011_1000
```

```
...  
data_value_2001 = data_value <<< 3; // stored as 1111_..._1011_1000  
                                   // repeat sign bit during arithmetic left shift
```

```
// give an example where the logical left shift << 3 is different from arithmetic shift
```

```
// e.g., data_value2 = 32'b 1110_xxx ....
```

# Example (4-to-1 Multiplexer)

```
// using logic equations  
module mux4_logic (out, i0,  
    i1, i2, i3, s1, s0);
```

```
output out;  
input i0, i1, i2, i3, s0, s1;
```

```
assign out =  
(~s1 & ~s0 & i0) |  
(~s1 & s0 & i1) |  
(s1 & ~s0 & i2) |  
(s1 & s0 & i3);
```


```
endmodule
```

```
// using conditional operator  
module mux4_cond (out, i0,  
    i1, i2, i3, s0, s1);
```

```
output out;  
input i0, i1, i2, i3, s0, s1;
```

```
assign out = s1 ?  
( s0 ? i3 : i2) : (s0 ? i1 : i0);
```

```
endmodule
```

 

# Example (4-bit adder)

```
// using dataflow
// with proper synthesis constraint

module add4 (sum, c_out, a, b, c_in);
output [3:0] sum;
output c_out;
input [3:0] a, b;
input c_in;

// gate-level structure
// depends on synthesis constraints
assign {c_out, sum} = a + b + c_in;

endmodule
```

$$p_i = a_i \oplus b_i, \quad g_i = a_i b_i, \quad c_{i+1} = g_i + p_i c_i$$

$$c_1 = g_0 + p_0 c_{in}$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_{in}$$

$$c_3 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_{in}$$

$$c_4 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 c_{in}$$

$$s_i = p_i \oplus c_i$$

```
// explicit carry lookahead adder using p and g

module add4 (sum, c_out, a, b, c_in);
output [3:0] sum;
output c_out;
input [3:0] a, b;
input c_in;
wire p0, g0, p1, g1, p2, g2, p3, g3;
wire c4, c3, c2, c1;

assign p0=a[0]^b[0], p1=a[1]^b[1], p2=a[2]^b[2],
        p3=a[3]^b[3];
assign g0=a[0]&b[0], g1=a[1]&b[1], g2=a[2]&b[2],
        g3=a[3]&b[3];
assign c1 = g0|(p0&c_in),
        c2=g1|(p1&g0)|(p1&p0&c_in),
        c3=g2|(p2&g1)|(p2&p1&g0)|(p2&p1&p0&c_in),
        c4=g3|(p3&g2)|(p3&p2&g1)|(p3&p2&p1&g0)
            |(p3&p2&p1&p0&c_in);
assign sum[0] = p0 ^ c_in, sum[1] = p1 ^ c1,
        sum[2]=p2 ^ c2, sum[3] = p3 ^ c3;
assign c_out = c4;

endmodule
```

# **Behavioral Modeling**

# Procedural Assignments

- two structured procedures
  - **always** (SystemVerilog uses **always\_ff**, **always\_comb**, **always\_latch**)
  - **Initial** (not synthesizable)
- procedural assignments update LHS values of
  - **reg** (SystemVerilog uses **logic** to replace **reg** for avoiding confusion)
  - **integer**
  - **real** (non-synthesizable)
  - **time** (non-synthesizable)
- The value placed on a variable remain unchanged until another procedural assignment updates the variable with a different value
  - unlike continuous assignments (using **assign**) in dataflow where one assignment can cause the value of RHS expression to be continuously placed on the LHS expression

# **always** statement

- starts at time 0 and executes the statements in the always block repeated *ly in a looping fashion*
- used to model a block of activity that is repeated continuously in a digital circuit
- usually include timing/event control (e.g., @posedge) or sensitivity list (e.g., @(a, b, c, ...) )

```
module clock_gen (output reg clock);  
    initial clock = 1'b0;           // executed only once  
    always #10 clock = ~clock;    // executed continuously  
    initial #1000 $finish;         // finish execution at time step = 1000  
endmodule
```

# behavioral modeling

- statements inside **begin** ... **end** are executed *sequentially*
- statements inside **fork** ... **join** are executed *in parallel*
  - **fork** ... **join** block is not synthesizable
- Event-driven procedures: **always**, **initial**
- Sequential blocks: **begin...end**
- Parallel blocks: **fork...join**

```
module MyModule(...);  
  .  
  initial @(...) ↓  
  .  
  always @(...) ↻  
  .  
  always @(...) ↻  
  .  
endmodule
```

<pre>always @(...) begin → . . . End</pre>	<pre>initial @(...) begin → . . . end</pre>
<pre>always @(...) fork → . → . → . join</pre>	<pre>initial @(...) fork → . → . → . join</pre>



# behavioral statements

## (used inside initial or always blocks)

- procedural assignments
  - blocking ( **=** ) vs. non-blocking ( **<=** )
  - operators (such as +, -, \*, &, |, ^, ?:, ...)
  - timing control **#**, event control **@**
- conditional statements (**if ... else...**)
- multi-way branching (**case ... endcase**)
- looping statement
  - **while, repeat, for, forever**
- sequential and parallel blocks
  - sequential block (**begin ... end**)
  - parallel block (**fork ... join**)

# Sequential logic

- flip-flop using non-blocking assignment **<=**

```
module FF (q, d, clk);  
  output q;  
  input d, clk;  
  reg q; // LHS of procedural statement should be data type reg  
  
  always @(posedge clk)  
    q <= d; // non-blocking assignment <=  
  
endmodule
```

- flip-flop with active-low asynchronous reset

```
Module FF_asyn_rst (q, d, clk, reset);  
  output q;  
  input d, clk, reset;  
  reg q;  
  
  always @(posedge clk or negedge reset) // use negedge for active-low control signal  
    if (~reset) q <= 1'b0;  
    else q <= d;  
  
endmodule
```

# Combinational logic

- Use blocking assignment =

```
module adder32 (a, b, sum);  
  output [31:0] sum;  
  input [31:0] a, b ;  
  reg sum;  
  
  always @( a or b)  
    sum = a + b; // blocking assignment =  
  
endmodule
```

- could use similar continuous assignment assign

```
module adder32 (a, b, sum);  
  output [31:0] sum;  
  input [31:0] a, b ;  
  wire sum;  
  
  assign sum = a + b; // continuous assignment assign  
  
endmodule
```




# Sequencing Elements (Latch and Flip-Flop)


   
## Latch: *Level sensitive*

- pass input to output at **time interval** when level of control is logic 1
- a.k.a. transparent latch

```
// Verilog code for latch
always @ (CLK or D)
  if (CLK) Q <= D;
```



## Flip-Flop: *edge triggered*


- pass input to output at the **moment** of clock rising or falling edge
- a.k.a. opaque edge-triggered flip-flop

```
// Verilog code for DFF
always @ (posedge CLK)
  Q <= D;
```
 
# inferring a D-latch

- Model a latch using not fully specified **if ..**
- Model a multiplexer using fully specified **if ... else ...**

```
module d_latch (GATE, DATA, Q);  
    input GATE, DATA;  
    output Q;  
    reg Q;  
  
    always @(GATE or DATA)  
        if (GATE)  
            Q = DATA;  
  
endmodule
```




```
module d_CL (  
    input gate, data,  
    output reg q );  
  
    // infer a combinational logic,  
    // not a latch  
    always @ (gate or data)  
        if (gate)  
            q = data;  
        else  
            q = 'b0;  
  
endmodule
```
 
# inferring a D-flip-flop

- Model a flip-flop (FF) using non-blocking assignment ( **<=** ) with *edge-triggered* event ( **@posedge** or **@negedge** )
  - c.p. latch modeling using *level-sensitive* event

```
module dff_pos (DATA, CLK, Q);  
  input DATA, CLK;  
  output Q;  
  reg Q;  
  
  always @(posedge CLK)  
    Q <= DATA;  
endmodule
```



# Shift registers

## using non-blocking statements

- each flip-flop shift to its neighbor, except for the two boundary FFs that acts as input and output registers
- line buffer (in CNN hardware) is realized by shift registers
- quiz: how to model a long shift registers ?
  - $\{ sr[1:n-1], out \} \leq \{ d, sr[1:n-1] \};$  // n shift registers:  $\{ sr[1:n-1], out \}$

```
// shift register, OK
always @(posedge clock)
begin
    reg1 <= d;
    reg2 <= reg1;
    reg3 <= reg2;
    out  <= reg3;
end
```


```
// 4 FFs with same input d
// problematic ?
always @(posedge clock)
begin
    reg1 = d;
    reg2 = reg1;
    reg3 = reg2;
    out  = reg3;
end
```

# synthesis of non-blocking and blocking
 
## (shift registers vs. multi-bit register with same input)


- non-blocking assignment (  $\leq$  )

```
module rtl (clk, data, regc, regd);  
input data, clk;  
output regc, regd;  
  
reg regc, regd;  
  
always @(posedge clk)  
begin  
    regc <= data;  
    regd <= regc;  
end  
endmodule
```



- blocking assignment ( = )
 
```
module rtl (clk, data, rega, regb);  
input data, clk;  
output rega, regb;  
  
reg rega, regb;  
  
always @(posedge clk)  
begin  
    rega = data;  
    regb = rega;  
end  
endmodule
```





 
# FF with Asynchronous reset (active-high)

- Reset FF content whenever reset=high (active high), independent of clock signal (asynchronous)
  - Event of edge-triggered clk and reset signals
- remember to Initialize register content before execution using resettable DFFs
  - **initial** is not synthesizable, only used in simulation


```
module dff_async_reset (DATA, CLK, RESET, Q);  
  input DATA, CLK, RESET;  
  output Q;  
  reg Q;  
  
  always @(posedge CLK or posedge RESET)  
    if (RESET)  
      Q <= 1'b0;  
    else  
      Q <= DATA;  
endmodule
```


 
# DFF with Synchronous set (active-high)

- sensitive list includes only clock signal
  - synthesized into normal DFF with extra combinational logic for the input data

```
module dff_sync_set (DATA, CLK, SET, Q);  
  input DATA, CLK, SET;  
  output Q;  
  reg Q;  
  
  //synopsys sync_set_reset "SET"  
  always @(posedge CLK)  
    if (SET)  
      Q <= 1'b1;  
    else  
      Q <= DATA;  
endmodule
```




# Separation of Combinational and Sequential Logic

- use blocking assignment (=) for combinational logic
- use non-blocking assignment (<=) for sequential logic
- do not mix blocking and non-blocking assignments in a single always block

```
// model CL using =  
always @ (a or b or c or d) begin  
    w1 = a & b;  
    w2 = c | d;  
    s = w1 + w2;  
end
```
 
```
// model SL using <=  
always @(posedge clk) begin  
    q <= s;  
end
```



```
// merged CL and SL  
always @(posedge clk) begin  
    q <= (a & b) + (c | d);  
end
```

# Pipelined $A*B+C$

```
module pipelined (  
  input [31:0] A, B;  
  input [63:0] C;  
  input clk;  
  output [63:0] final_out);  
  
  reg [63:0] pipe1_C, pipe1_AB, pipe2_out;  
  
  always @ (posedge clk) begin  
    pipe1_AB <= A*B;  
    pipe1_C <= C;  
  end  
  
  always @(posedge clk)  
    pipe2_out <= pipe1_AB + pipe1_C;  
  
  assign final_out = pipe2_out;  
  
endmodule
```

# Use of **@\***, or **@(\*)** for CL

```
always @(a or b or c or d or e or f or g or h or p or m)
begin
out1 = a ? b+c: d+e;    // out1, out2 should be reg
out2 = f ? g+h: p+m;
end
```

// all input variables are included automatically

```
always @(*) // IEEE 1364-2001
```

```
begin
```



```
out1 = a ? b+c: d+e;
```

```
out2 = f ? g+h: p+m;
```

```
end
```
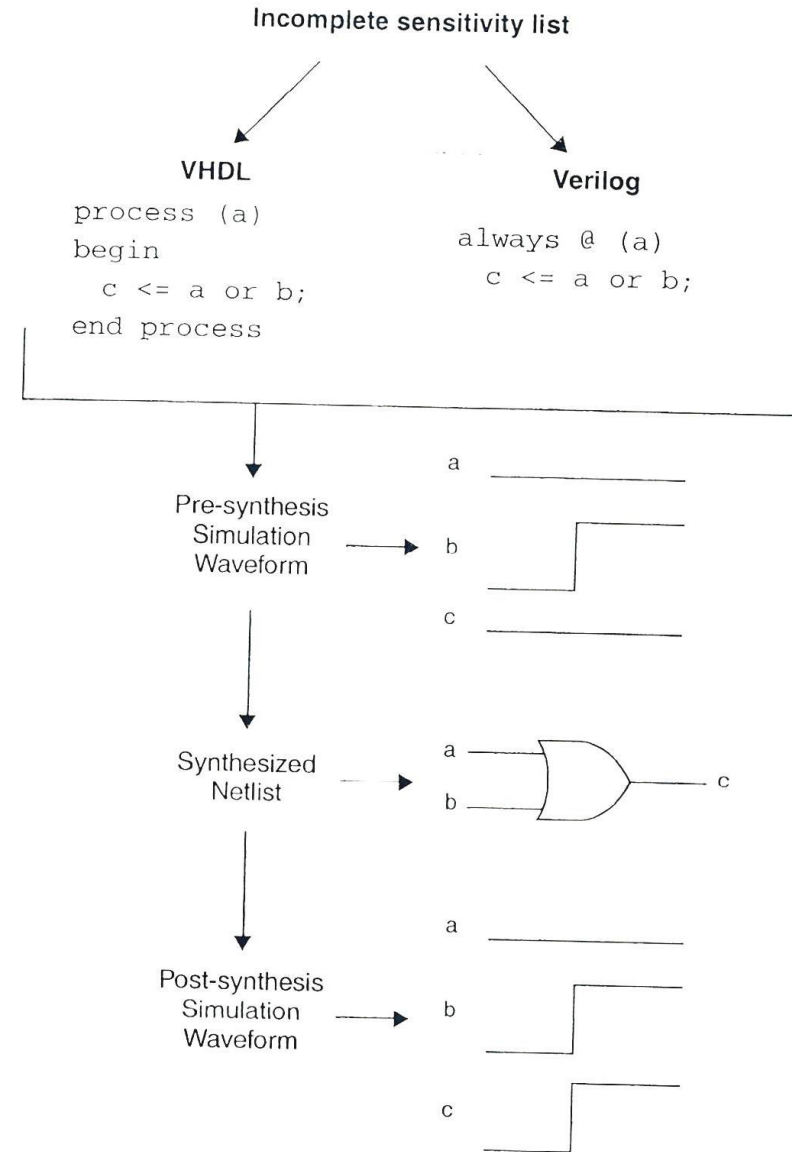 
# simulation mismatch due to incomplete sensitivity list

- make sure that sensitivity lists contain only necessary signals
  - e.g. always @(\*) ... for pure CL
  - missing signals in sensitivity list cause mis-match in RTL (pre-synthesis) simulation and gate-level (post-synthesis) simulation
- adding unnecessary sensitivity list slows down simulation



# conditional statements (**if ... else ...**)

```
if (!lock) buffer = data;  
if (enable) out = in; // infer a latch  
if (enable) out = in else out = d; // infer a MUX2
```

```
if (number_queued < MAX_Q_DEPTH)  
    begin    data_queue = data;  
            number_queued = number_queued + 1;  
    end  
else  
    $display ("Queue Full. Try Again");
```

```
if (alu_control == 0)    y = x + z;  
else if (alu_control == 1) y = x - z;  
else if (alu_control == 2) y = x * z;  
else $display ("Invalid ALU control sign");
```

# Unspecified Condition: Inferring Latch

- Fully specified condition
  - Describe combinational logic

```
always @ (a, b, c) begin
  if (c == 1)
    d=a+b;
  else
    d=0;
end
```

```
always @ (a, b, c) begin
  d=0;
  if (c == 1)
    d=a+b;
end
```

- Unspecified condition
  - Inferring latch to store the the previous value

```
always @ (a, b, c) begin
  if (c == 1)
    d=a+b; // d is stored in a latch controlled by c
end
```



# Multiway Branching (case Statements)

```
reg [1:0] alu_control;
```

```
...
```

```
case (alu_control)
```

```
    2'd0    : y = x + z;
```

```
    2'd1    : y = x - z;
```

```
    2'd2    : y = x * z;
```

```
    default : $display("Invalid ALU control signal");
```

```
endcase
```

```
if (alu_control == 0)      y = x + z;  
else if (alu_control == 1) y = x - z;  
else if (alu_control == 2) y = x * z;  
else $display ("Invalid ALU control sign");
```

# 4-to-1 MUX with case

```
// 4-to-1 multiplexer (i1, i2, i3, s[1:0], out)
```

```
module mux4 (out, i0, i1, i2, i3, s0, s1);
```

```
output out;
```

```
input i0, i1, i2, i3, s0, s1;
```

```
reg out;
```

```
always @(s1, s0, i0, i1, i2, i3)
```

```
case ({s1, s0})
```

```
    2'd0: out = i0;
```

```
    2'd1: out = i1;
```

```
    2'd2: out = i2;
```

```
    2'd3: out = i3;
```

```
    default: $display ("Invalid control signals");
```

```
endcase
```

```
endmodule
```

# full case and parallel case

- full case
  - all possible branches are specified
  - otherwise, **latches** are synthesized
- parallel case
  - no cases overlap (one and only one of the branches is executed each time)
  - hardware multiplexers are synthesized in parallel case
  - if not determined, hardware *priority encoder* is synthesized (such as 1xxx, x1xx, xx1x, xxx1)

# both full case and parallel case

- a hardware multiplexer is synthesized

```
// full case, and parallel case
// infer multiplexer

input [1:0] a;
always @ (a, w, x, y, z) begin
    case (a)
        2'b11: b=w;
        2'b10: b=x;
        2'b01: b=y;
        2'b00: b=z;
    endcase
end
```

# casex, casez

- **casez**
  - treat all **z** values as don't care, **z** can also be represented by **?**
- **casex**
  - treat all **z** and **x** values as don't care

```
reg [3:0] encoding;  
integer state;
```

```
// not parallel case, but full case,  
// infer priority encoder
```

```
casex (encoding)
```

```
    4'b1xxx : next_state = 3; // this case has highest priority
```

```
    4'bx1xx : next_state = 2;
```

```
    4'bxx1x : next_state = 1;
```

```
    4'bxxx1 : next_state = 0;
```

```
    default : next_state = 0;
```

```
endcase
```

# 4-to-1 multiplexer (4:1 MUX)

- input
  - in0, in1, in2, in3, s[1:0]
- output
  - out

```
reg out;  
  
always @(s, in0, in1, in2, in3)  
case (s)  
    2'b00: out = in0;  
    2'b01: out = in1;  
    2'b10: out = in2;  
    2'd11: out = in3;  
    default: $display ("Invalid control signals");  
endcase
```

# 1-to-4 demultiplexer (1:4 DEMUX)

- input
  - in, s[1:0]
- output
  - out0, out1, out2, out3
  - all outputs except the selected one are z

```
reg out0, out1, out2, out3;
```

```
always @(s, in0, in1, in2, in3)
```

```
case (s)
```

```
2'b00: begin out0 = in;    out1=1'bz; out2=1'bz; out3=1'bz; end
```

```
2'b01: begin out0 = 1'bz; out1=in;    out2=1'bz; out3=1'bz; end
```

```
2'b10: begin out0 = 1'bz; out1=1'bz; out2=in;    out3=1'bz; end
```

```
2'd11: begin out0 = 1'bz; out1=1'bz; out2=1'bz; out3=in;    end
```

```
default: $display ("Invalid control signals");
```

```
endcase
```

## 4:2 priority encoder using **case**

- input
  - in0, in1, in2, in3
- output
  - out[1:0]

```
reg [1:0] out;  
  
always @(in3, in2, in1, in0)  
  case ({in3, in2, in1, in0})  
    4'b1xxx: out = 2'b11;  
    4'b01xx: out = 2'b10;  
    4'b001x: out = 2'b01;  
    default : out = 2'b00;  
  endcase
```



# 4:2 encoder

- input
  - in0, in1, in2, in3
- output
  - out[1:0]

```
reg [1:0] out;  
reg      valid;  
  
always @(in3, in2, in1, in0)  
    valid = 1;  
    case ({i3, i2, i1, i0})  
        4'b1000: out = 2'b11;  
        4'b0100: out = 2'b10;  
        4'b0010: out = 2'b01;  
        4'b0001: out = 2'b00;  
        default : begin out = 2'bxx; valid = 0; end  
    endcase
```

# 2:4 decoder

- input
  - in[1:0]
- output
  - out0, out1, out2, out3

```
wire [1:0] in;  
reg out0, out1, out2, out3;
```

```
always @(in)
```

```
case (in)
```

```
    2'b00: begin out0=1; out1=0; out2=0; out3=0; end
```

```
    2'b01: begin out0=0; out1=1; out2=0; out3=0; end
```

```
    2'b10: begin out0=0; out1=0; out2=1; out3=0; end
```

```
    2'd11: begin out0=0; out1=0; out2=0; out3=1; end
```

```
endcase
```

# while Loop

```
integer count;

initial
begin
count = 0;
while (count < 128)
    count = count + 1;
end
```

```
`define TRUE 1'b1
`define FALSE 1'b0
reg [15:0] flag;
integer i;
reg continue;

// find the leading 1 in flag
initial
begin
flag = 16'b 0010_0000_0000_0000
i = 0;
continue = `TRUE;
while ((i<16) && continue)
    begin
        if (flag[i]) continue = `FALSE;
        i=i+1;
    end
end
```

# for Loop

- **for** loops are generally used when there is a **fixed** beginning and end to the loop
- If the loop is simply looping on a certain condition, it is better to use the **while** loop

```
integer count;  
  
initial  
for (count=0; count<128; count=count+1)  
  $display("Count=%d", count);
```

```
`define MAX_STATES 32  
integer state[0:MAX_STATES-1];  
integer i;  
  
initial  
begin  
  for (i=0; i<32; i=i+2)  
    state[i]=0;    //initialize even locations  
  for (i=1; i<32; i=i+2)  
    state[i]=1;    //initialize odd locations  
end
```

# 16-bit LOD using **for** loop (~38 gates)

```
`define TRUE 1'b1
`define FALSE 1'b0
```

```
module LZD_for (
```

```
input [15:0]din, output reg [3:0]zero_cnt); input [15:0] din, output reg [3:0] zero_cnt);
```

```
reg continue;
```

```
integer i;
```

```
// zero_cnt is the number of leading zeros
```

```
// continue is false, if leading one is found
```

```
always@(*) begin
```

```
    continue = `TRUE;
```

```
    for (i=15; continue && (i>=0); i=i-1) begin
```

```
        zero_cnt = din[i] ? 4'd15 - i : 4'd0;
```

```
        continue = din[i] ? `FALSE : `TRUE;
```

```
    end
```

```
end
```

```
endmodule
```

Hierarchical cell	Global cell area		Local cell area			Design
	Absolute Total	Percent Total	Combi-national	Noncombi-national	Black-boxes	
LZD top	339.3936	100.0	0.0000	0.0000	0.0000	LZD top
u LZD case	126.3024	37.2	126.3024	0.0000	0.0000	LZD case
u LZD for	106.5456	31.4	106.5456	0.0000	0.0000	LZD for
u LZD while	106.5456	31.4	106.5456	0.0000	0.0000	LZD while
Total			339.3936	0.0000	0.0000	

**Delay=0.33ns**

**Area=106 um x um (um<sup>2</sup>)**  
**~=(106/2.82) NAND2 gates**  
**~=38 gate equivalent**

# Quiz

- what is value of cnt if din=0000\_0000\_0000\_0000?

```
continue = `TRUE;  
for (i=15; continue && (i>=0); i=i-1) begin  
    cnt = din[i] ? 4'd15 - i : 4'd0;  
    continue = din[i] ? `FALSE : `TRUE;  
end
```

- How to change the above code to detection # of leading bits before bit-inverse ?
  - if din=0001\_xxxx\_xxxx\_xxxx, cnt=3 (din[13]=0, din[12]=1)
  - if din=1110\_xxxx\_xxxx\_xxxx, cnt=4 (din[13]=1, din[12]=0)
  - if din=0000\_0000\_0000\_0000, din=16
  - if din=0000\_0000\_0000\_0000, din=16

# example: ripple carry adder (RCA) using for loop in behavioral modeling

```
always @ (*) begin
```

```
    c[0] = cin;
```

```
    for (i=0; i<=31; i++)
```

```
        {c[i+1], s[i]} = a[i] + b[i] + c[i];
```

```
    cout = c[32];
```

```
end
```

```
// the for loop will be unrolled as follows
```

```
// {c[1],s[0]}=a[0]+b[0]+c[0];
```

```
// {c[2],s[1]}=a[1]+b[1]+c[1];
```

```
...
```

```
// {c[32],s[31]}=a[31]+b[31]+c[31];
```

# shift registers (many registers)

`x[0] <= d`

`x[1] <= x[0]`

`x[2] <= x[1]`

`...`

`x[N-2] <= x[N-3]`

`out <= x[N-2]`

```
// a total of N shift registers, each bw bits
reg [bw-1:0] x[0:N-2];
reg [bw-1:0] d, out;
always @ (posedge clk) begin
    x[0] <= d;
    for (i=1; i<=N-2; i=i+1)
        x[i] <= x[i-1];
    out <= x[N-2];
end
```

```
// a total of N shift registers
reg [bw-1:0] x[0:N-2];
reg [bw-1:0] d, out;
always @ (posedge clk) begin
    {x[0:N-2], out} <= {d, x[0:N-2]};
end
```



# Dopt Product 4 (DP4)

- 4-D dot-product:  $a[0]*b[0] + a[1]*b[1] + a[2]*b[2] + a[3]*b[3]$

```
module DP4 (input[16*4-1:0]in_a, in_b, output [31:0]out);  
  wire [15:0] a[3:0], b[3:0];
```

```
  // convert two long bit-vectors in_a, in_b into two arrays a, b  
  assign {a[3],a[2],a[1],a[0]}=in_a;  
  assign {b[3],b[2],b[1],b[0]}=in_b;
```

```
  integer i;  
  reg [31:0] tmp[0:3];  
  always @ (*) begin  
    tmp[0] = a[0]*b[0];  
    for (i=1; i<=3; i=i+1) tmp[i] = a[i]*b[i] + tmp[i-1];  
  end
```

```
  assign out = tmp[3];
```

```
endmodule
```

# DPn

- n-D dot-product

```
module #parameter n=4 DPn (input[16*n-1:0]in_a, in_b, output [31:0]out);
reg [15:0] a[n-1:0];
reg [15:0] b[n-1:0];
integer i;
always@ (*) begin // convert two long bit-vectors into two arrays
    for (i=0; i<n; i=i+1) begin
        a[i]= in_a[16*i +:16];
        b[i]= in_b[16*i +:16];
    end
end

reg [31:0] tmp[0:n];
always @ (*) begin
    tmp[0] = 0;
    for (i=0; i<=n-1; i=i+1) tmp[i+1] = a[i]*b[i] + tmp[i];
end
assign out = tmp[n];
endmodule
```

# Example: Saturation Adder


- clip the computation results to a fixed range

```
signed [7:0] a, b, sum, tmp, max, min;  
// wire [8:0] carry; // if carry out bits are known  
  
assign max = 8'd127;  
assign min = 8'd-128;  
assign tmp = a + b;  
always @ (*) begin  
    if ( a[7] == b[7] && tmp[7] != a[7] )    // carry[ [8] != carry]7]  
        sum = a[7] ? min : max; // sum = { a[7], 7{~a[7]} };  
    else  
        sum = tmp;  
end
```

# Clock Gating

 
# clock gating

```
module dff(Q, D, clk);  
input D, clk;  
output Q;  
reg Q;  
wire gclk, en;  
// clock signal is from the output of AND  
// glitch might cause extra clock edges  
assign gclk = clk & en;  
always @(posedge gclk)  
    Q <= D;  
endmodule
```



**gclk might have glitches !!!  
cause unexpected latching**

 
```
module dff(Q, D, clk);  
input D, clk;  
output Q;  
reg Q;  
wire en;  
  
// data input from MUX  
always @(posedge clk)  
if (en) begin  
    Q <= D;  
end  
endmodule
```



**The clk port might still have  
switching power!  
not efficiently reduce dynamic  
power**
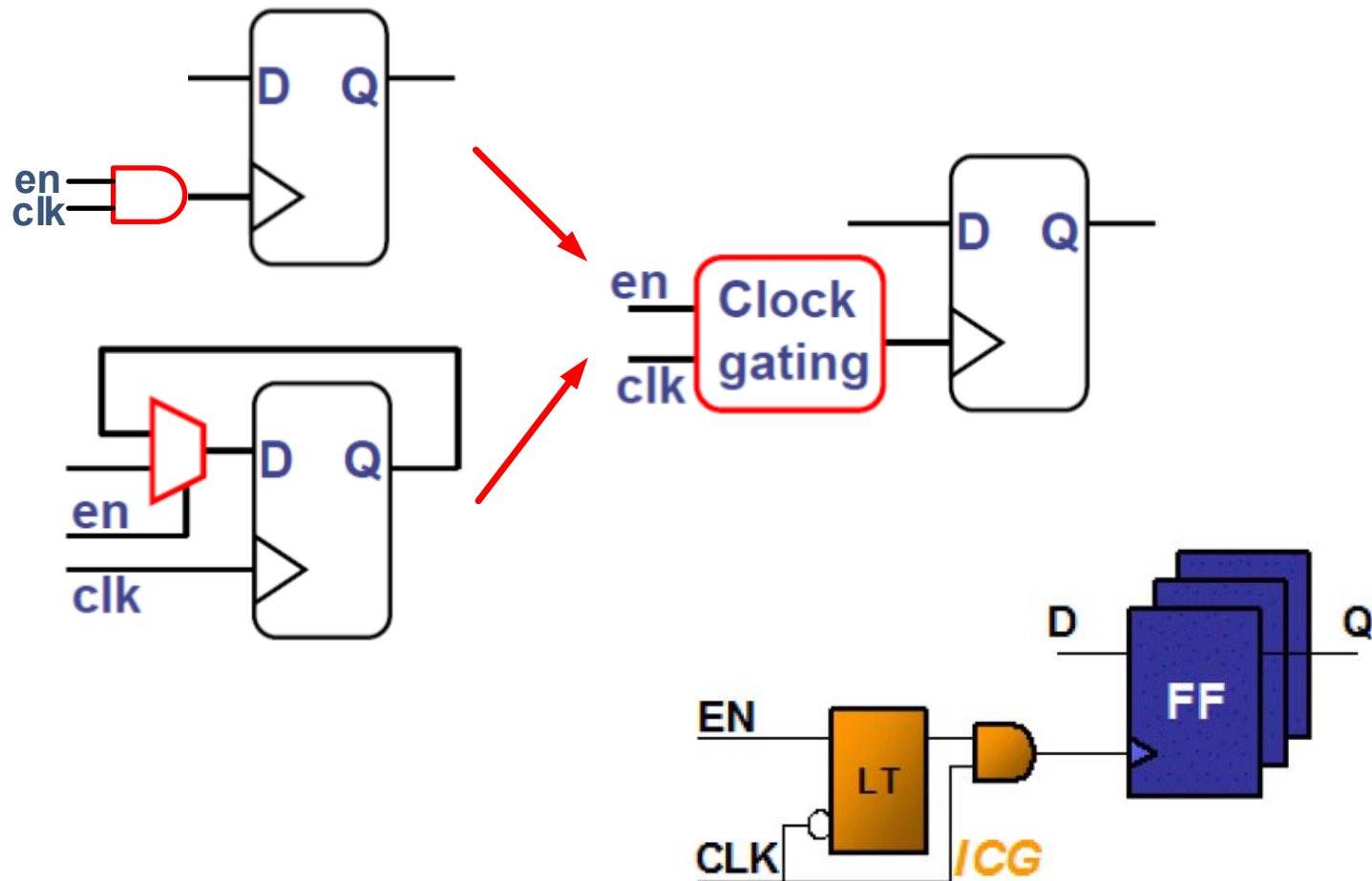
# Synthesized Clock Gating

- When synthesis is done with proper commands
  - Both designs lead to safe clock gating circuit (with latch)



# Tasks and Functions

# Tasks vs. Functions

- task is similar to subroutine in FORTRAN
- function is similar to function in FORTRAN

Table 8-1      *Tasks and Functions*

Functions	Tasks
A function can enable another function but not another task.	A task can enable other tasks and functions.
Functions always execute in 0 simulation time.	Tasks may execute in non-zero simulation time.
Functions must not contain any delay, event, or timing control statements.	Tasks may contain delay, event, or timing control statements.
Functions must have at least one <b>input</b> argument. They can have more than one <b>input</b> .	Tasks may have zero or more arguments of type <b>input</b> , <b>output</b> , or <b>inout</b> .
Functions always return a single value. They cannot have <b>output</b> or <b>inout</b> arguments.	Tasks do not return with a value, but can pass multiple values through <b>output</b> and <b>inout</b> arguments.



# Tasks vs. Functions

- defined in a module and local to the module
  - called from the **always** or **initial** blocks, or other tasks and functions
- tasks are used for commonly Verilog code
  - contain delays, timing, event constructs, or multiple output arguments
  - ***can have input, output and inout arguments***
- functions are used for code that
  - is purely **combinational**
  - executes in zero simulation time
  - provides ***exactly one output***
  - can have input arguments

# Tasks (task ... endtask)

```
module operation;
...
parameter delay=10;
reg [15:0] A, B;
reg [15:0] AB_AND, AB_OR, AB_XOR;
always @ (A or B)
begin
    bitwise_oper(AB_AND, AB_OR, AB_XOR,
        A, B);
end

...
task bitwise_oper;
output [15:0] ab_and, ab_or, ab_xor;
input [15:0] a, b;
begin
    #delay ab_and = a & b;
    ab_or = a | b;
    ab_xor = a ^ b;
end
end task

...
endmodule
```

**task could have**

**(1) multiple outputs**

**(2) delay/timing constructions**

```
// another task declaration
//
task bitwise_oper (
output [15:0] ab_and, ab_or, ab_xor,
input [15:0] a, b);
begin
    #delay ab_and = a & b;
    ab_or = a | b;
    ab_xor = a ^ b;
end
endtask
```

# Example: Asymmetric Sequence Generator

```
module sequence;
reg clk;

initial init_sequence;           // invoke task init_sequence
always asymmetric_sequence; // invoke another task

task init_sequence; begin clk= 1'b0; end endtask

task asymmetric_sequence;
begin
    #12 clk = 1'b0;
    #5  clk = 1'b1;
    #3  clk = 1'b0;
    #10 clk = 1'b1;
end endtask

endmodule
```

# Automatic (Re-entrant) Tasks

```
// all normally declared task items are statically allocated and shared.  
// automatic task allows for dynamic allocation for each invocation  
// where each task call operates in an independent memory space.  
  
module top;  
reg [15:0] cd_xor, ef_xor;  
reg [15:0] c, d, e, f;  
  
// this task can invoked concurrently with individual memory space  
task automatic bitwise_xor  
output [15:0] ab_xor;  
input [15:0] a, b;  
begin  
    ab_xor = a ^ b;  
end endtask  
  
// two tasks are called concurrently in two procedural blocks  
always @(posedge clk) bitwise_xor (ef_xor, e, f);  
always @(posedge clk2) bitwise_xor (cd_xor, c, d); // clk2 has twice frequency  
endmodule
```

# Function (**function** ... **endfunction**)

```
module parity;  
  reg [31:0] addr;  
  reg parity;  
  always @ (addr)  
    parity = calc_parity(addr);
```

```
function calc_parity;  
  input [31:0] address;  
  begin  
    calc_parity = ^address;  
  end  
endfunction  
  
endmodule
```

function could have

- (1) only one returned output
- (2) no delay/timing constructions
- (3) purely combinational

```
// alternate function definition  
function calc_parity  
  (input [31:0] address);  
  begin  
    calc_parity = ^address;  
  end  
endfunction
```

# Example: Left/Right Shifter

```
module shifter;
  'define LEFT_SHIFT 1'b0;
  'define RIGHT_SHIFT 1'b1;
  reg [31:0] addr, left_addr, right_addr;
  reg control;
  always @ (addr)
  begin
    left_addr = shift (addr, 'LEFT_SHIFT);
    right_addr = shift (addr, 'RIGHT_SHIFT);
  end

  function [31:0] shift; // function output is a 32-bit value
  input [31:0] address;
  input control;
  begin
    shift = (control == 'LEFT_SHIFT) ? (address << 1) : (address >>1);
  end
endfunction

endmodule
```

# Automatic (Recursive) Functions

```
// functions are normally used non-recursively  
// automatic function allows all function declarations allocated dynamically  
// for each recursive call  
// each call to an automatic function operates in an independent variable space.
```

```
module top;
```

```
function automatic integer factorial;
```

```
input [31:0] oper;
```

```
integer i;
```

```
begin
```

```
    if (oper >= 2 ) factorial = factorial(oper-1) * oper; // recursive functional call
```

```
    else factorial = 1;
```

```
end automatic
```

```
integer result;
```

```
initial result = factorial(4);
```

```
endmodule
```

# constant Function

## (input arguments are constant)

// the arguments to a constant function are constant expressions

```
module ram_model (address, write, chip_select, data);  
parameter data_width = 32;  
parameter ram_depth = 256;  
localparam addr_width = clogb2 (ram_depth);  
input [addr_width – 1 : 0] address;  
input write, chip_select;  
inout [data_width – 1:0] data;  
  
function integer clogb2 (input integer depth);  
begin  
    for (clogb2=0; depth >0; clogb2=clogb2+1);  
        depth = depth >> 1;  
end endfunction  
  
reg [data_width – 1:0] data_store [0:ram_depth – 1];  
.....  
endmodule
```



# signed function (returned value is signed)

```
module top;
...

function automatic signed [63:0] compute_signed (input [63:0] vector);
...      // returned function value is signed
endfunction
...
always @ ... begin
...
if (compute_signed(vector) < -3)
begin ... end
...
end
...
endmodule
```